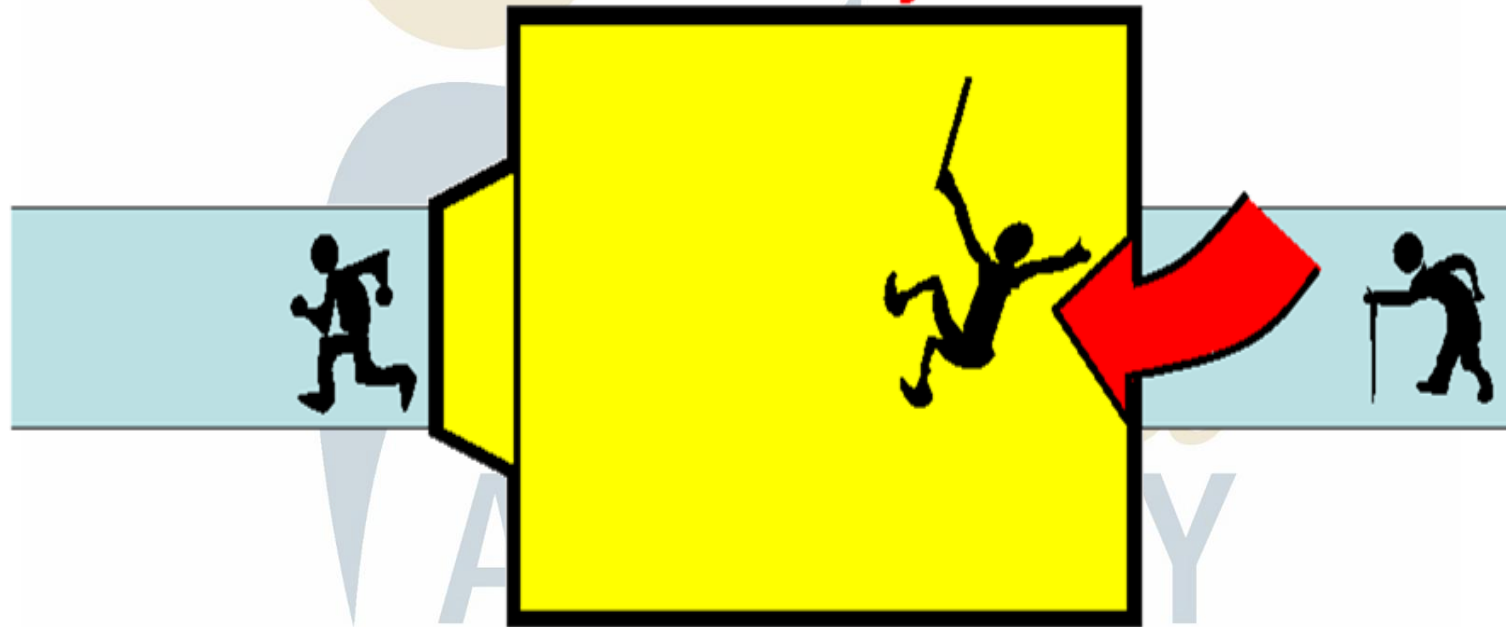


Physics – Grade 10


Unit One – Electricity

Chapter 2 – Potential Difference

Battery



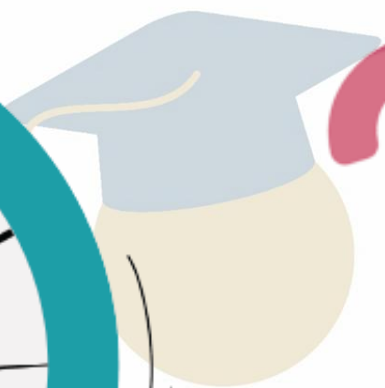Prepared & Presented by: **Mr. Mohamad Seif**



Be Smart
ACADEMY



Quiz 1

Physics

15 min



Consider battery delivers a constant voltage $V_{PN} = 12V$ connected to 6 lamps as shown in the adjacent figure.


Given L_1 and L_2 are identical

We connect a voltmeter across the terminals of L_3 , it reads $-3V$.

1. Show on figure the connections of the voltmeter.

2. What does the voltmeter read V_{DE} or V_{ED} ?

3. Calculate V_{BC} and V_{CD} , knowing that $V_{EJ} = 4V$.

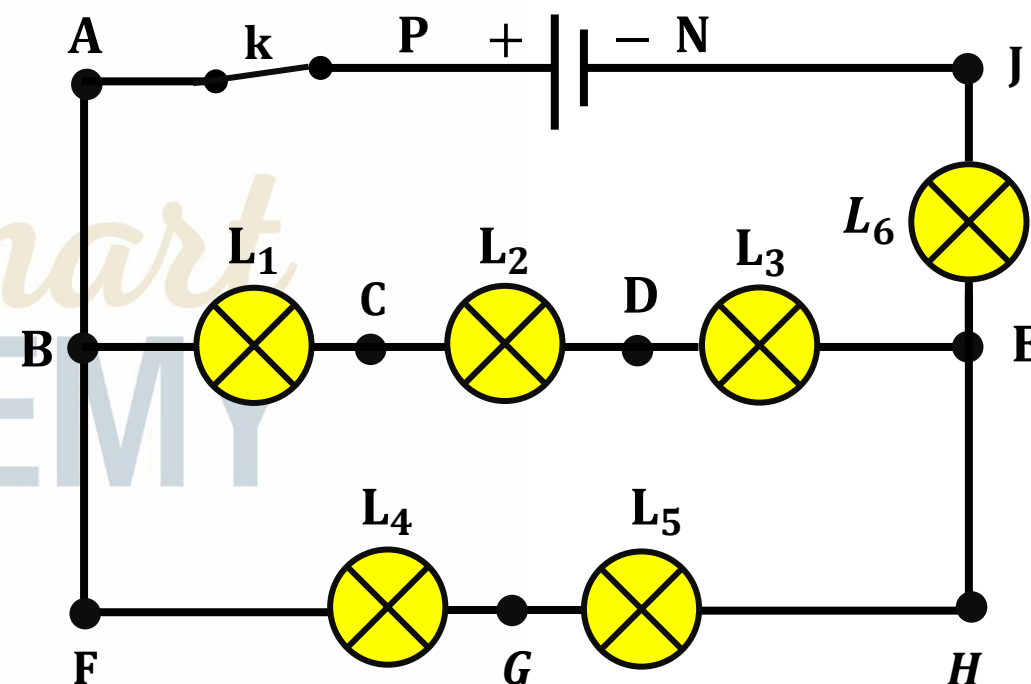

Quiz 1

Physics

15 min




$V_{PN} = 12V$; L_1 and L_2 are identical; L_4 and L_5 are identical; $y = -3V$.

1. Show on figure the connections of the voltmeter.

Since the voltmeter reads $-3V$, then the Com is connected to positive pole

2. What does the voltmeter read V_{DE} or V_{ED} ?

The voltmeter reads $V_{ED} = -3V$, because the (com) is connected to D, and the voltmeter reads from V to com.

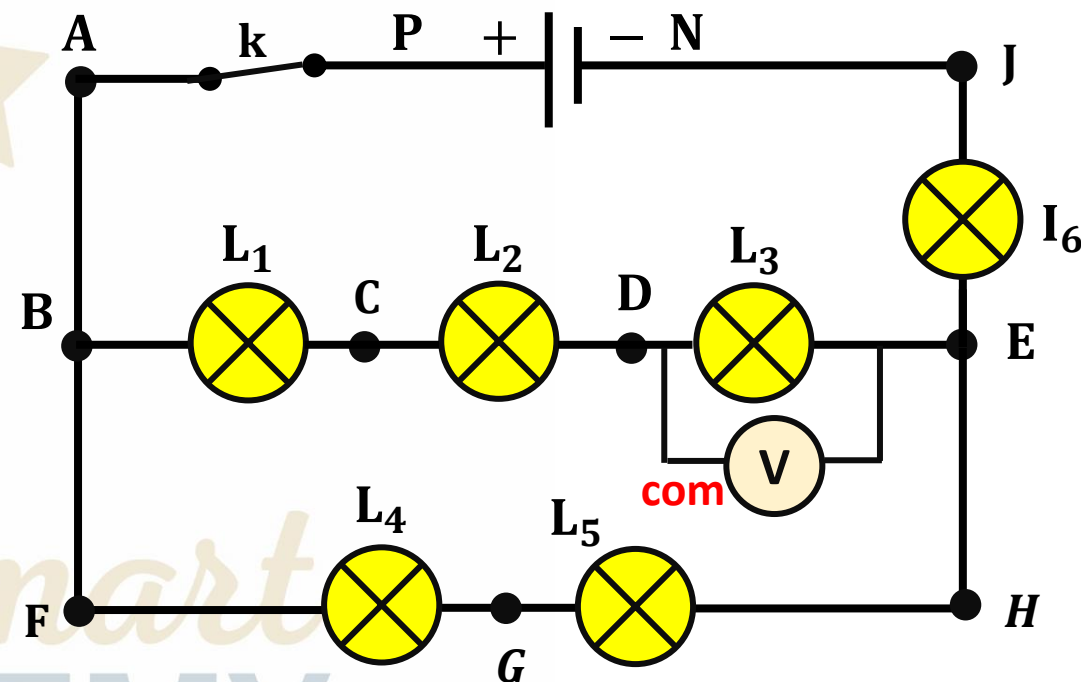

Quiz 1

Physics

15 min



$V_{PN} = 12V$; L_1 and L_2 are identical; L_4 and L_5 are identical; $y = -3V$.


3. Calculate V_{BC} and V_{CD} ,
knowing that $V_{EJ} = 4V$.

L_1 and L_2 are identical then:

$$V_{BC} = V_{CD}$$

$$V_{PN} = V_{PA} + V_{AB} + V_{BC} + V_{CD} + V_{DE} + V_{EJ} + V_{JN}$$

$$V_{PN} = V_{PA} + V_{AB} + V_{BC} + V_{BC} + V_{DE} + V_{EJ} + V_{JN}$$

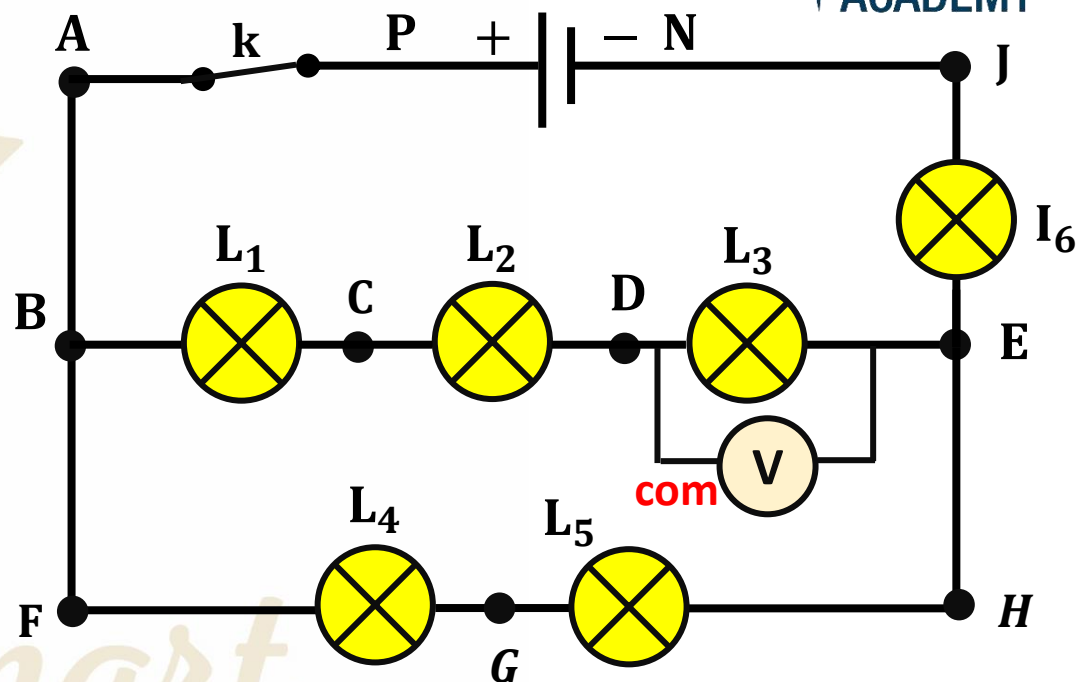

Quiz 1

Physics

15 min



$V_{PN} = 12V$; L_1 and L_2 are identical; L_4 and L_5 are identical; $y = -3V$.

$$V_{PN} = V_{PA} + V_{AB} + V_{BC} + V_{BC} + V_{DE} + V_{EJ} + V_{JN}$$


$$12V = 0V + 0V + 2V_{BC} + 3V + 4V + 0V$$

$$12V = 2V_{BC} + 7V$$

$$12V - 7V = 2V_{BC}$$

$$5V = 2V_{BC} \quad V_{BC} = \frac{5V}{2} = 2.5V$$

$$V_{BC} = V_{CD} = 2.5V$$

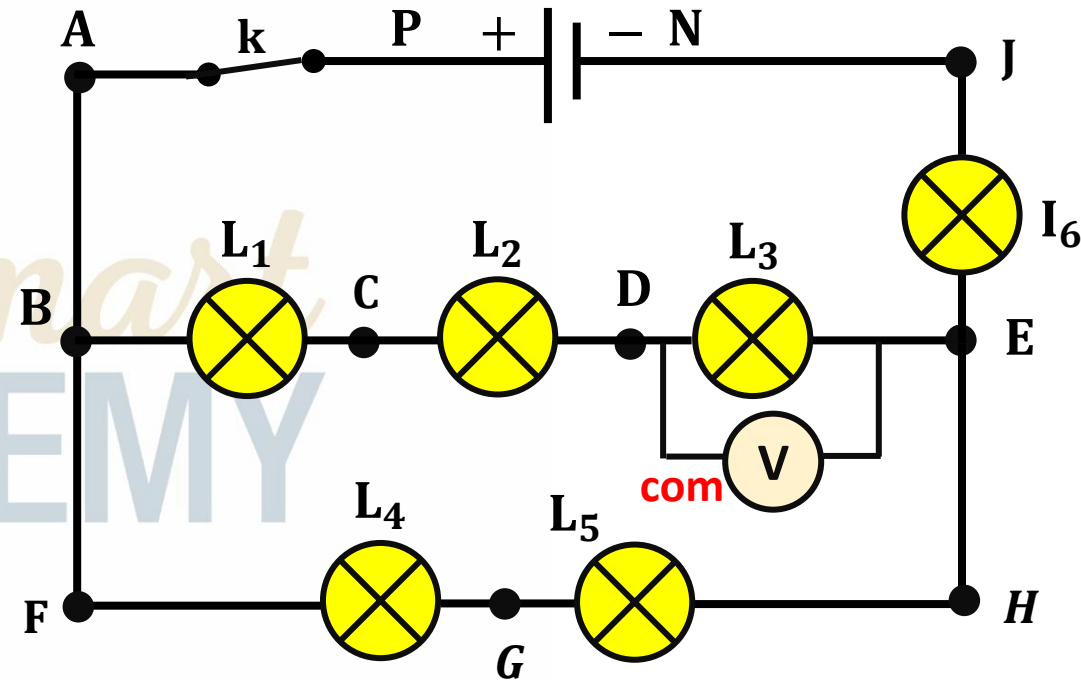

Quiz 1


Physics

15 min



Now an oscilloscope are connected across the terminals of L_4 . Doc 2 shows a screen of an oscilloscope ($S_V = 3V/\text{div}$).

- Show on figure the connections of the oscilloscope across L_4 .
- Calculate the voltage across L_4 .
- Calculate the potential difference across L_5 .
- B is a reference potential. Determine the electric potentials V_C and V_E .

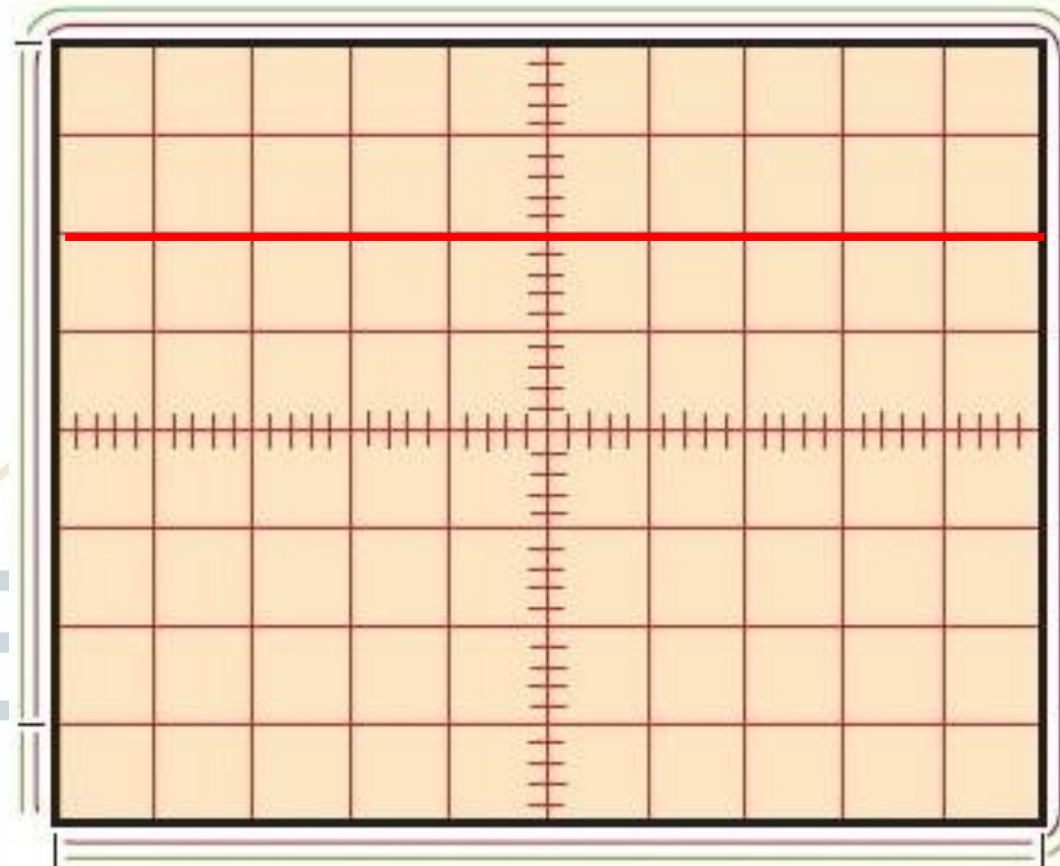

Quiz 1

Physics

15 min



a) Show on figure the connections of the oscilloscope across L_4 .


Since the luminous line moves up, then phase connected to F and ground connected to G.

b) Calculate the voltage across L_4 .

$$V_{FG} = S_V \times y$$

$$V_{FG} = 3V/\text{div} \times 2\text{div}$$

$$V_{FG} = 6V$$

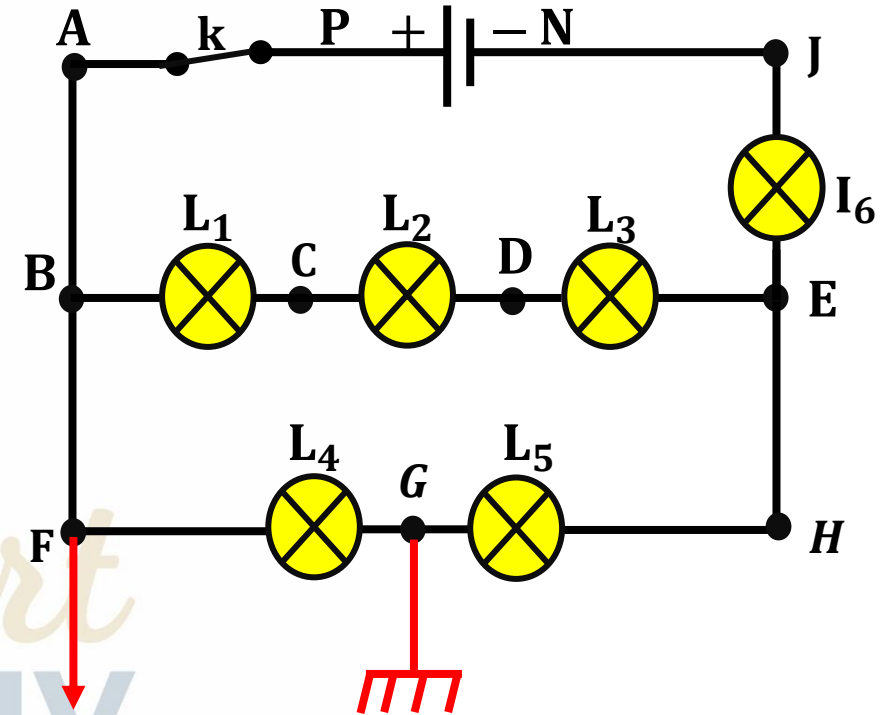

Quiz 1

Physics

15 min



c) Calculate the potential difference across L_5 .

Using law of addition of voltage:


$$V_{PN} = V_{PA} + V_{AB} + V_{BF} + V_{FG} + V_{GH} + V_{HE} + V_{EJ} + V_{JN}$$

$$12V = 0V + 0V + 0V + 6V + V_{GH} + 0V + 4V + 0V$$

$$12V = 10V + V_{GH}$$

$$12V - 10V = V_{GH}$$

$$V_{GH} = 2V$$

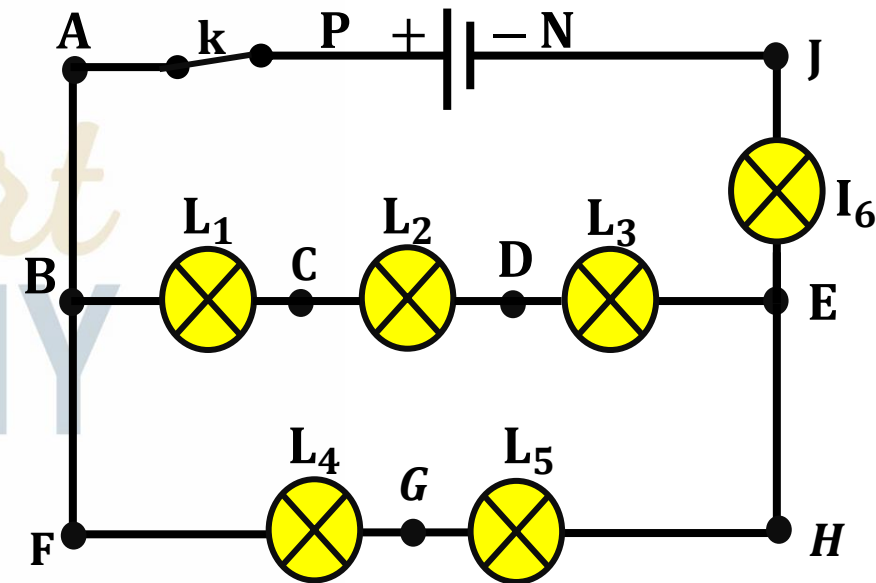

Quiz 1

Physics

15 min



d) B is a reference potential. Determine the electric potentials V_C and V_E .

$$V_{BC} = V_B - V_C$$

$$2.5V = 0V - V_C$$


$$V_C = -2.5V$$

$$V_{CD} = V_C - V_D \quad 2.5V = -2.5V - V_D$$

$$V_D = -5V$$

$$V_{DE} = V_D - V_E \quad 3V = -5 - V_E$$

$$V_D = 8V$$

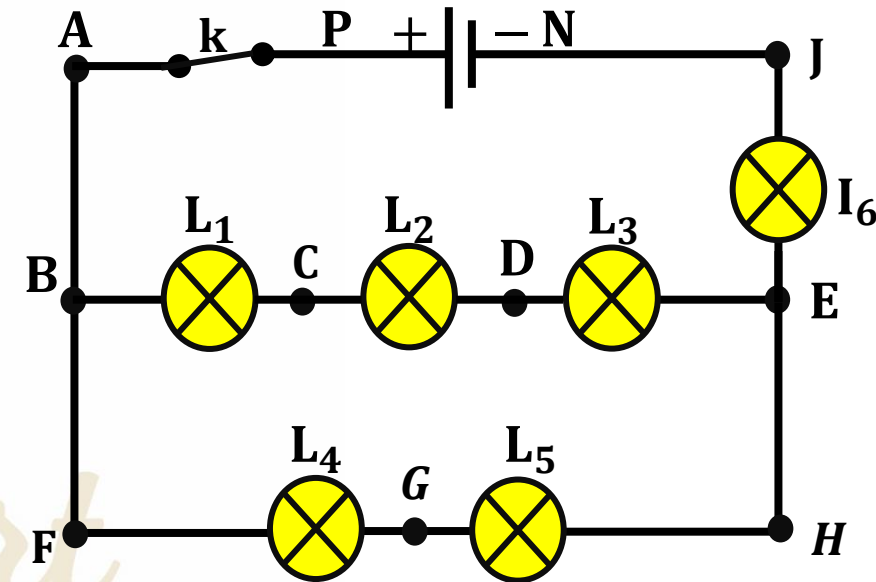

The End





Be Smart Academy

ACADEMY

