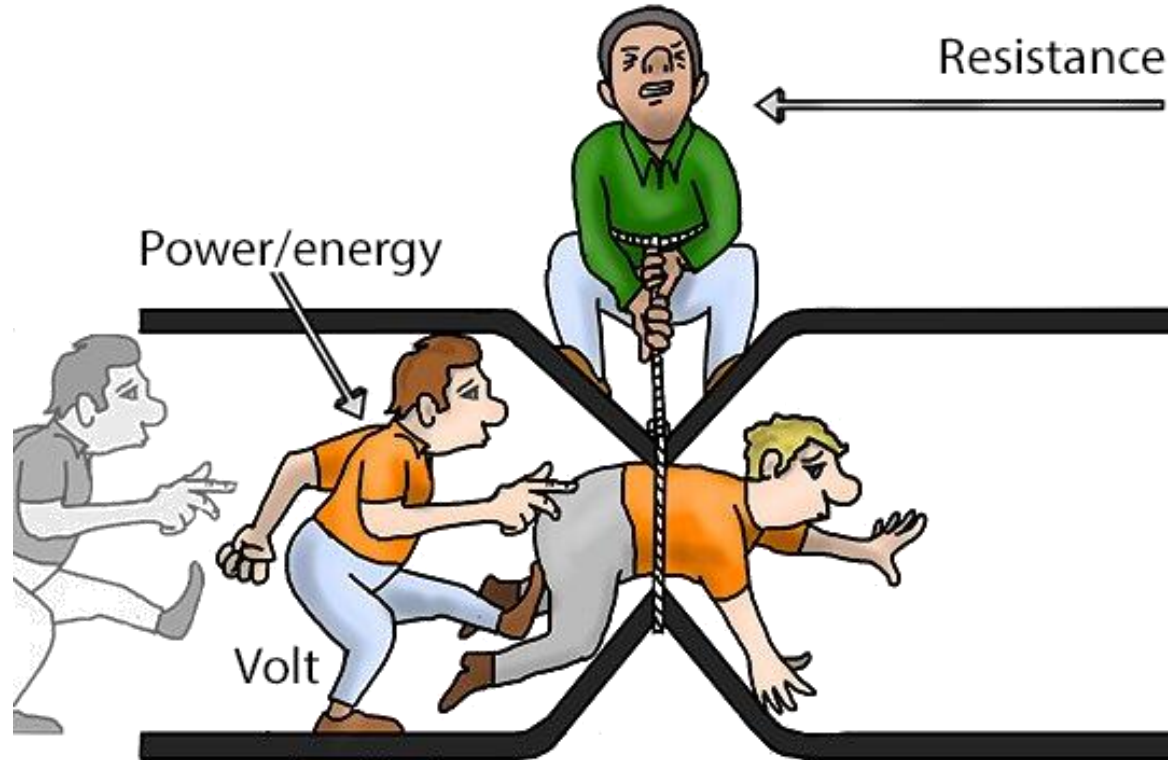


# Physics – Grade 10


## Unit One



## Electricity
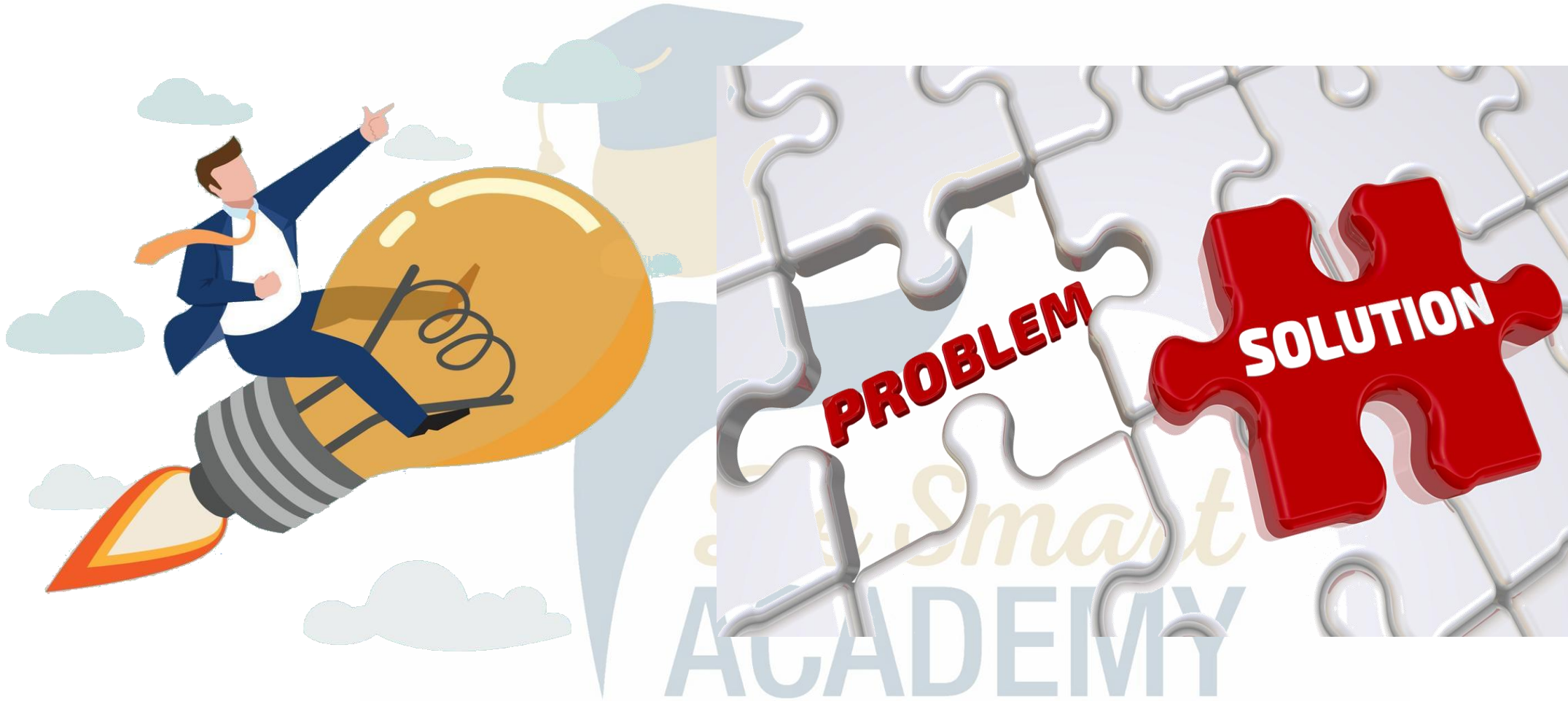
## Chapter 4 – Resistors

Prepared & Presented by: **Mr. Mohamad Seif**



**Think then Solve**


## Exercise 1:



Consider the circuit represented in the adjacent figure.

$G$  is a generator that maintains across its terminals a constant voltage  $V_{PN} = 12\text{V}$ ,  $(A)$  is an ammeter of negligible resistance.  $(R_1)$  is a resistor of resistance  $R_1 = 30\Omega$ ; and  $R_2$  is a resistor of resistance  $R_2$ , and  $(K)$  is a switch.

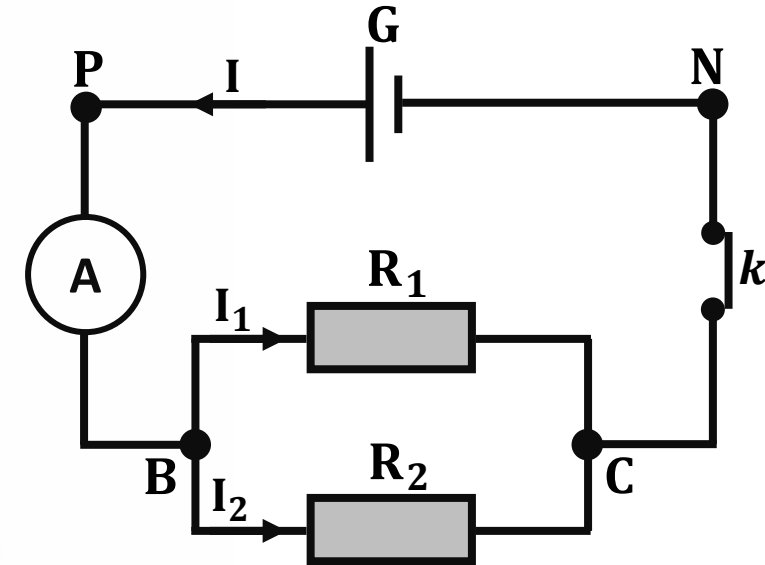When we close  $(K)$ , the ammeter  $(A)$  indicates  $0.6\text{ A}$




## Exercise 1:



### Part A: Determination of the value of $V_{BC}$ :

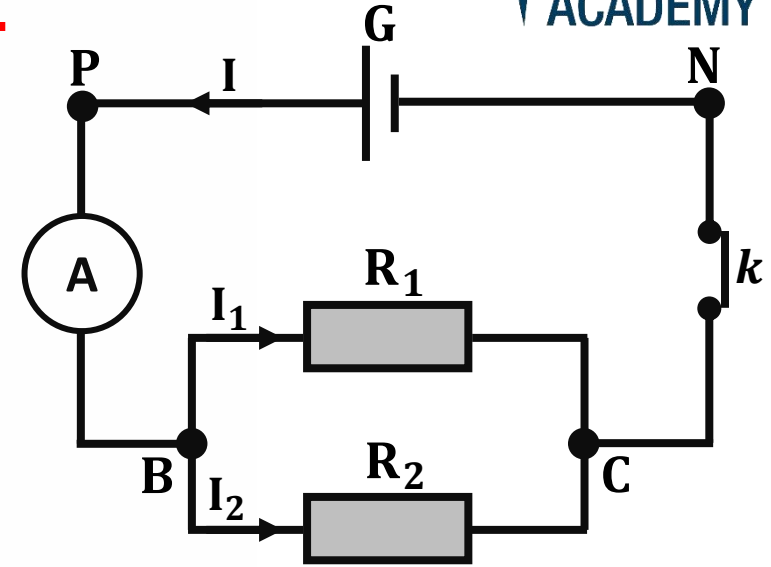1. The voltage across (A) is zero. Why?
2. The voltage across (K) is zero. Why?
3. Prove that the voltage  $V_{BC} = 12V$ .




*Be Smart*  
ACADEMY

## Exercise 1:



$V_{PN} = 12V$  ; ammeter of negligible resistance;  $R_1 = 30\Omega$ ;  $R_2 = ?$ ;  $I = 0.6A$ .

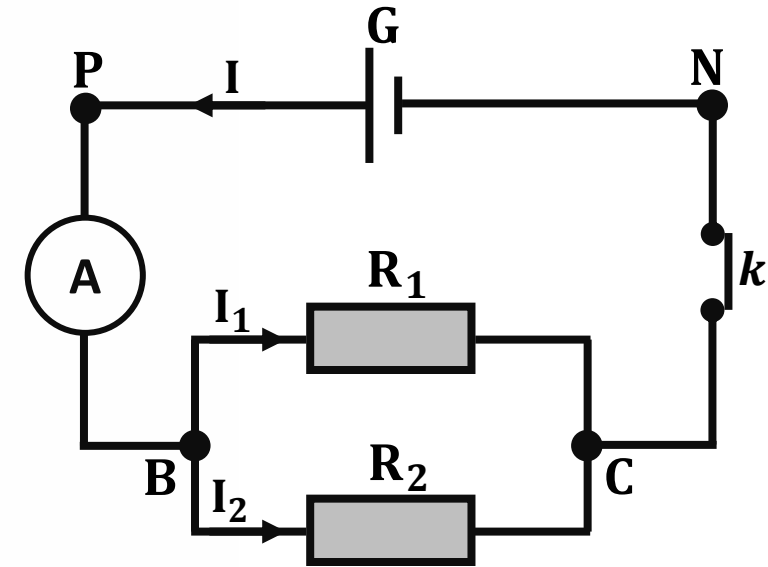1. The voltage across (A) is zero. Why?  
Since the ammeter is of negligible resistance, then the voltage across it is zero.
2. The voltage across (K) is zero. Why?  
Because the switch is closed, then the voltage across it is zero.





## Exercise 1:


$V_{PN} = 12V$  ; ammeter of negligible resistance;  $R_1 = 30\Omega$ ;  
 $R_2 = ?$ ;  $I = 0.6A$ .

3. Prove that the voltage  $V_{BC} = 12V$ .

$$V_{PN} = V_{PB} + V_{BC} + V_{CN}$$

$$12V = 0V + V_{BC} + 0V$$

$$V_{BC} = 12V$$

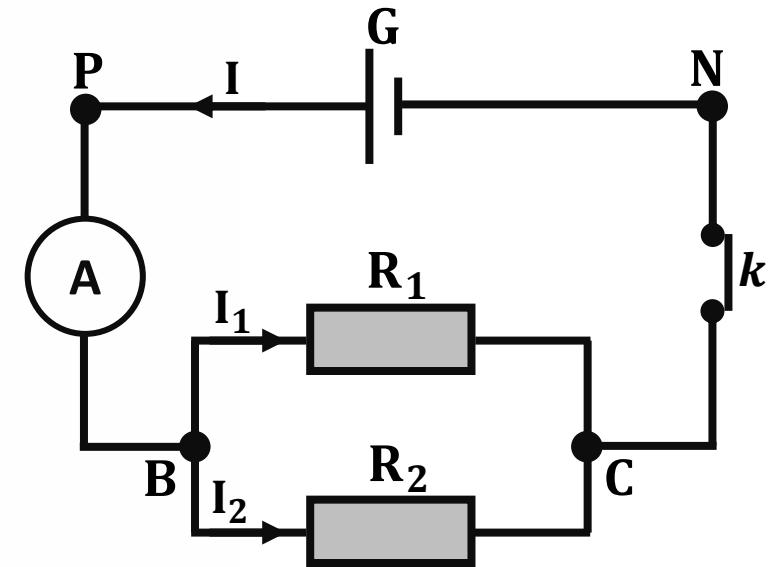


## Exercise 1:



$V_{PN} = 12V$  ; ammeter of negligible resistance;  $R_1 = 30\Omega$ ;  $R_2 = ?$ ;  $I = 0.6A$ .

### Part B: Determination of the value of $R_2$ :

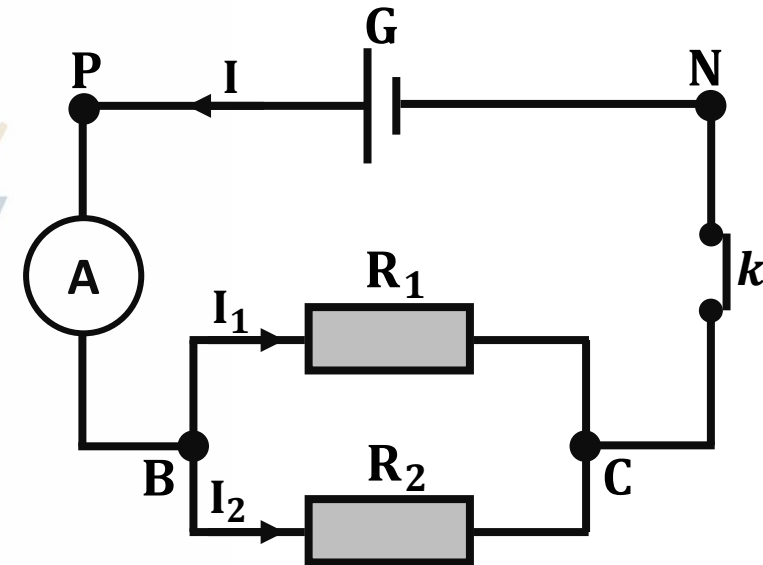1. Determine the value of the current  $I_1$  through  $R_1$
2. Deduce the value of the current  $I_2$  through  $R_2$
3. Show that the value of  $R_2$  is  $60\Omega$ .



## Exercise 1:



$V_{PN} = 12V$  ; ammeter of negligible resistance;  $R_1 = 30\Omega$ ;  $R_2 = ?$ ;  $I = 0.6A$ .

1. Determine the value of the current  $I_1$  through  $R_1$


$R_1$  and  $R_2$  are connected in parallel then:

$$V_{BC} = V_1 = V_2 = 12V$$

Using ohm's law then:  $V_1 = R_1 \times I_1$

$$I_1 = \frac{V_1}{R_1} = \frac{12}{30}$$

$$I_1 = 0.4A$$

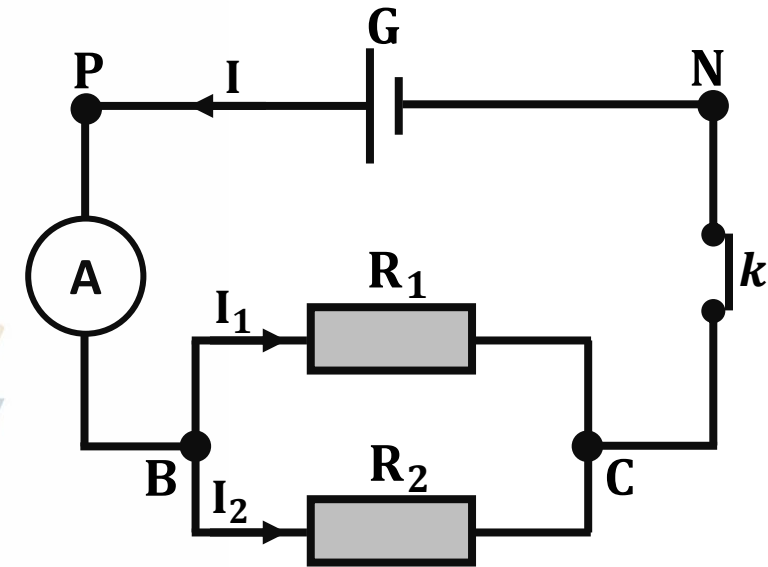



## Exercise 1:



$V_{PN} = 12V$  ; ammeter of negligible resistance;  $R_1 = 30\Omega$ ;  $R_2 = ?$ ;  $I = 0.6A$ .

2. Deduce the value of the current  $I_2$  through  $R_2$


$R_1$  and  $R_2$  are connected in parallel then:

$$I = I_1 + I_2$$

$$I - I_1 = I_2$$

$$0.6A - 0.4A = I_2$$

$$I_2 = 0.2A$$

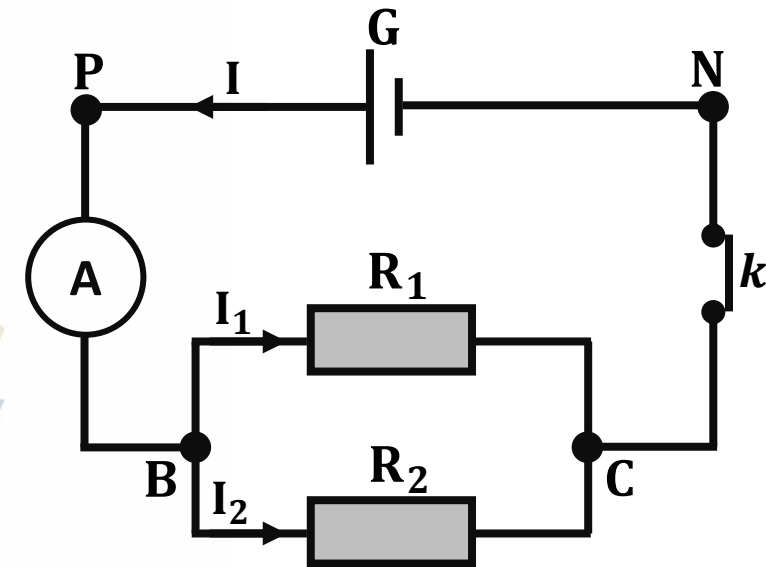

## Exercise 1:




3. Show that the value of  $R_2$  is  $60\Omega$ .

$$V_2 = R_2 \times I_2$$

$$R_2 = \frac{V_2}{I_2} = \frac{12V}{0.2A}$$

$$R_2 = 60\Omega$$

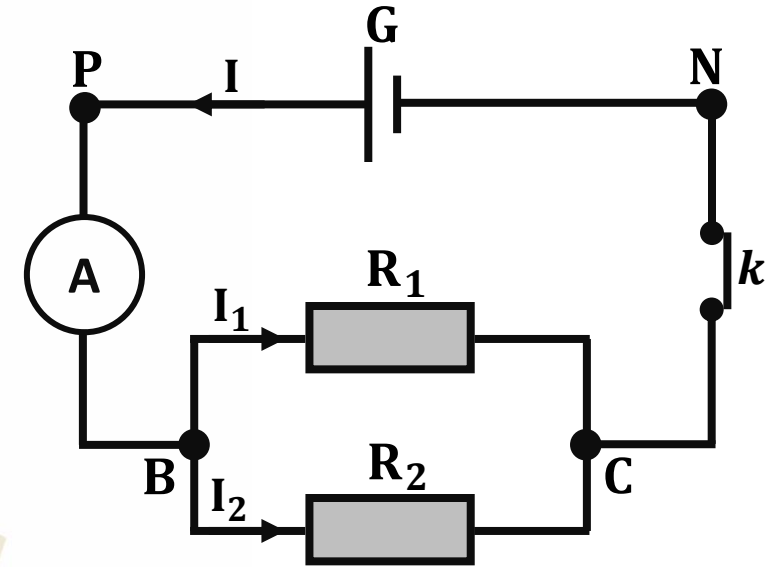

## Exercise 1:



### Part C: Equivalent resistance:

$R_1$  and  $R_2$  can be replaced by a single resistor of resistance ( $R_{eq}$ ).

1. Calculate the equivalent resistance by two methods.
2. An instrument allows a direct measurement of  $R$ . Name this instrument.

*Be Smart*  
ACADEMY



## Exercise 1:



1. Calculate the equivalent resistance by two methods.

First method:

$$V_{PN} = R_{eq} \times I$$

$$R_{eq} = \frac{V_{PN}}{I} = \frac{12V}{0.6}$$

$$R_{eq} = 20\Omega$$

Second method:

$$R_{eq} = \frac{R_1 \times R_2}{R_1 + R_2}$$

$$R_{eq} = \frac{30 \times 60}{30 + 60}$$

$$R_{eq} = \frac{1800}{900}$$

$$R_{eq} = 20\Omega$$

## Exercise 1:



**2. An instrument allows a direct measurement of  $R$ .  
Name this instrument.**


**The instrument that measures directly is ohmmeter**


*Be Smart*  
**ACADEMY**





# The End

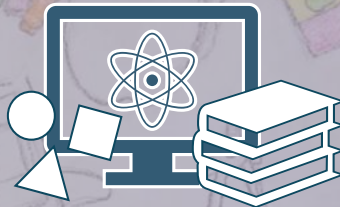

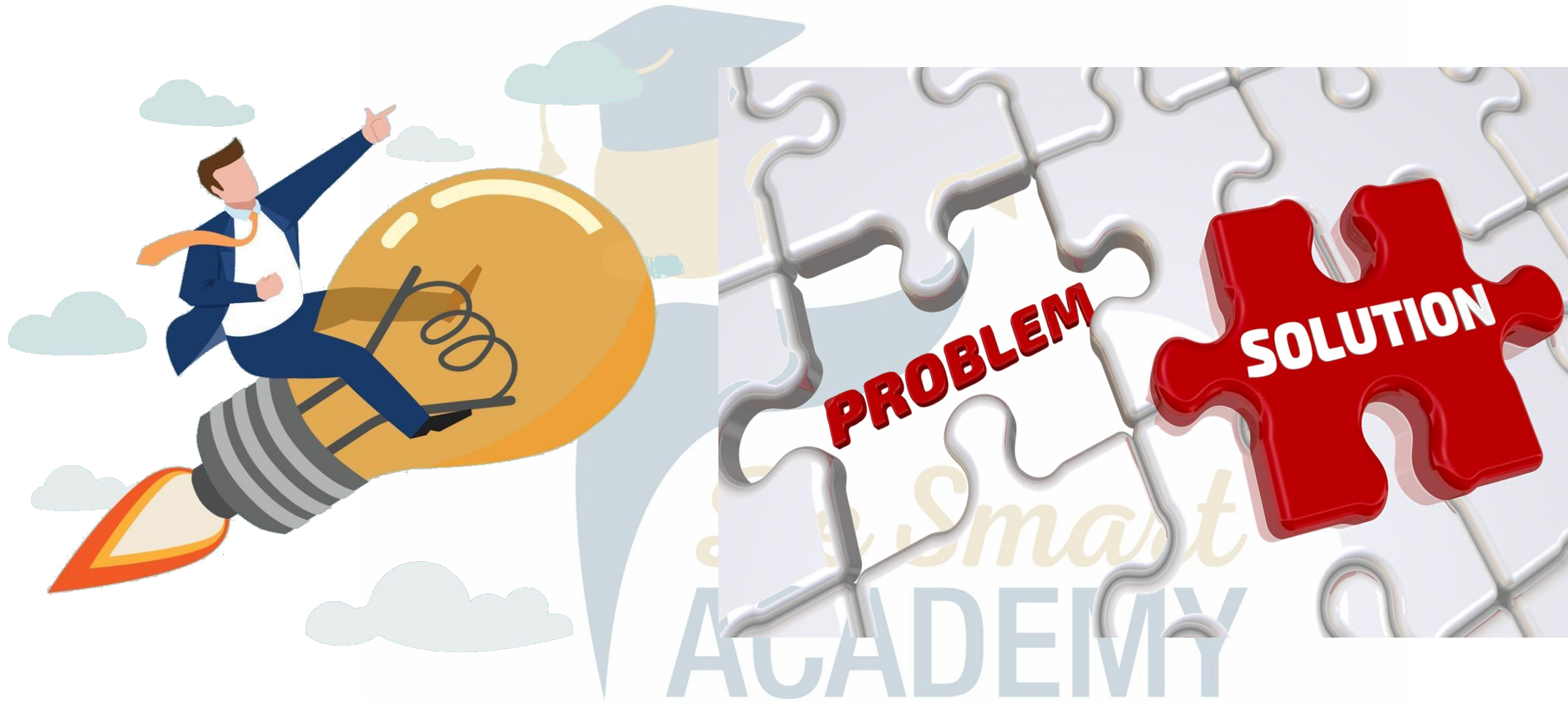

**Think then Solve**




## Exercise 2:



The adjacent circuit diagram shows the combination of four resistors  $R_1 = R_3 = R_4 = 20\Omega$  and  $R_2 = 10\Omega$  are connected to a generator of voltage  $V_{PN} = 24V$ .

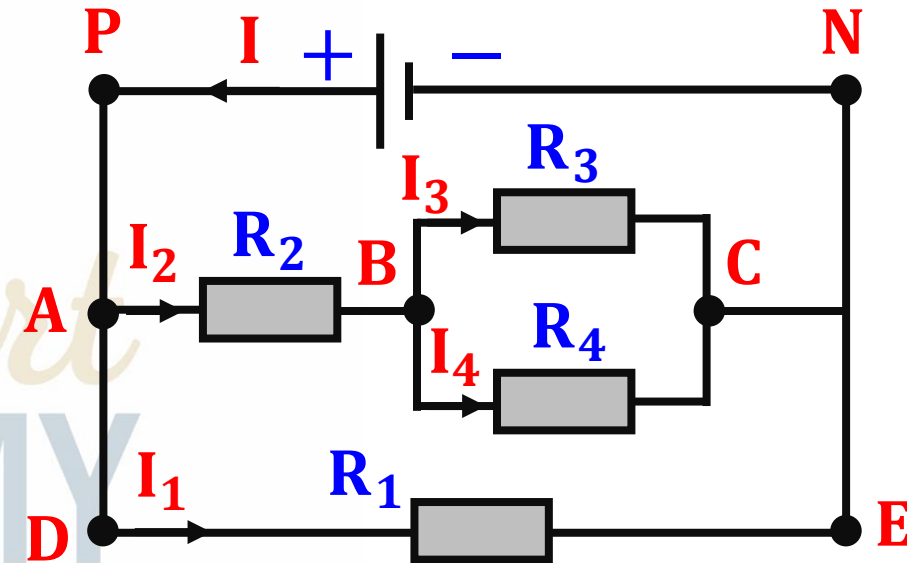1. Show that the resistance of the equivalent resistor to these four resistors is  $R_{eq} = 10\Omega$ .
2. Calculate  $I$  the intensity of the current delivered by the generator.
3. Calculate the intensity of the current traversing each resistor.




## Exercise 2:



4. Determine  $V_{AC}$ ,  $V_{AB}$  and  $V_{BC}$ .

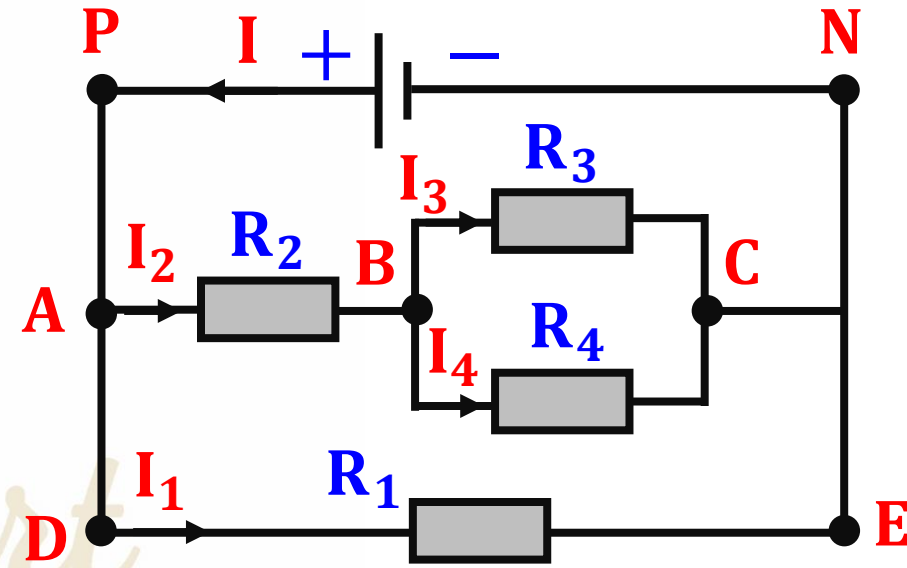5. It is required to replace  $R_2$  by a conducting wire made of a metal of resistivity  $\rho = 4 \times 10^{-5} \Omega m$  and of cross-sectional area  $S = 1 mm^2$ .

Calculate the length of this wire so that the resistance is kept constant.



## Exercise 2:




$V_{PN} = 24V$ ;  $R_1 = R_3 = R_4 = 20\Omega$  and  $R_2 = 10\Omega$ .

1. Show that the resistance of the equivalent resistor to these four resistors is  $R_{eq} = 10\Omega$ .

$R_3$  and  $R_4$  connected in parallel then:

$$R_A = \frac{R_3 \times R_4}{R_3 + R_4} = \frac{20 \times 20}{20 + 20}$$

$$R_A = \frac{400}{40} = 10\Omega$$

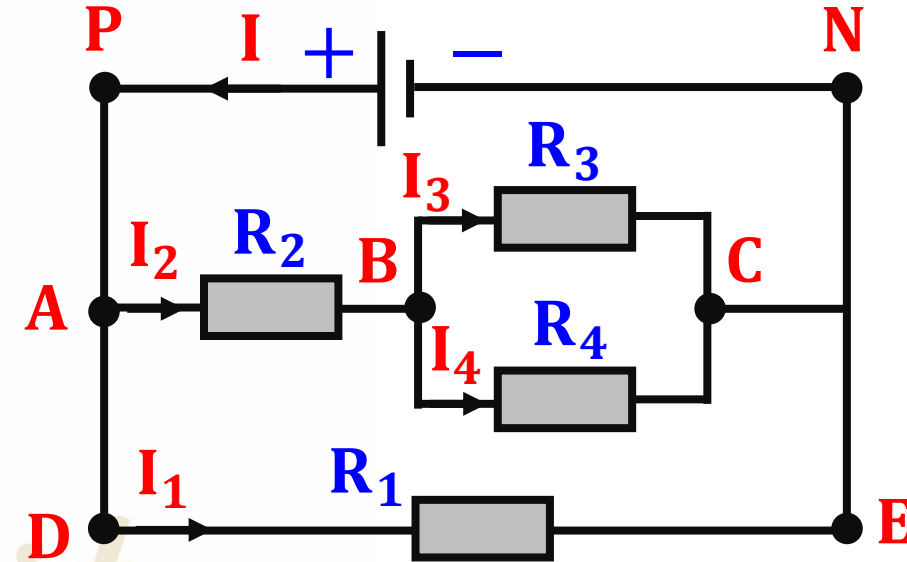





## Exercise 2:

$R_2$  and  $R_A$  connected in series then:

$$R_B = R_A + R_2$$

$$R_B = 10 + 10 = 20\Omega$$

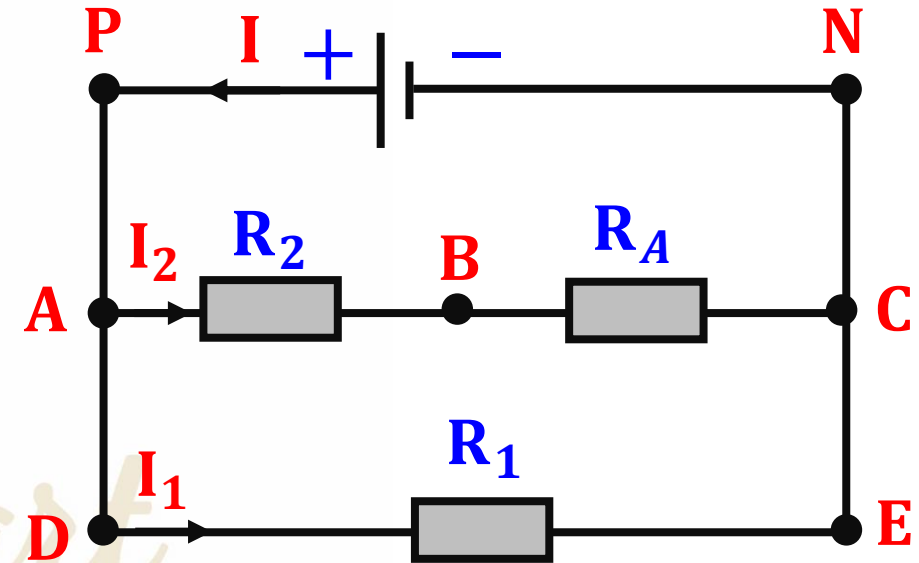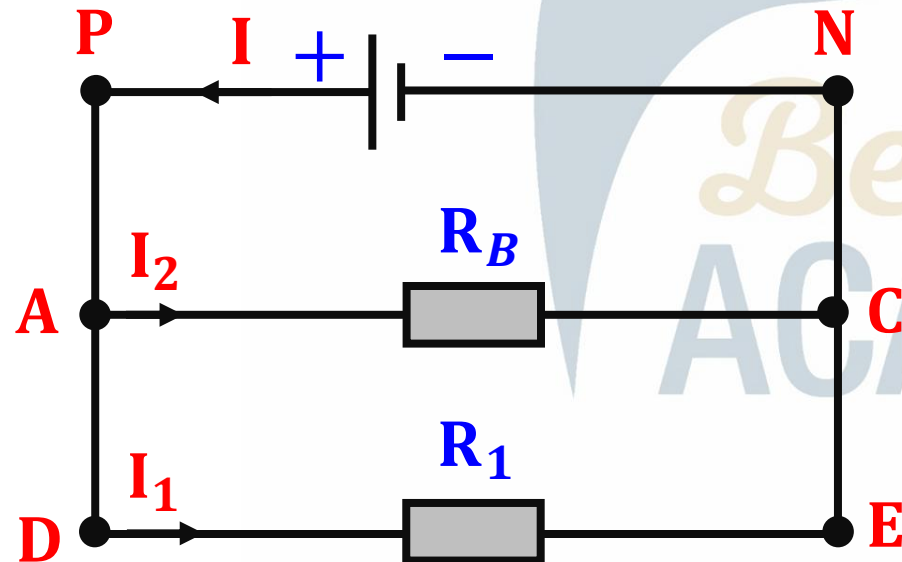



## Exercise 2:



$R_B$  and  $R_1$  connected in parallel:

$$R_{eq} = \frac{R_1 \times R_B}{R_1 + R_B} = \frac{20 \times 20}{20 + 20}$$

$$R_{eq} = \frac{400}{40} = 10\Omega$$

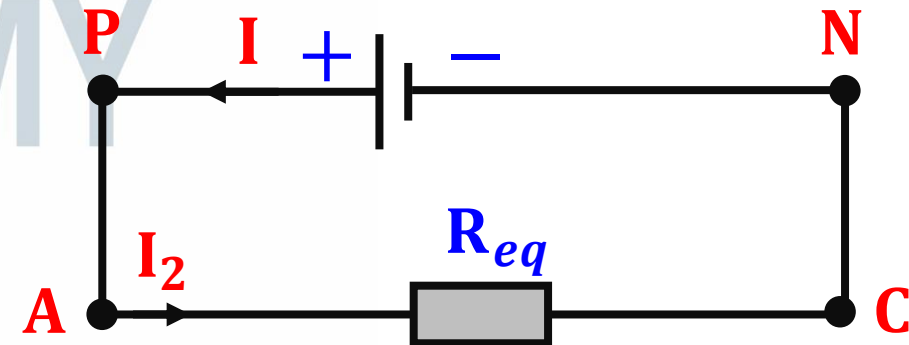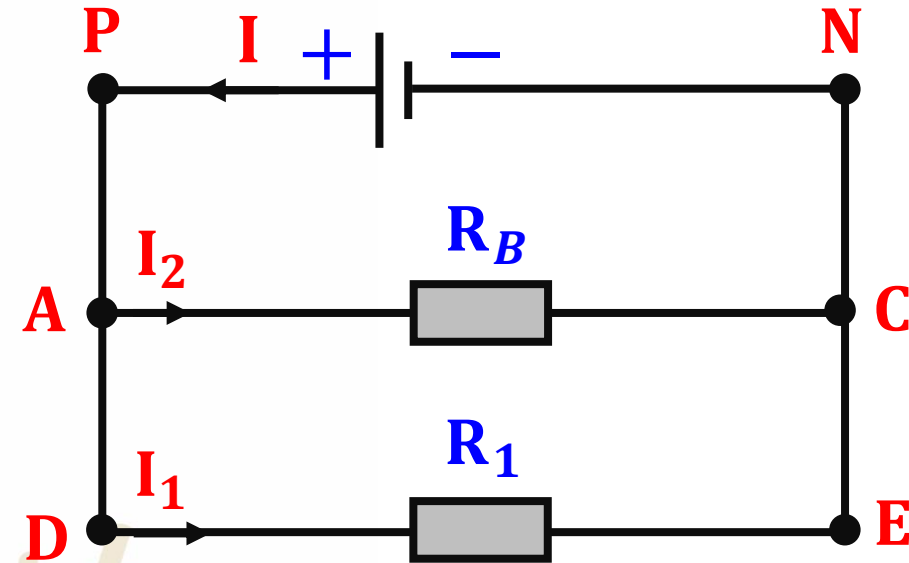

## Exercise 2:




$V_{PN} = 24V$ ;  $R_1 = R_3 = R_4 = 20\Omega$  and  $R_2 = 10\Omega$ .

2. Calculate  $I$  the intensity of the current delivered by the generator.


$$V_{PN} = R_{eq} \times I$$

$$I = \frac{V_{PN}}{R_{eq}}$$

$$I = \frac{24}{10}$$

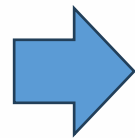

$$I = 2.4A$$

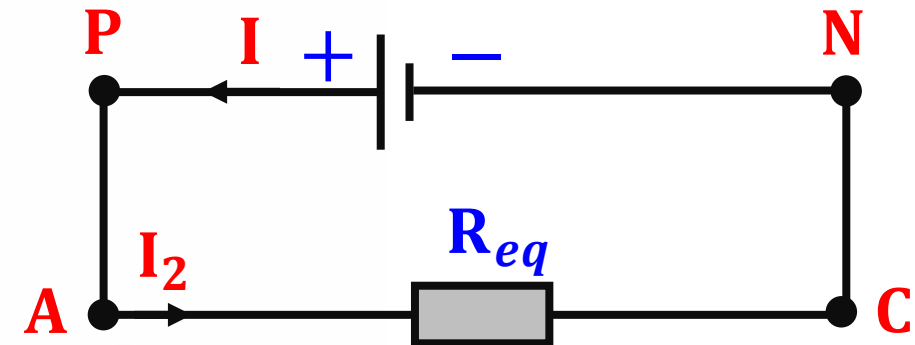

## Exercise 2:



$V_{PN} = 24V$ ;  $R_1 = R_3 = R_4 = 20\Omega$  and  $R_2 = 10\Omega$ .


2. Calculate the intensity of the current traversing each resistor

$R_1$  parallel with the generator then:  
use law of uniqueness of voltage:


$$V_{PN} = V_{DE} = 24V$$

$$U_{DE} = R_1 \times I_1$$
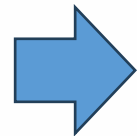
$$I_1 = \frac{U_{DE}}{R_1} = \frac{24}{20}$$



$$I_1 = 1.2A$$

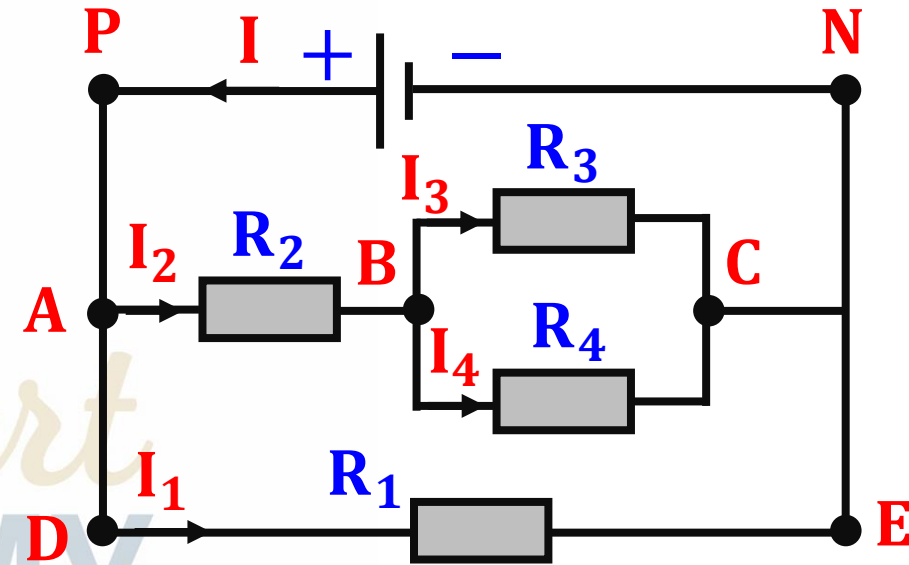

## Exercise 2:



$V_{PN} = 24V$ ;  $R_1 = R_3 = R_4 = 20\Omega$  and  $R_2 = 10\Omega$ .


Using law of addition of current then:

$$I = I_1 + I_2$$

$$2.4A = 1.2A + I_2$$

$$2.4 - 1.2 = I_2$$

$$I_2 = 1.2A$$

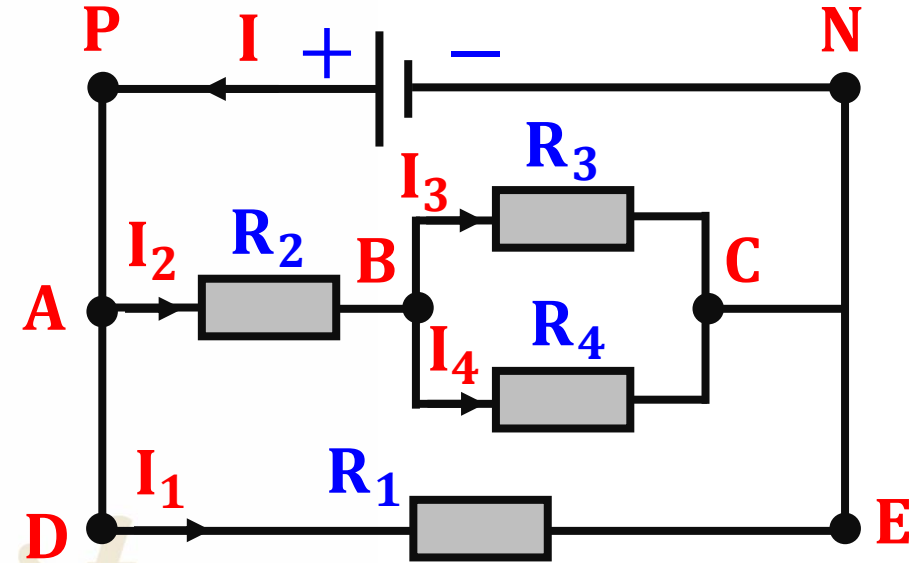



## Exercise 2:



$V_{PN} = 24V$ ;  $R_1 = R_3 = R_4 = 20\Omega$  and  $R_2 = 10\Omega$ .

Since  $R_3$  and  $R_4$  then:  $I_3 = I_4$


$$I_2 = I_3 + I_4$$

$$1.2A = I_3 + I_3$$

$$1.2A = 2I_3$$

$$I_3 = \frac{1.2}{2}$$

$$I_3 = I_4 = 0.6A$$

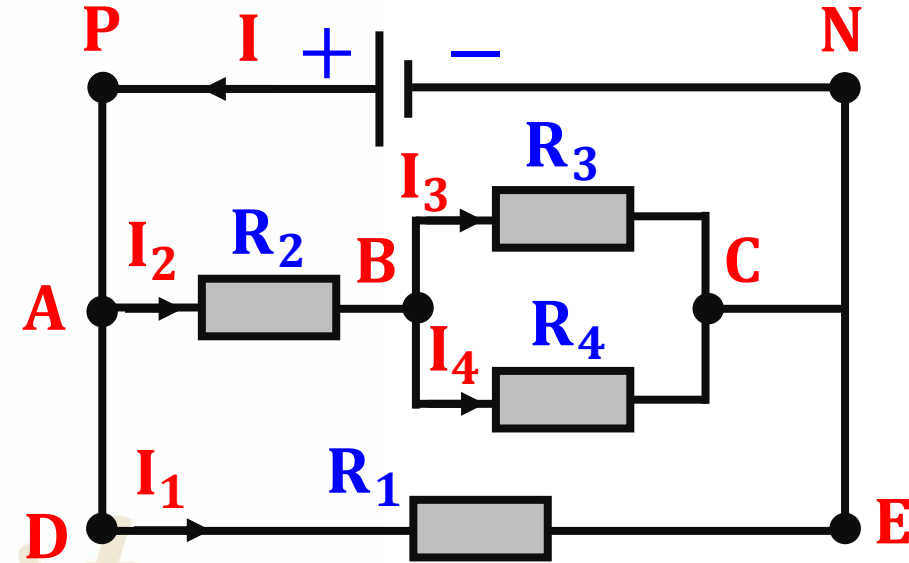

## Exercise 2:




$V_{PN} = 24V$ ;  $R_1 = R_3 = R_4 = 20\Omega$  and  $R_2 = 10\Omega$ ;  $I = 2.4A$ ;  
 $I_1 = 1.2A$ ;  $I_2 = 1.2A$ ;  $I_3 = 0.6A$  and  $I_4 = 0.6A$

4. Determine  $V_{AC}$ ,  $V_{AB}$  and  $V_{BC}$ .

$$V_{AC} = R_B \times I_1$$

$$V_{AC} = 20 \times 1.2$$

$$V_{AC} = 24V$$

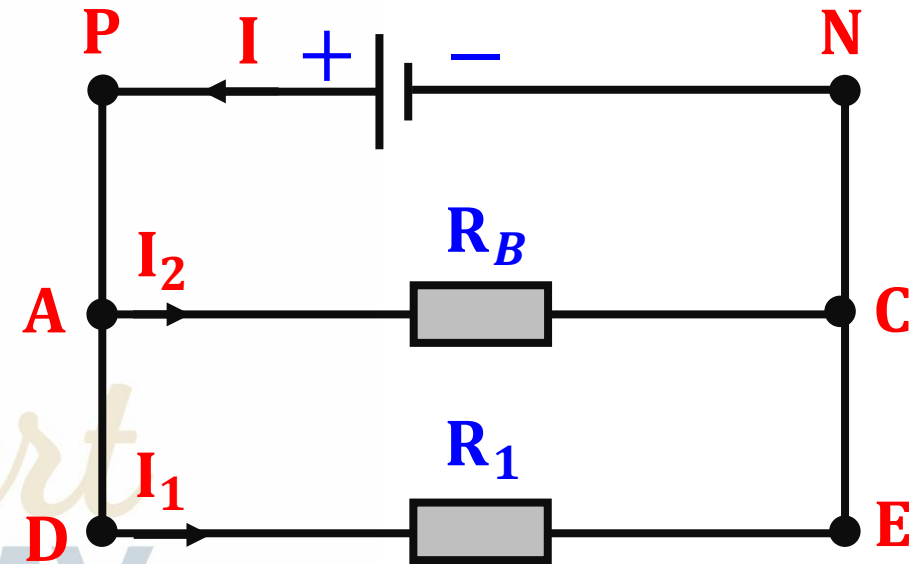

## Exercise 2:




$V_{PN} = 24V$ ;  $R_1 = R_3 = R_4 = 20\Omega$  and  $R_2 = 10\Omega$ ;  $I = 2.4A$ ;  
 $I_1 = 1.2A$ ;  $I_2 = 1.2A$ ;  $I_3 = 0.6A$  and  $I_4 = 0.6A$

4. Determine  $V_{AC}$ ,  $V_{AB}$  and  $V_{BC}$ .

$$V_{AB} = R_2 \times I_2$$

$$V_{AB} = 10 \times 1.2$$

$$V_{AB} = 12V$$

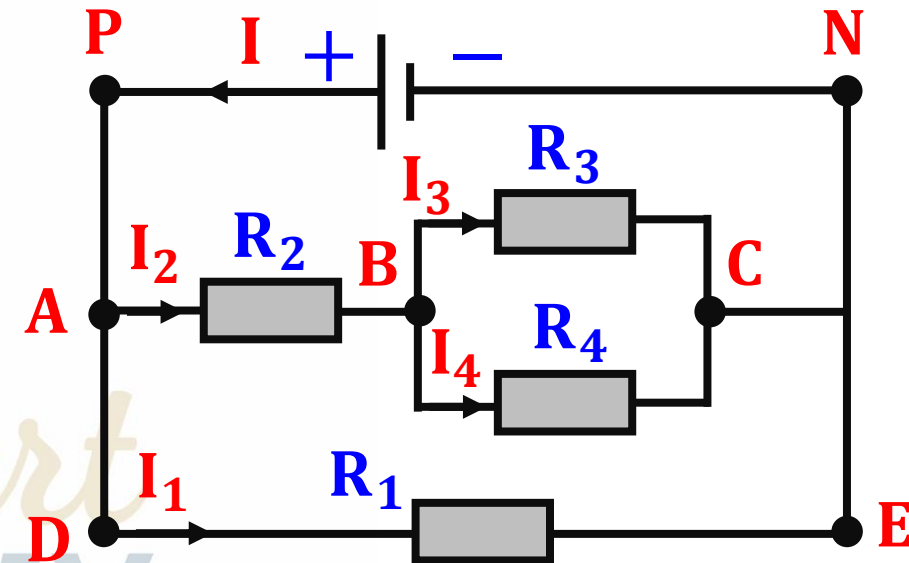

### Exercise 3:



$V_{PN} = 24V$  ;  $R_1 = R_3 = R_4 = 20\Omega$  and  $R_2 = 10\Omega$  ;  $I = 2.4A$ ;  $I_1 = 1.2A$ ;  $I_2 = 1.2A$ ;  $I_3 = 0.6A$  and  $I_4 = 0.6A$

4. Determine  $V_{AC}$ ,  $V_{AB}$  and  $V_{BC}$ .


$$V_{BC} = R_3 \times I_3 = 20 \times 0.6$$

$$V_{BC} = 12V$$

Second method:

$$V_{AC} = V_{AB} + V_{BC}$$

$$24V = 12V + V_{BC}$$

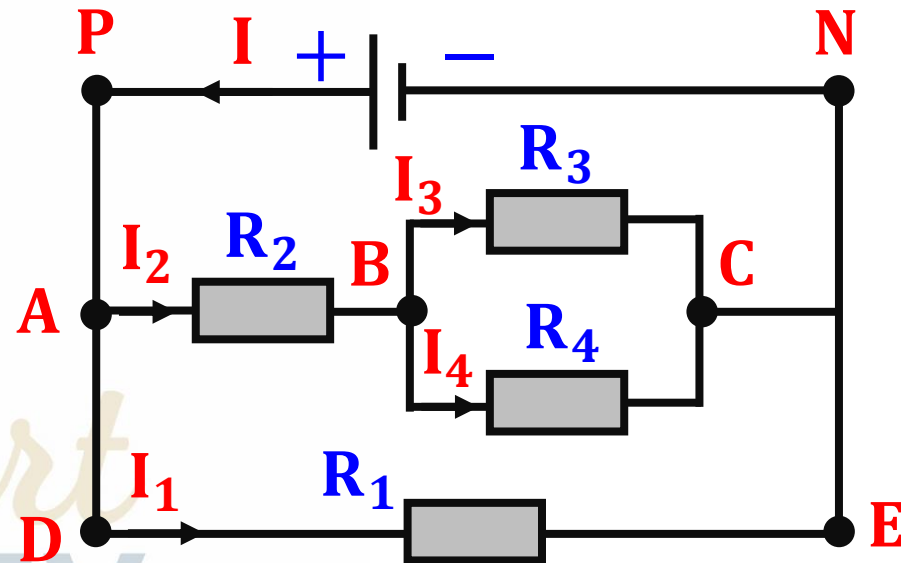

$$V_{BC} = 12V$$

## Exercise 2:



4. It is required to replace  $R_2$  by a conducting wire made of a metal of resistivity  $\rho = 4 \times 10^{-5} \Omega m$  and of cross-sectional area  $S = 1 mm^2$ . Calculate the length of this wire so that the resistance is kept constant.

$$R_2 = \frac{\rho \times L}{S}$$

$$\frac{R_2}{1} = \frac{\rho \times L}{S}$$

$$R_2 \times S = \rho \times L$$


$$L = \frac{R_2 \times S}{\rho}$$


$$L = \frac{10 \times 1 \times 10^{-6}}{4 \times 10^{-4}}$$

$$L = 0.025m = 2.5cm$$



# The End

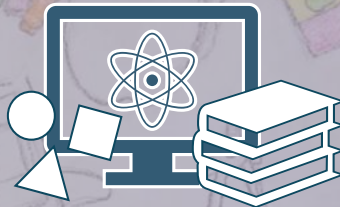

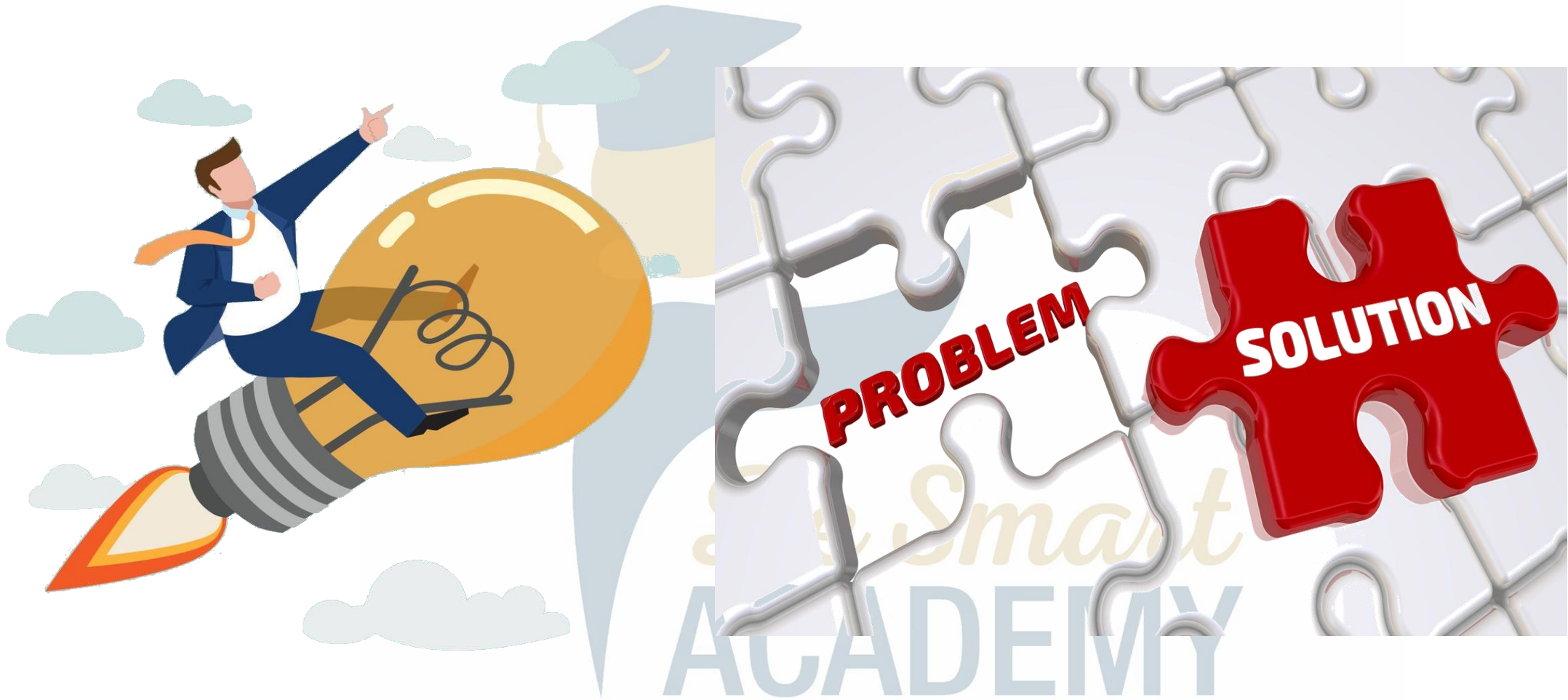

**Think then Solve**




### Exercise 3



Consider the electric circuit that consists of a dry cell of voltage  $V_{PN} = 12V$  and three resistors  $R_1 = 1.6\Omega$ ,  $R_2 = 4\Omega$  and  $R_3 = 6\Omega$  as shown in figure 1.

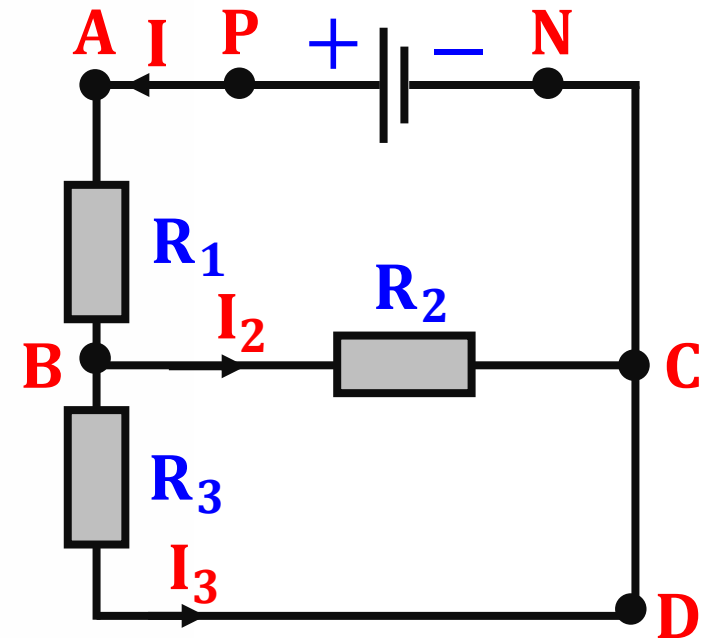
1. Calculate the equivalent resistance of the circuit.
2. Calculate the main current  $I$ .
3. Calculate the voltage  $V_{AB}$  across  $R_1$ .
4. Determine  $V_{BC}$  then deduce the voltage  $V_{BD}$  across  $R_3$ .



### Exercise 3



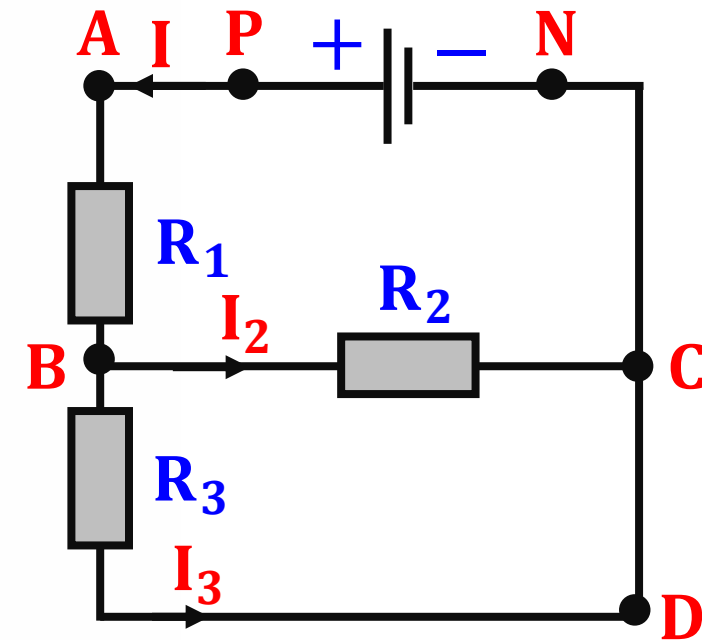5. Calculate the current  $I_2$  traversing  $R_2$  and the current  $I_3$  traversing  $R_3$
6. Calculate the power consumed by  $R_1$ . Deduce the energy dissipated in 1 minute.
7. In what form does this energy appear?



## Exercise 3



$V_{PN} = 12V$ ;  $R_1 = 1.6\Omega$ ;  $R_2 = 4\Omega$  and  $R_3 = 6\Omega$

1. Calculate the equivalent resistance of the circuit.

$R_2$  and  $R_3$  are connected in parallel then:


$$R_A = \frac{R_2 \times R_3}{R_2 + R_3} = \frac{4 \times 6}{4 + 6} = \frac{24}{10} = 2.4\Omega$$

$R_A$  and  $R_1$  are connected in series then:

$$R_{eq} = R_1 + R_A$$

$$R_{eq} = 1.6 + 2.4$$

$$R_{eq} = 4\Omega$$

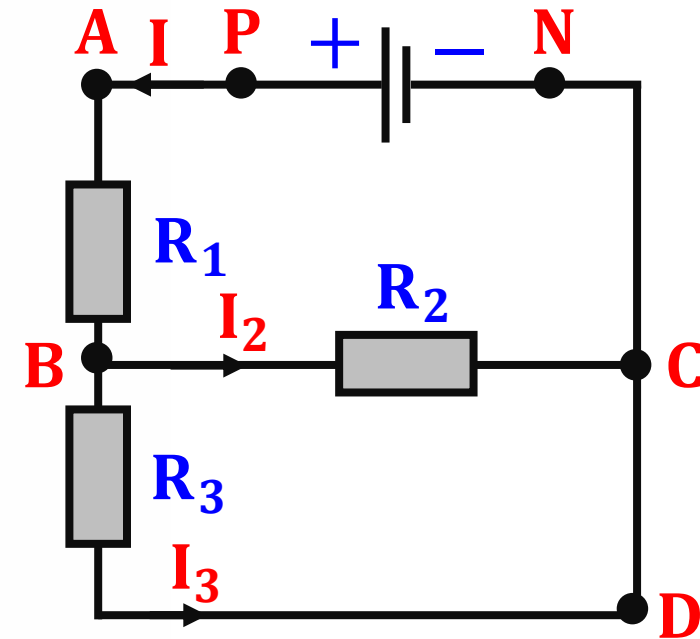

## Exercise 3




$V_{PN} = 12V$ ;  $R_1 = 1.6\Omega$ ;  $R_2 = 4\Omega$  and  $R_3 = 6\Omega$

2. Calculate the main current  $I$ .

$$U_{PN} = R_{eq}I$$

$$I = \frac{U_{PN}}{R_{eq}} = \frac{12V}{4}$$

$$I = 3A$$

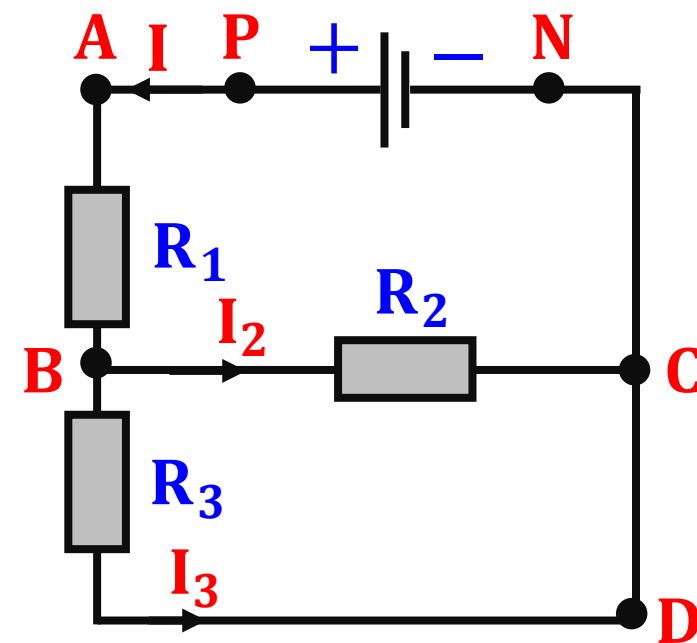



## Exercise 3




$V_{PN} = 12V$ ;  $R_1 = 1.6\Omega$ ;  $R_2 = 4\Omega$  and  $R_3 = 6\Omega$

3. Calculate the voltage  $V_{AB}$  across  $R_1$ .

$$V_{AB} = R_1 I$$

$$V_{AB} = 1.6 \times 3$$

$$V_{AB} = 4.8V$$

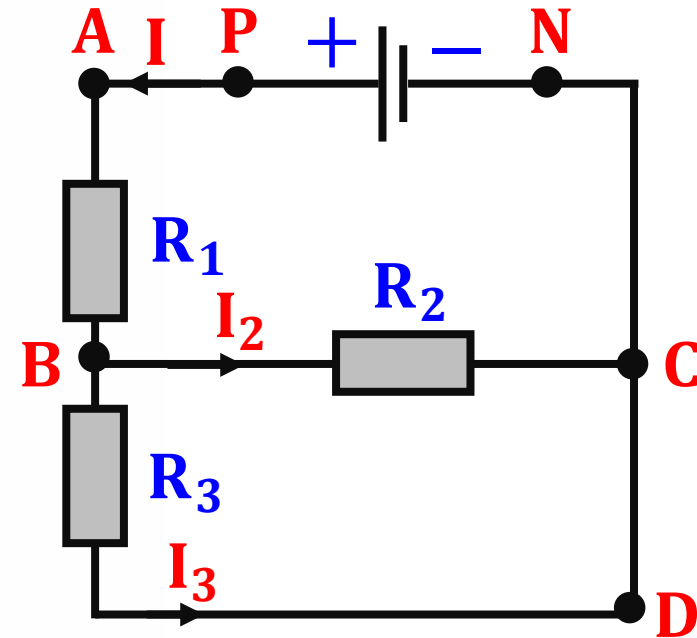

## Exercise 3



$V_{PN} = 12V$ ;  $R_1 = 1.6\Omega$ ;  $R_2 = 4\Omega$  and  $R_3 = 6\Omega$

4. Determine  $V_{BC}$  then deduce the voltage across  $R_3$ .


$$V_{PN} = V_{AB} + V_{BC} + V_{CN}$$

$$12V = 4.8V + V_{BC} + 0V$$

$$V_{BC} = 7.2V$$

Since  $R_2$  and  $R_3$  are in parallel:

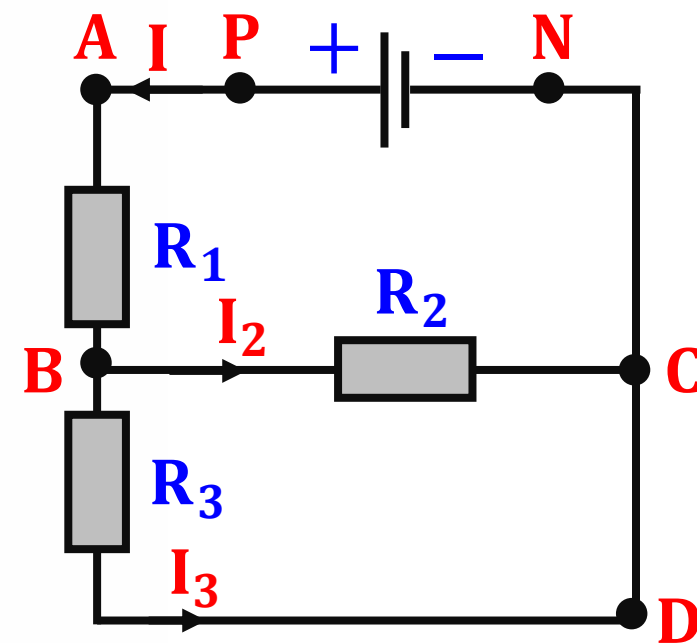$V_{BC} = V_{BD} = 7.2V$  Law of uniqueness of voltage in parallel



## Exercise 3



$$V_{PN} = 12V; R_1 = 1.6\Omega; R_2 = 4\Omega \text{ and } R_3 = 6\Omega$$

5. Calculate the current  $I_2$  traversing  $R_2$  and the current  $I_3$  traversing  $R_3$ .


$$V_{BC} = R_2 \times I_2 \Rightarrow I_1 = \frac{V_{BC}}{R_2} = \frac{7.2V}{4} = 1.8A$$

At junction point B:

$$I = I_1 + I_2 \Rightarrow I - I_1 = I_2$$

$$3A - 1.8A = I_2$$

$$I_2 = 1.2A$$

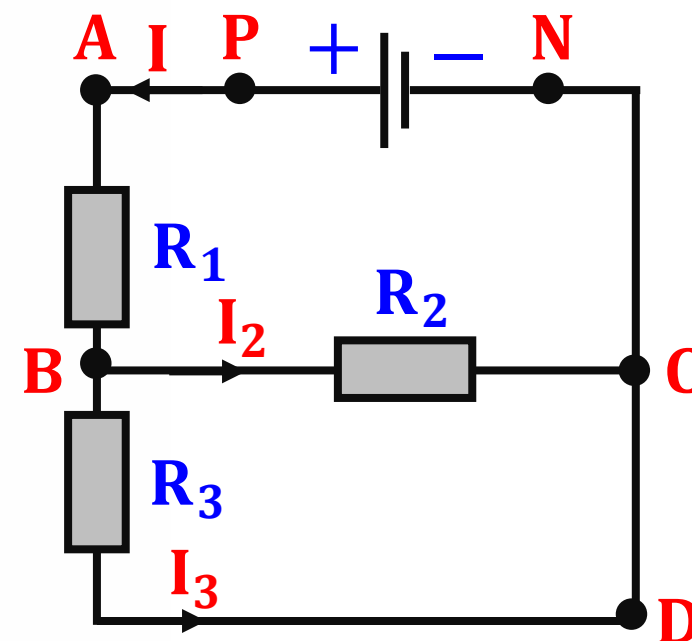

## Exercise 3



$$V_{PN} = 12V; R_1 = 1.6\Omega; R_2 = 4\Omega \text{ and } R_3 = 6\Omega$$

6. Calculate the power consumed by  $R_1$ . Deduce the energy in joules, dissipated in 1 minute.

The consumed power is:

$$P = V_{AB} \times I$$

$$P = 4.8 \times 3$$

$$P = 14.4W$$

The dissipated energy:

$$E = P \times t$$

$$E = 14.4 \times (1 \times 60)$$

$$E = 864J$$

## Exercise 3



**7. In what form does this energy appear?**

**The energy appears by joules effect as a heat**





# The End

