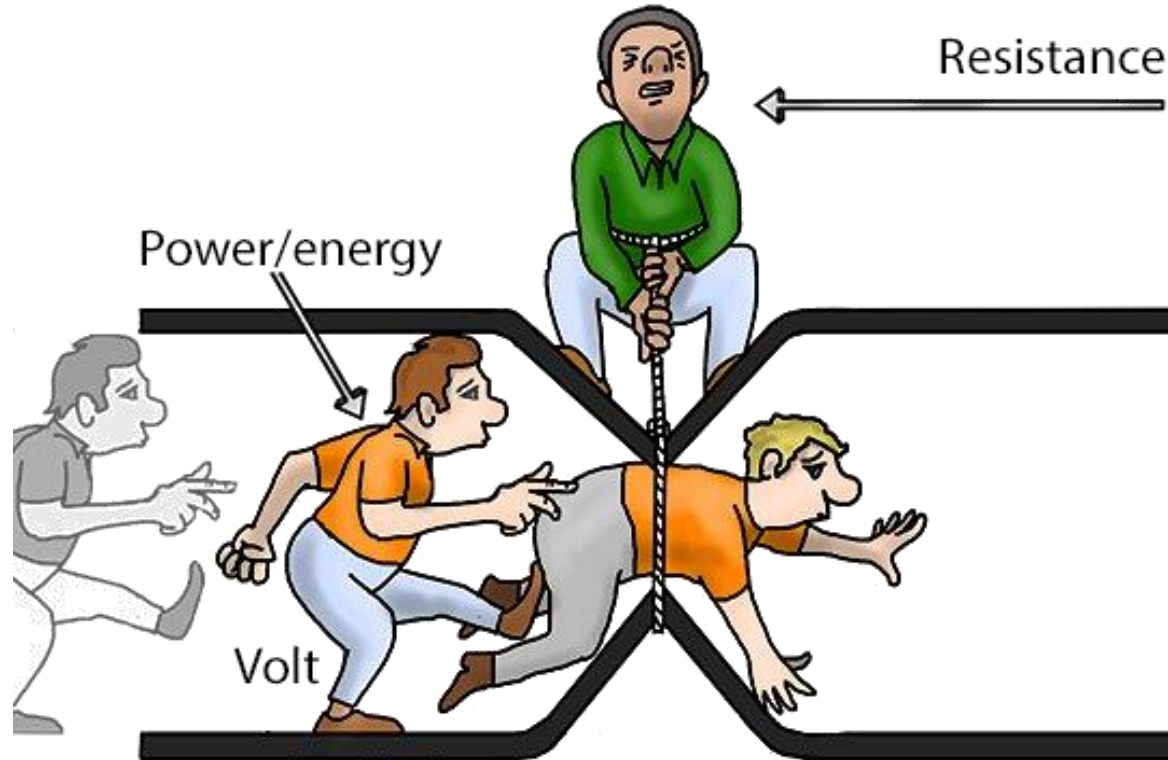


Physics – Grade 10


Unit One



Electricity


Chapter 4 – Resistors

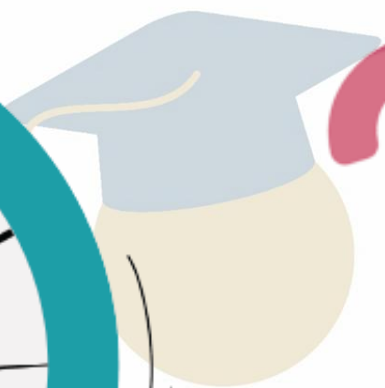Prepared & Presented by: **Mr. Mohamad Seif**




Be Smart
ACADEMY

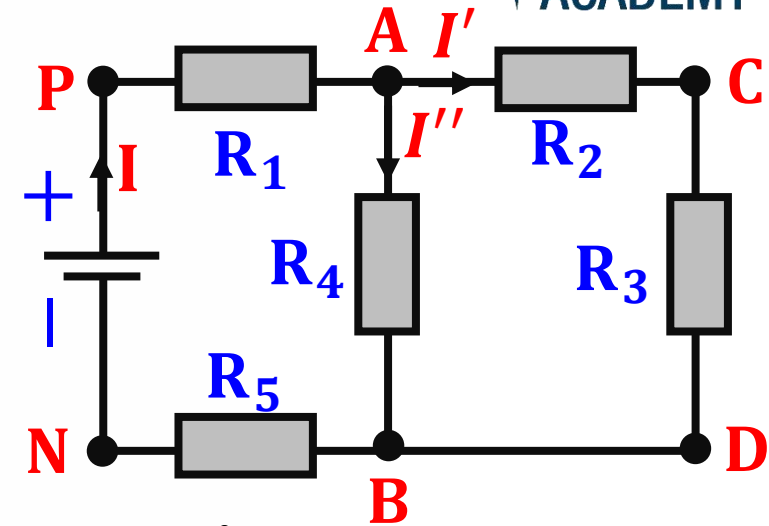Five resistors of resistances $R_1 = 4\Omega$; $R_2 = 5\Omega$; $R_3 = 10\Omega$; $R_4 = 3\Omega$; $R_5 = 2\Omega$ respectively, are connected to an ideal battery of voltage $V_{PN} = 12V$ as shown in the adjacent figure.



1. Determine the resistance of the equivalent resistor.
2. Show that the main current sent by the battery is $I = 0.15A$.
3. Determine the voltages V_{PA} ; V_{AB} and V_{BN} .

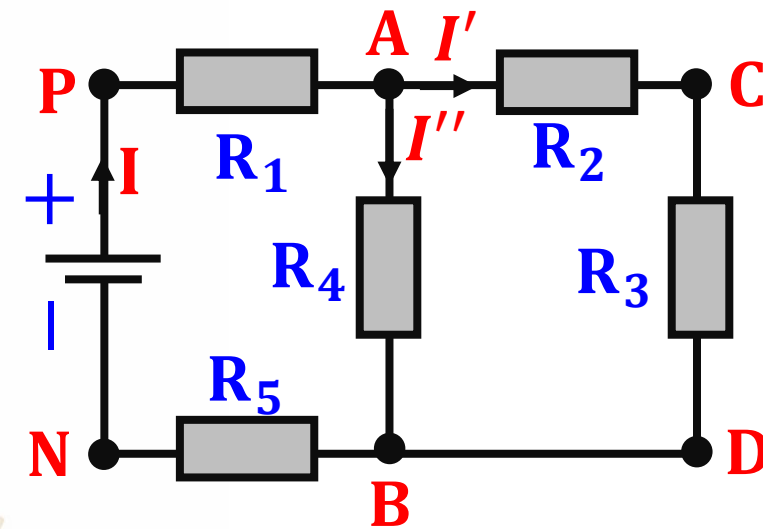4. Deduce the dissipated power P_{PA} ; P_{AB} and P_{BN} .
5. Verify that the total power dissipated by this circuit is equal to the power delivered by the battery.
6. Calculate the intensity of currents I' and I'' .
7. Determine the electric energy supplied by the battery during 1 min.



Quiz

physics

20 min





$V_{PN} = 12V$; $R_1 = 4\Omega$; $R_2 = 5\Omega$; $R_3 = 10\Omega$; $R_4 = 3\Omega$; $R_5 = 2\Omega$.

1. Determine the resistance of the equivalent resistor

R_2 and R_3 are in series:

$$R_A = R_2 + R_3$$

$$R_A = 5 + 10 = 15\Omega$$

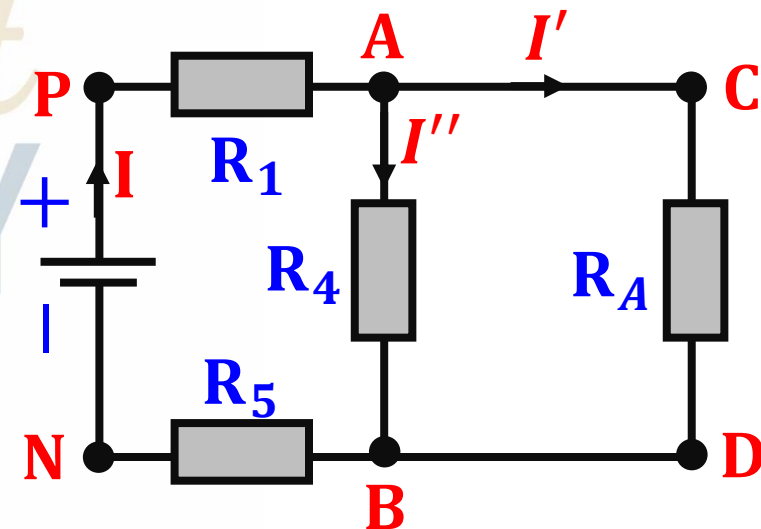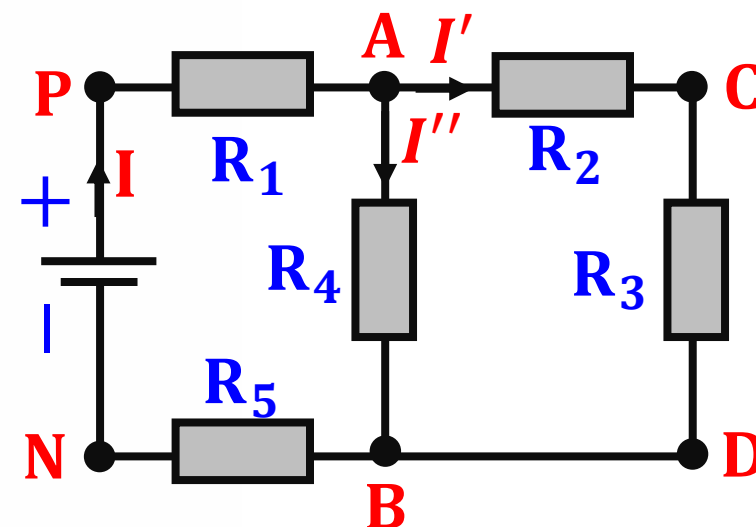

Quiz

physics



20 min



$$V_{PN} = 12V; R_1 = 4\Omega; R_2 = 5\Omega; R_3 = 10\Omega; R_4 = 3\Omega; R_5 = 2\Omega.$$

R_A and R_4 are in parallel:
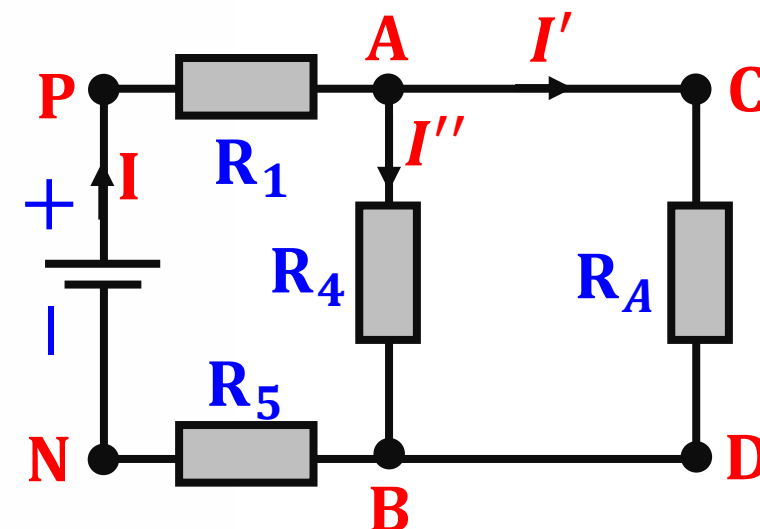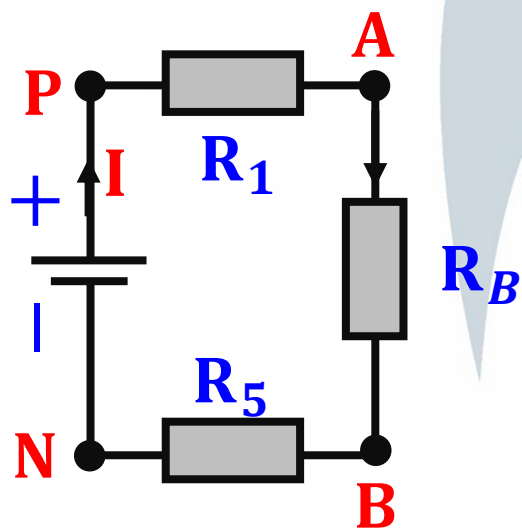
$$R_B = \frac{R_A \times R_4}{R_A + R_4} = \frac{15 \times 3}{15 + 3} = 2.5\Omega$$



Quiz

physics

20 min




$V_{PN} = 12V$; $R_1 = 4\Omega$; $R_2 = 5\Omega$; $R_3 = 10\Omega$; $R_4 = 3\Omega$; $R_5 = 2\Omega$.

R_1 ; R_B and R_5 are in series:

$$R_{eq} = R_1 + R_B + R_5$$

$$R_{eq} = 4 + 2.5 + 2$$

$$R_{eq} = 8.5\Omega$$

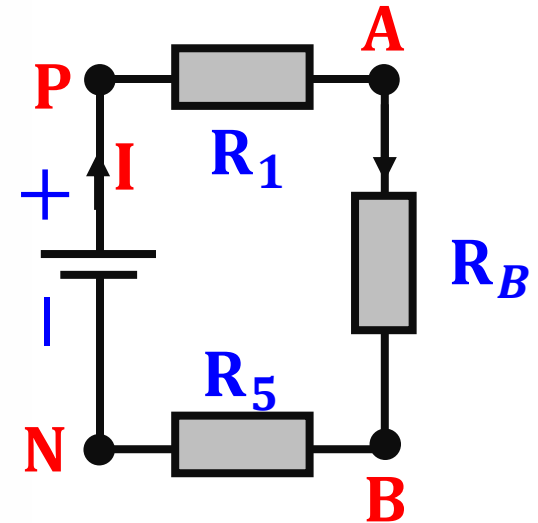

Quiz

physics

20 min




$$V_{PN} = 12V; R_1 = 4\Omega; R_2 = 5\Omega; R_3 = 10\Omega; R_4 = 3\Omega; R_5 = 2\Omega.$$

2. Deduce the intensity of the current sent by the battery.

$$V_{PN} = R_{eq} \times I$$

$$I = \frac{V_{PN}}{R_{eq}} = \frac{12}{8.5}$$

$$I = 141A$$

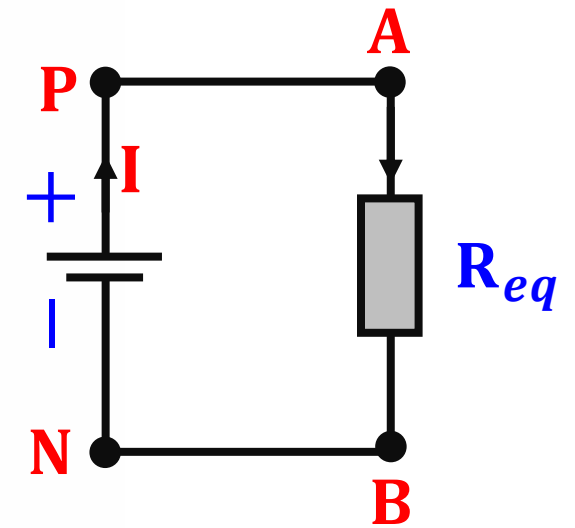

$V_{PN} = 12V$; $R_1 = 4\Omega$; $R_2 = 5\Omega$; $R_3 = 10\Omega$; $R_4 = 3\Omega$; $R_5 = 2\Omega$.

3. Determine the voltages V_{PA} ; V_{AB} and V_{BN}

$$V_{PA} = R_1 \times I$$

$$V_{PA} = 4 \times 1.41$$

$$V_{PA} = 5.64V$$

$$V_{AB} = R_B \times I$$


$$V_{AB} = 2 \times 1.41$$

$$V_{AB} = 2.82V$$

$$V_{BN} = R_5 \times I$$

$$V_{BN} = 2 \times 1.41$$

$$V_{BN} = 2.82V$$

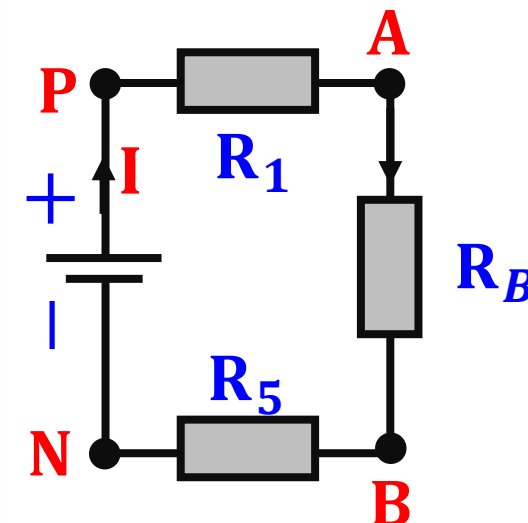

Quiz

physics

20 min



$V_{PN} = 12V$; $R_1 = 4\Omega$; $R_2 = 5\Omega$; $R_3 = 10\Omega$; $R_4 = 3\Omega$; $R_5 = 2\Omega$.

4. Deduce the dissipated power P_{PA} ; P_{AB} and P_{BN} .

$$P_{PA} = V_{PA} \times I$$

$$P_{PA} = 5.64V \times 1.41$$

$$P_{PA} = 7.95W$$

$$P_{AB} = V_{AB} \times I$$


$$P_{AB} = 2.82V \times 1.41$$

$$P_{AB} = 3.97W$$

$$P_{BN} = V_{BN} \times I$$

$$P_{BN} = 2.82 \times 1.41$$

$$P_{BN} = 3.97W$$

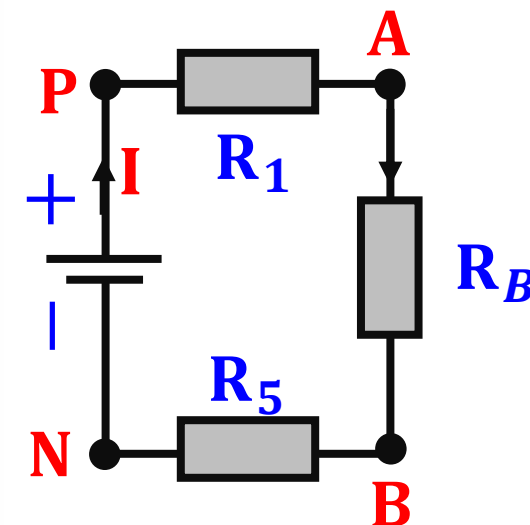

Quiz

physics

20 min



$$V_{PN} = 12V; R_1 = 4\Omega; R_2 = 5\Omega; R_3 = 10\Omega; R_4 = 3\Omega; R_5 = 2\Omega.$$

5. Verify that the total power dissipated by this circuit is equal to the power delivered by the battery.

$$P_{PN} = V_{PN} \times I$$

$$P_{PN} = R_{eq} \times I^2$$

$$P_{PN} = 12V \times 1.41$$

$$P_{diss} = 8.5 \times (1.41)^2$$

$$P_{PN} = 16.92W$$

$$P_{PN} = P_{PA} + P_{AB} + P_{BN}$$

$$P_{diss} = 16.92W$$

$$P_{PN} = 7.95 + 3.97 + 3.97$$

$$P_{PN} = 16.92W$$

$V_{PN} = 12V$; $R_1 = 4\Omega$; $R_2 = 5\Omega$; $R_3 = 10\Omega$; $R_4 = 3\Omega$; $R_5 = 2\Omega$.

6. Calculate the intensity of currents I' and I'' .


$$V_{AB} = R_4 \times I'' \Rightarrow I'' = \frac{V_{AB}}{R_4} = \frac{2.82V}{3}$$

$$I'' = 0.94A$$

Law of addition of current (junction point A)

$$I = I' + I'' \Rightarrow I - I'' = I' \Rightarrow 1.42 - 0.94 = I'$$

$$I' = 0.48A$$

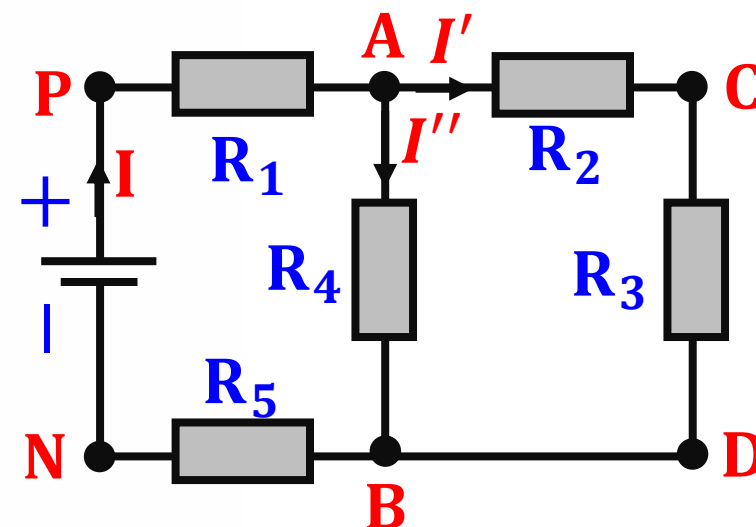

Quiz

physics

20 min




$V_{PN} = 12V$; $R_1 = 4\Omega$; $R_2 = 5\Omega$; $R_3 = 10\Omega$; $R_4 = 3\Omega$; $R_5 = 2\Omega$.

7. Determine the electric energy supplied by the battery during 1 min.

$$E = P_{PN} \times t$$

$$E = 16.92 \times (1 \times 60)$$

$$E = 1015.2J$$

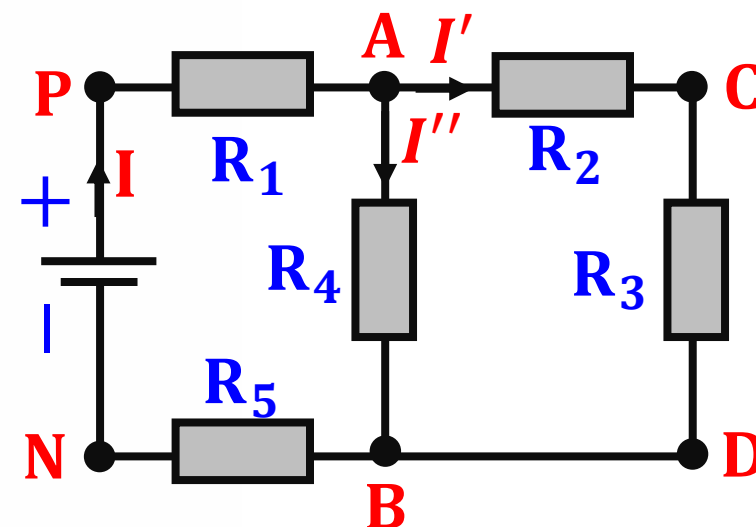

The End

