

Physics – Grade 10

Unit One – Electricity



Chapter 5 Generator and Receiver

Prepared & Presented by: **Mr. Mohamad Seif**



OBJECTIVES

1 Define a generator

2 Identify the characteristics of a generator:

Define a Generator



What is a generator?

A Generator: is an electric device that **converts** forms of **energy** into **electric energy**.



Define a Generator




Examples about generators:

Name of Generator	Convert energy from to +		
Thermal power stations	Chemical energy	Electric energy	thermal energy
Dry cell	Chemical energy	Electric energy	thermal energy
Solar cell	Radiant energy	Electric energy	thermal energy

Define a Generator



The symbol of a generator is:

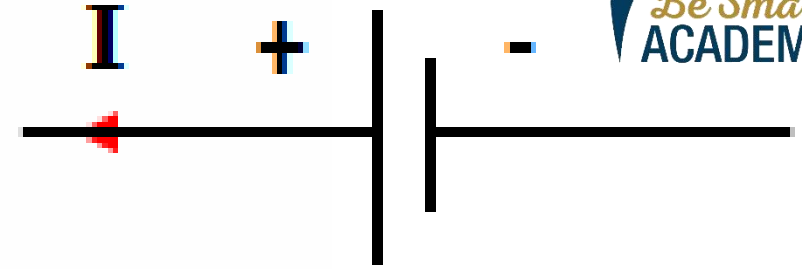

The current **enters** through the **negative (-)** pole and **leaves** through the **positive (+)** pole.

Be Smart
ACADEMY

Characteristics of a generator:



A generator is represented by $G(E, r)$ and characterized by:

- **Electromotive force (E in [V]):**

The maximum voltage across the terminals of the generator at no load.

- **Internal resistance (r in [Ω]):**

The internal resistance causes the heating of the generator while functioning due to Joule's effect.

Characteristics of a generator:



Types of generators

Ideal generator

**generator with
negligible internal
resistance ($r = 0$)**

Actual generator


**generator with internal
resistance ($r \neq 0$)**

Characteristics of a generator:



Application 1: An electric current I leaves the generator from terminal A and enters the terminal B.

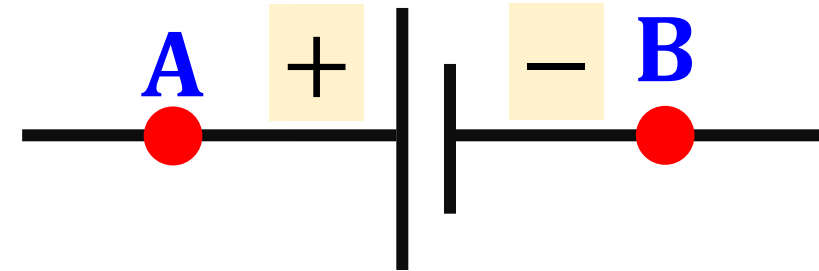1. Which one is the positive pole? Justify



Because the current I leaves the terminal A, then A is the positive pole of the generator and B is the negative pole of the generator

2. The internal resistance of the generator is neglected, specify the type of this generator.

Since the internal resistance is neglected ($r=0$), the generator is ideal

Physics – Grade 10

Unit One – Electricity



Chapter 5

Generator and Receiver

Be Smart
ACADEMY

Prepared & Presented by: **Mr. Mohamad Seif**




OBJECTIVES

1 Current – Voltage characteristic of a Generator

Current – Voltage characteristic of a Generator

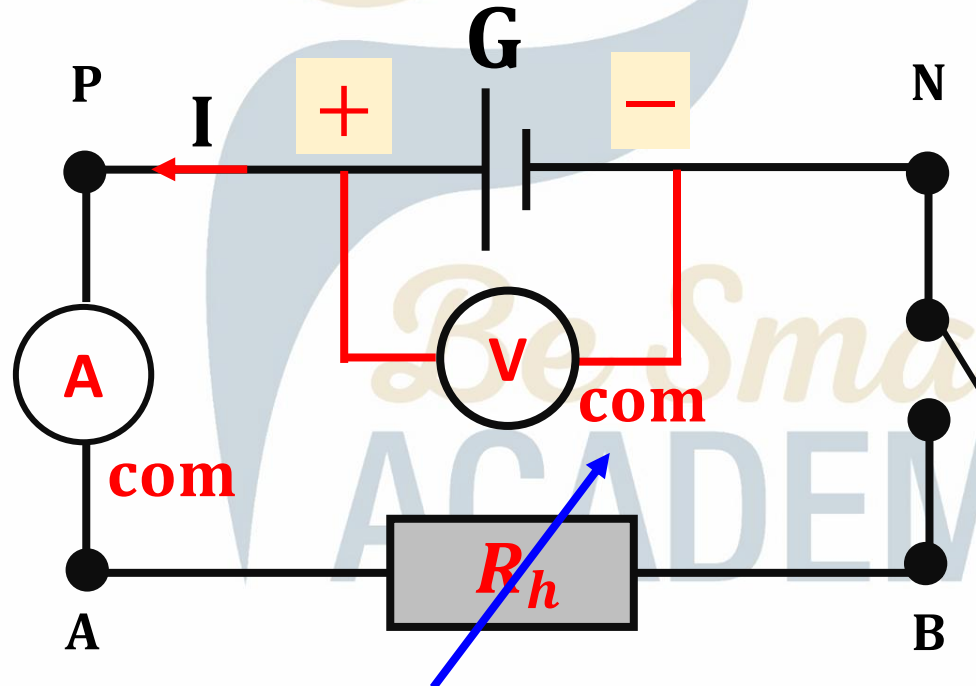- Set up the following electric circuit that consists of **generator G**, **rheostat**, **voltmeter**, **ammeter**, **connecting wires** and a **switch k**.




Current – Voltage characteristic of a Generator



When the switch is opened, the ammeter indicates zero, the voltmeter indicates the maximum value.

After closing the switch:

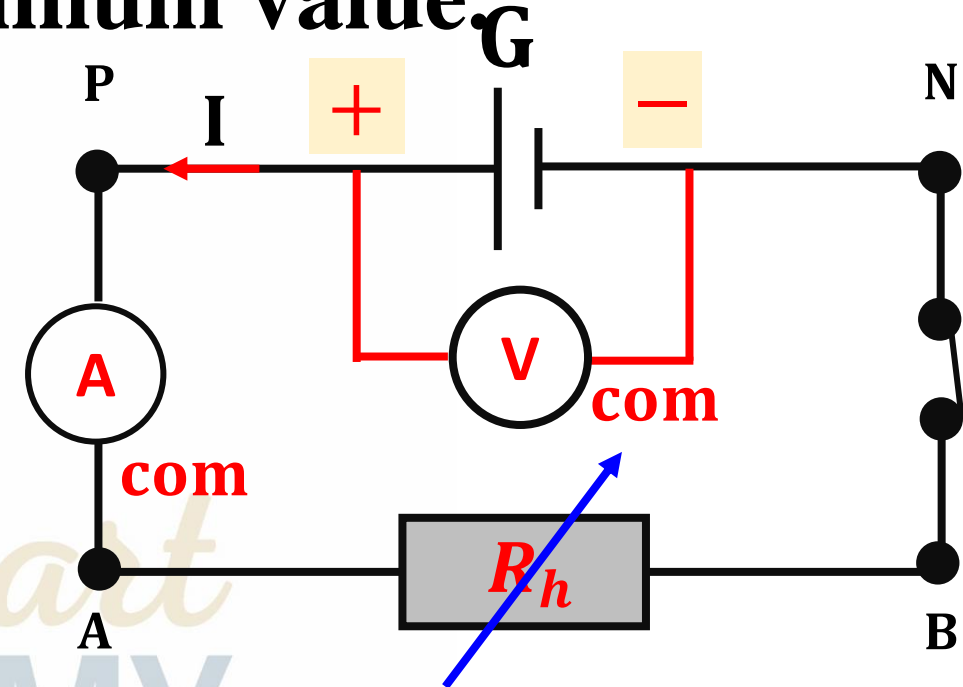- Increase the resistance of the rheostat to a certain value and record the new values of I and V .
- Repeat this step a few times and tabulate the results.



Current – Voltage characteristic of a Generator




The values of the current and the voltage are recorded in the following table

$I(A)$	0	0.1	0.2	0.3
$V(v)$	8	6	4	2

Be Smart
ACADEMY

Current – Voltage characteristic of a Generator

$I(A)$	0	0.1	0.2	0.3
$V(v)$	8	6	4	2

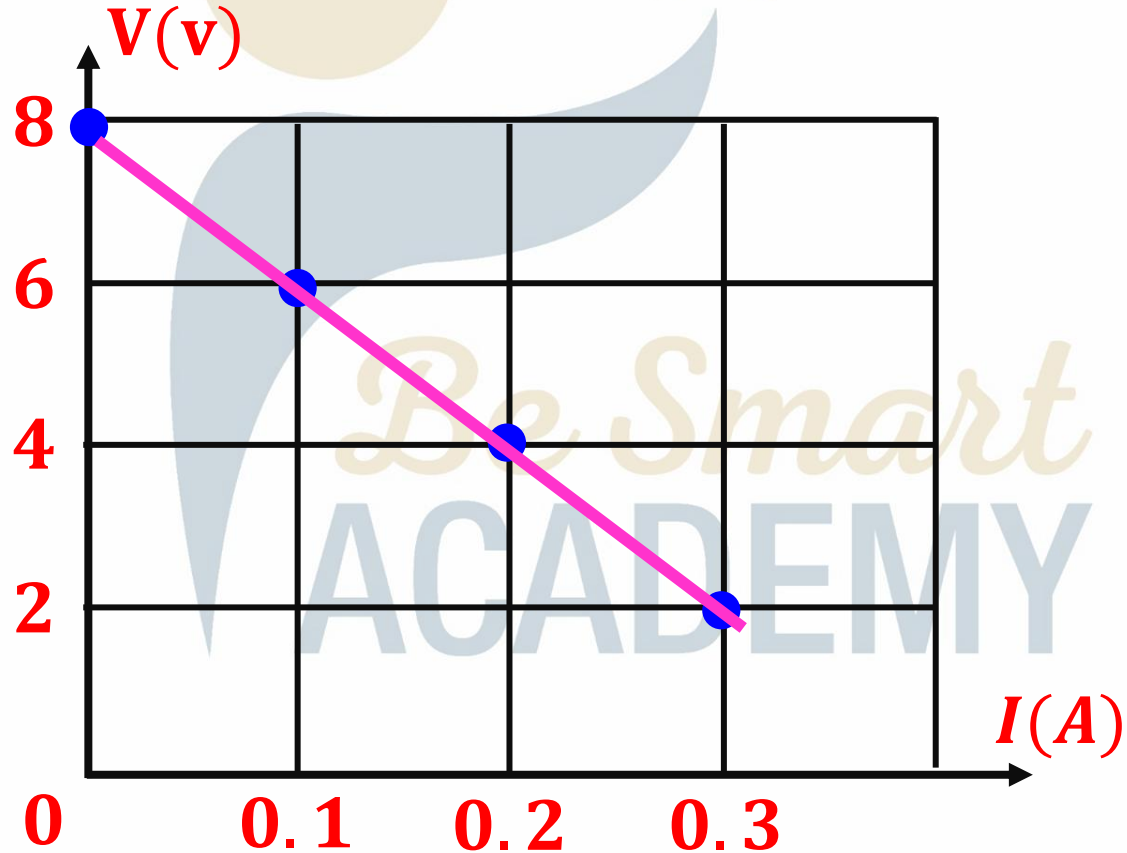

Current – Voltage characteristic of a Generator




This graph is called the **current-voltage characteristics** of a generator.

The curve is a straight line of **negative slope** and **NOT** passing through the **origin**.

The equation of the St. Line is

$$U = a \cdot I + b$$

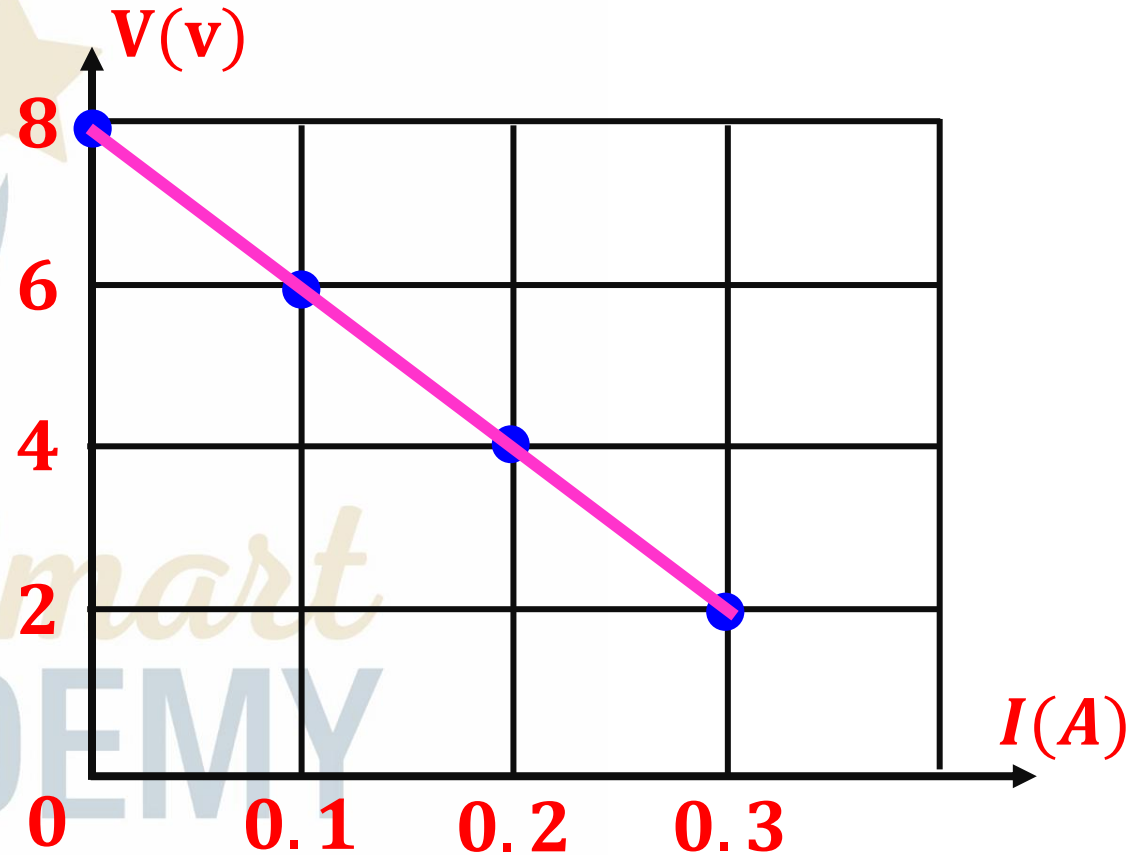a : is the slope of the curve ($a = -r$) and $b = E$.



Current – Voltage characteristic of a Generator


$$U = a \cdot I + b$$

$$a = \frac{V_2 - V_1}{I_2 - I_1}$$

$$a = \frac{6 - 2}{0.1 - 0.3} = \frac{4}{-0.2}$$


$$a = -20V/A$$

$$a = -r = -20$$

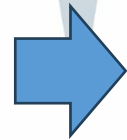


$$r = 20\Omega$$

$b = E$: is the y intercept

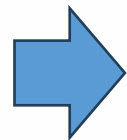

$$b = 8V$$

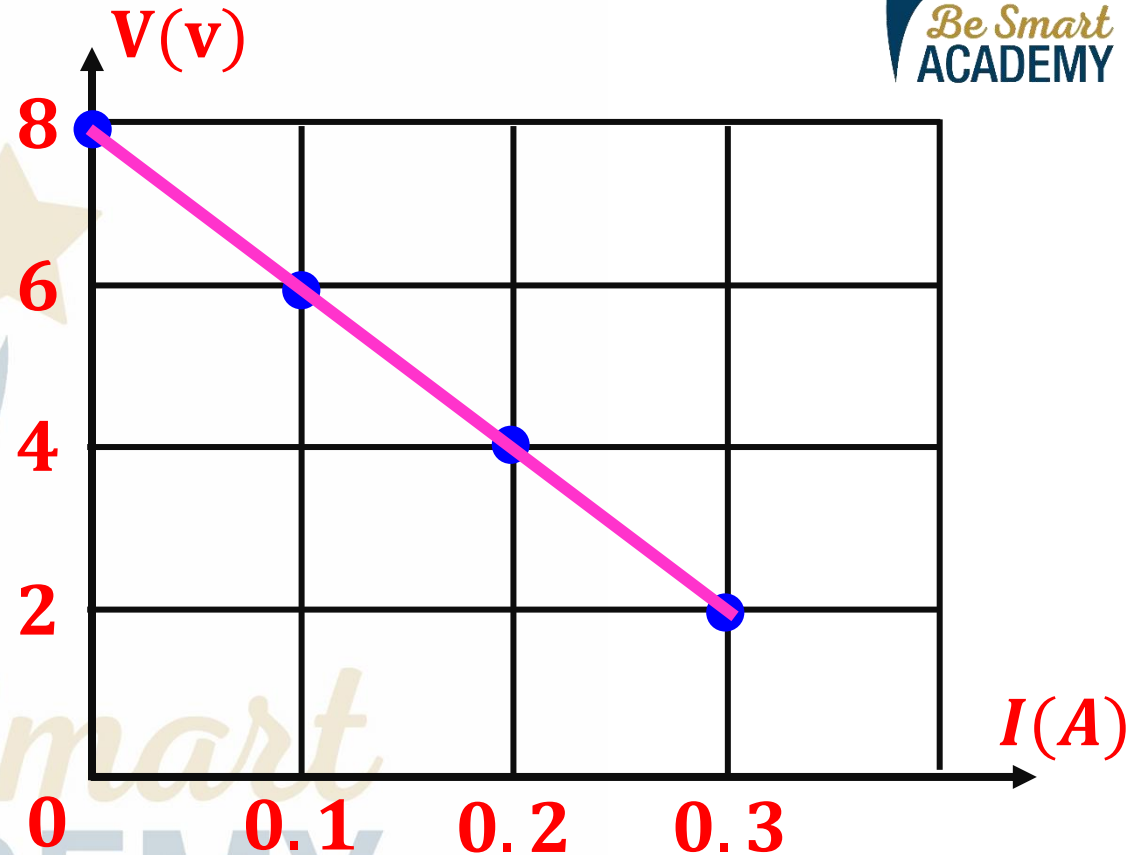

Current – Voltage characteristic of a Generator




Ohm's Law for a generator:

$$U_G = -rI + E$$

E: Electromotive force (maximum voltage), expressed in volts (V).

r: The internal resistance of the generator, expressed in ohm (Ω)

Current – Voltage characteristic of a Generator

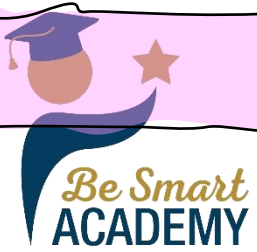

Application 2:

To determine the characteristic values of a generator, we set up an electric circuit.

When we close the switch k , the values of V and I are recorded and tabulated as shown below.

$I(\text{mA})$	0	100	200	300	400	500
$V(\text{V})$	5	4.5	4	3.5	3	2.5

Current – Voltage characteristic of a Generator




1. Draw a figure of the electric circuit.
2. Plot the graph of V as a function of I .
Scale: x-axis: $1cm \rightarrow 100mA$ and y – axis: $1cm \rightarrow 1V$.
3. Determine the equation of the obtained curve.
4. Deduce the electromotive force E and the internal resistance r of the generator.

Be Smart
ACADEMY

Current – Voltage characteristic of a Generator

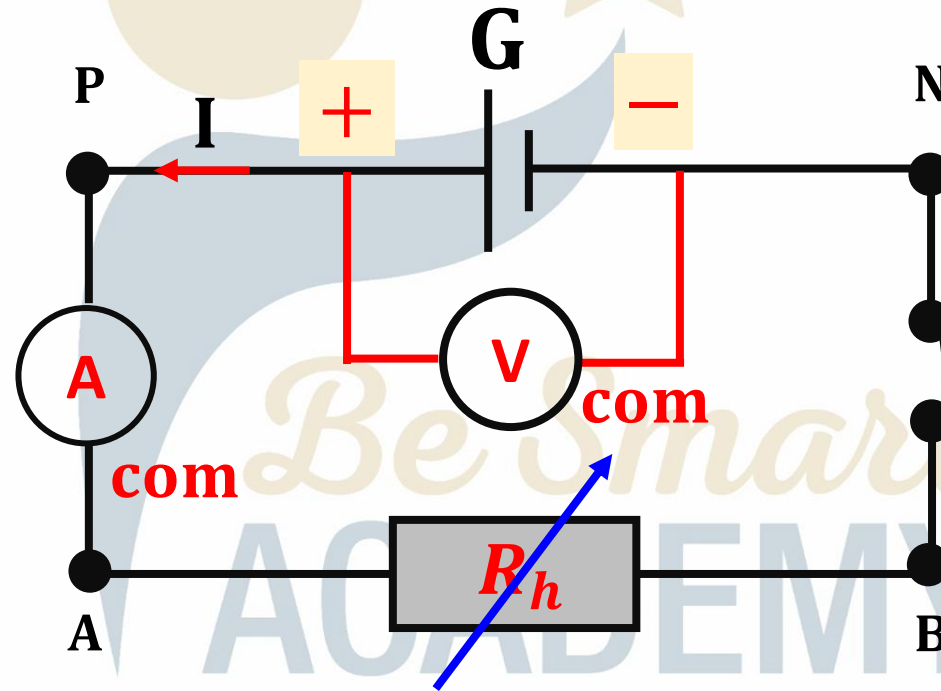1. Draw a figure of the electric circuit.



Current – Voltage characteristic of a Generator



2. Plot the graph of U as a function of I .


Scale:

x-axis: $1\text{cm} \rightarrow 100\text{mA}$

y – axis: $1\text{cm} \rightarrow 1\text{V}$

I(mA)	0	100	200	300	400	500
V(V)	5	4.5	4	3.5	3	2.5

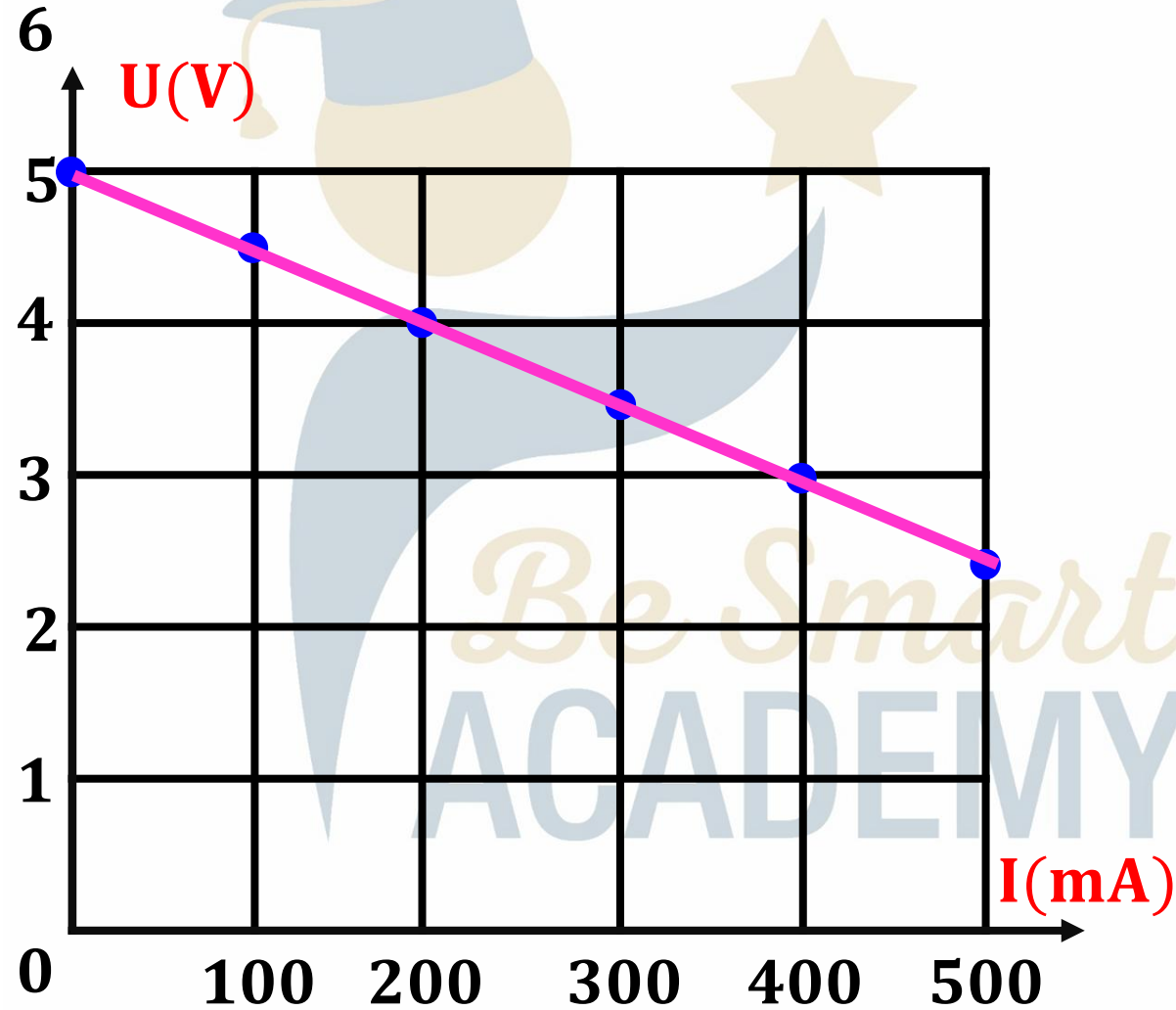Current – Voltage characteristic of a Generator



Current – Voltage characteristic of a Generator


3. Determine the equation of the obtained curve

The obtained curve is St. line of equation $U = aI + b$; where a is the slope and b is y intercept


$$a = \frac{U_2 - U_1}{I_2 - I_1}$$

$$a = \frac{5 - 3}{(0 - 400) \div 1000}$$
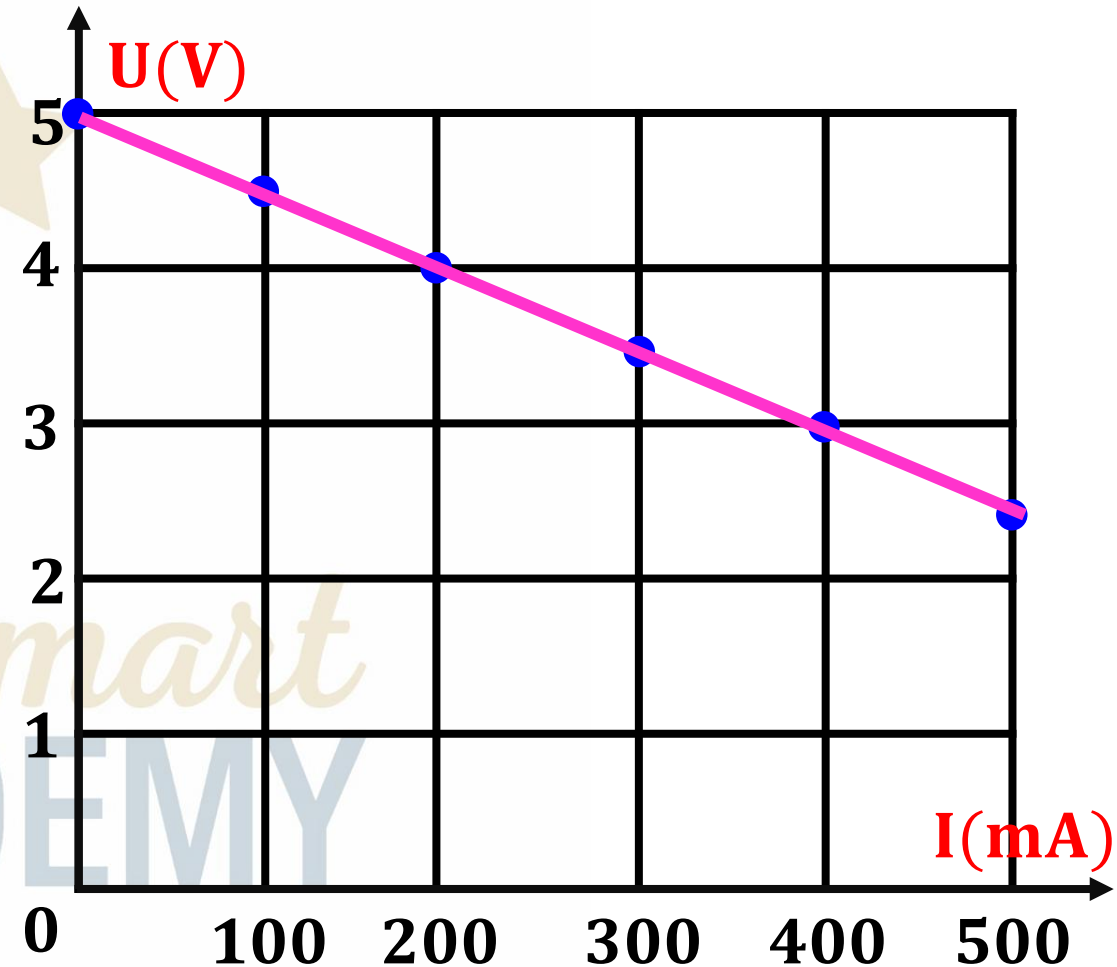
$$a = \frac{2}{-0.4} \rightarrow a = -5 \text{ V/A}$$



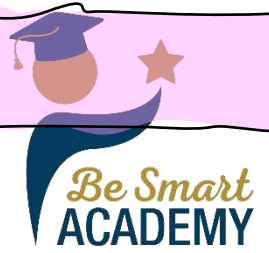Current – Voltage characteristic of a Generator



3. Determine the equation of the obtained curve

$$U = aI + b \rightarrow U = -5I + b$$

b is y-intercept $\rightarrow b = 5$


Substitute $(100\text{mA}; 4.5\text{V})$ in the line equation: $U = -5I + b$

$$4.5 = -5(100 \div 1000) + b$$

$$4.5 = -5 \times 0.1 + b$$

$$4.5 = -0.5 + b$$

$$b = 5\text{V}$$

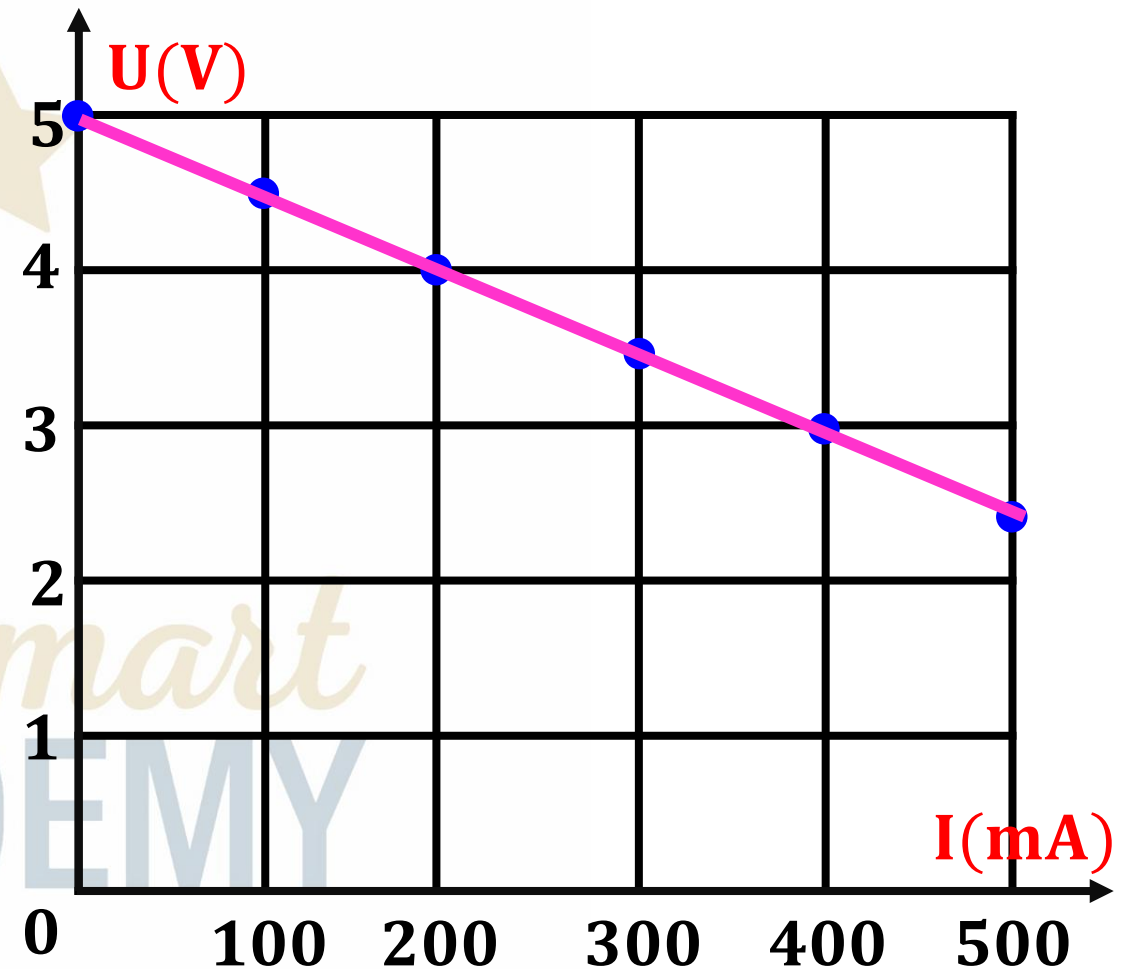

$$U = -4I + 5$$

Current – Voltage characteristic of a Generator




4. Deduce the electromotive force E and the internal resistance r of the generator

The equation of the obtained St. line

Ohm's law of the generator is

Compare the two equations to get:

$$-5 = -r$$

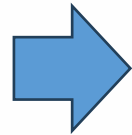

$$r = 5\Omega$$

$$E = 5V$$

$$U = -5I + 5$$

$$U = -rI + E$$

GOOD JOB!





Be Smart Academy

ACADEMY



Physics – Grade 10

Unit One – Electricity



Chapter 5

Generator and Receiver

Be Smart
ACADEMY

Prepared & Presented by: **Mr. Mohamad Seif**



OBJECTIVES

- 1 **Define the receiver**
- 2 **Current – Voltage characteristic of a receiver**

Definition of a receiver



Receiver is an electric device that **converts** the consumed **electric energy** into other **forms of energy**

Electric motor: electric motor converts electric energy to mechanical energy and thermal energy.



Fan: fan converts electric energy to mechanical energy and thermal energy.



Definition of a receiver



A receiver can be represented by $(E'; r')$

$(E'; r')$

A diagram showing the decomposition of the receiver's representation. A central point labeled $(E'; r')$ has two arrows pointing downwards and outwards to two separate text boxes. The left box describes the back electromotive force, and the right box describes the internal resistance.

Back electromotive force, in [V]

The minimum voltage needed by the receiver to operate.

Internal resistance, in $[\Omega]$


That causes the heating of the receiver while functioning due to Joule's effect.

Current – Voltage characteristic of a receiver



Set up the following electric circuit that consists of a **generator G**, **rheostat (R_h)**, **electric motor (M)**, **voltmeter**, **ammeter**, connecting wires and switch k.

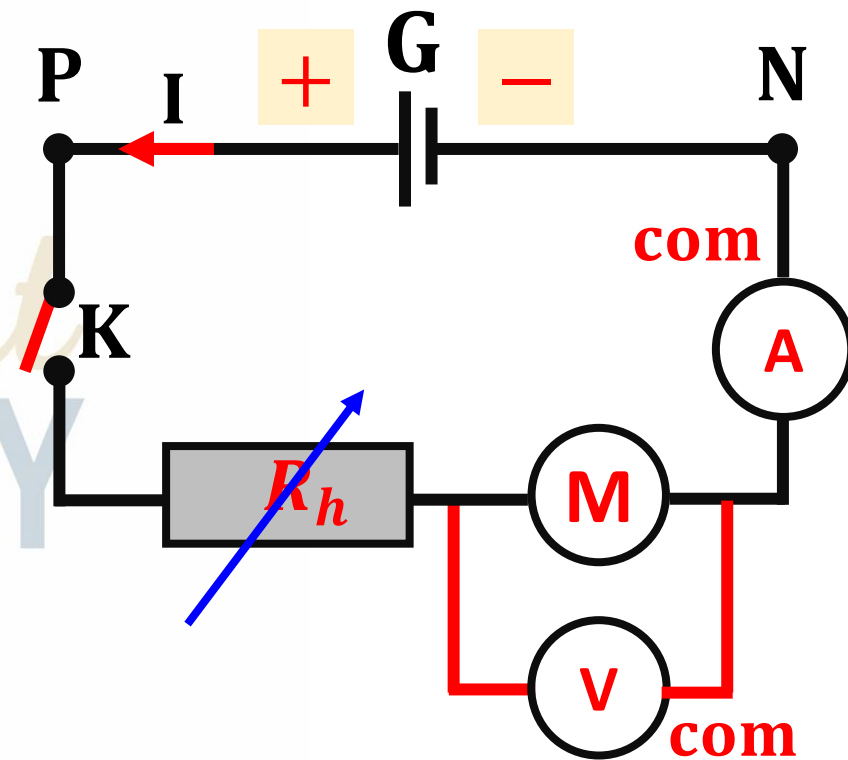When the switch (K) is opened:
The ammeter and the voltmeter indicate zero values.



Current – Voltage characteristic of a receiver




When the switch (K) is closed:

Give the rheostat's cursor different positions; then record the indications of the voltmeter and the Ammeter.


The results are arranged in the following table:

I(mA)	0	100	200	300	400	500
U(V)	3	3.5	4	4.5	5	5.5

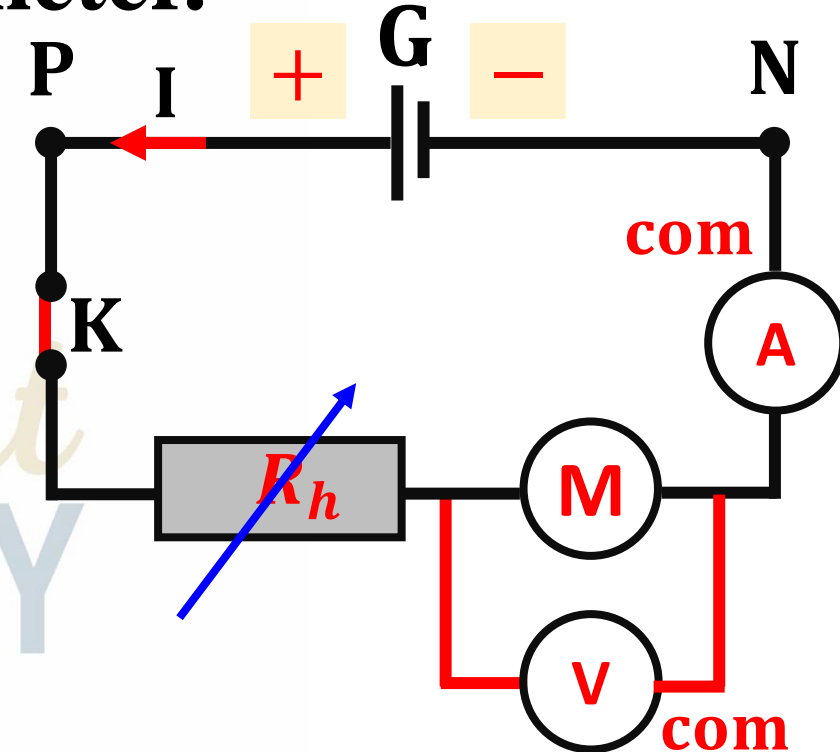

Current – Voltage characteristic of a receiver

I(mA)	0	100	200	300	400
U(V)	2	2.5	3	3.5	4

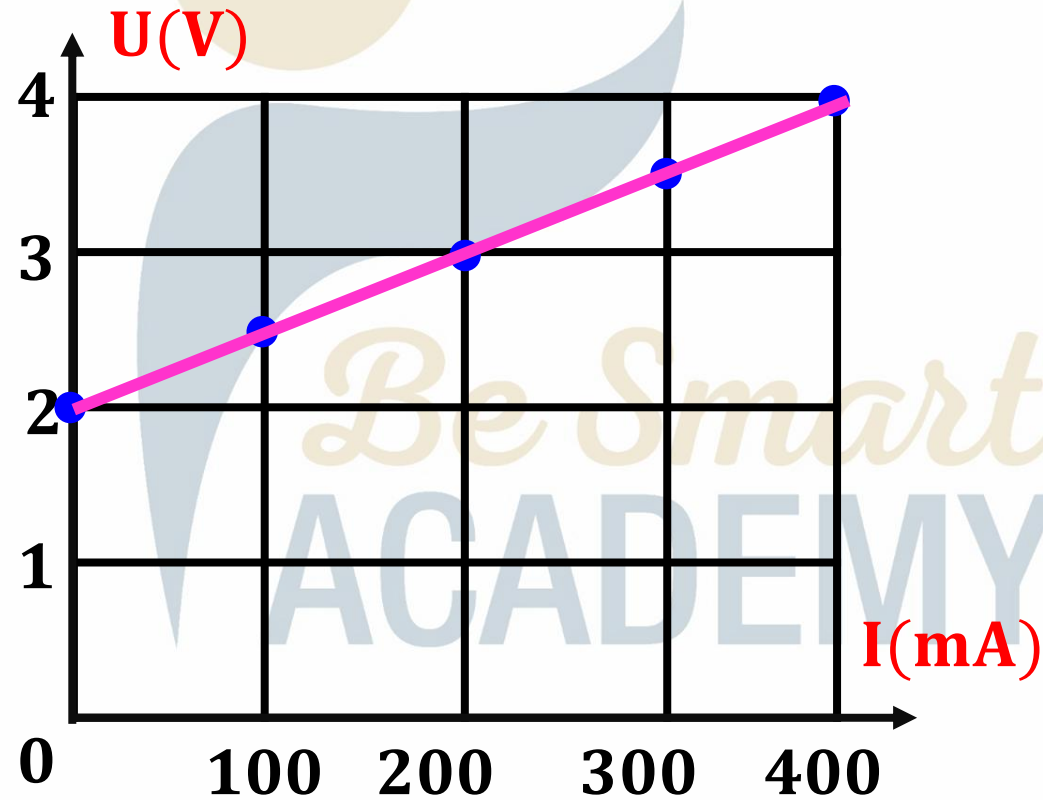

Current – Voltage characteristic of a receiver



We obtain a straight Line of **positive slope** and **NOT passing** through the origin.


This straight Line is called the **Current-voltage Characteristic** of the Receiver.

The equation of this straight line is:

$$U = aI + b$$

a: is the slope of the straight line.

b: is a constant, y- intercept.

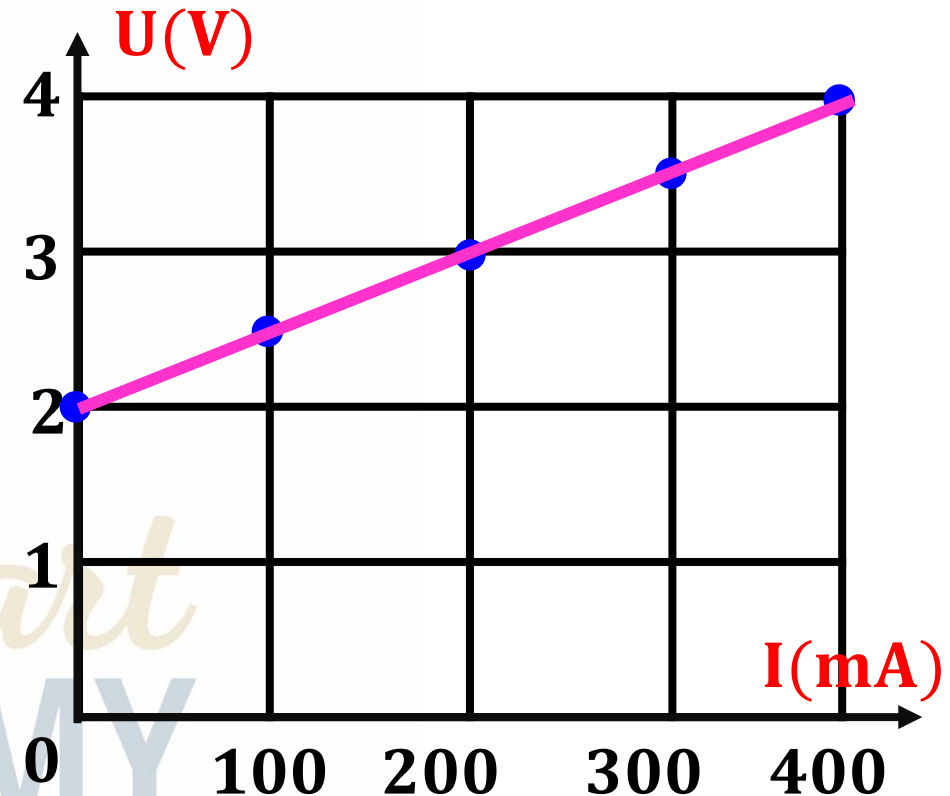

Current – Voltage characteristic of a receiver



Ohm's law of receiver:

$$U = r' I + E'$$

By comparing the equation of St. line with ohm's law

$$U = a. I + b$$

$$U = r' I + E'$$

$$a = r'$$

And

$$b = E'$$

Current – Voltage characteristic of a receiver



Application 3:

To determine the characteristic values of a of an active load (D), we connect it, in series with a rheostat and a generator G. An ammeter used to measure the electric current in the circuit and a voltmeter is connected across the terminals of the load D to record its voltage.

When we close the switch k, and we move the the cursor of the rheostat, the different values U and I are recorded in the table below.

Current – Voltage characteristic of a receiver




I(mA)	0	50	100	150	200
U(V)	2	3	4	5	6


1. Draw a diagram to represent the circuit of the experiment.
2. Draw the graph representing the voltage U as a function of the current I .
3. What is the shape of the obtained graph. Deduce the nature of the load (D).
4. Find the equation of the given straight line.
5. Determine the values of the characteristics of the load (D).

Current – Voltage characteristic of a receiver

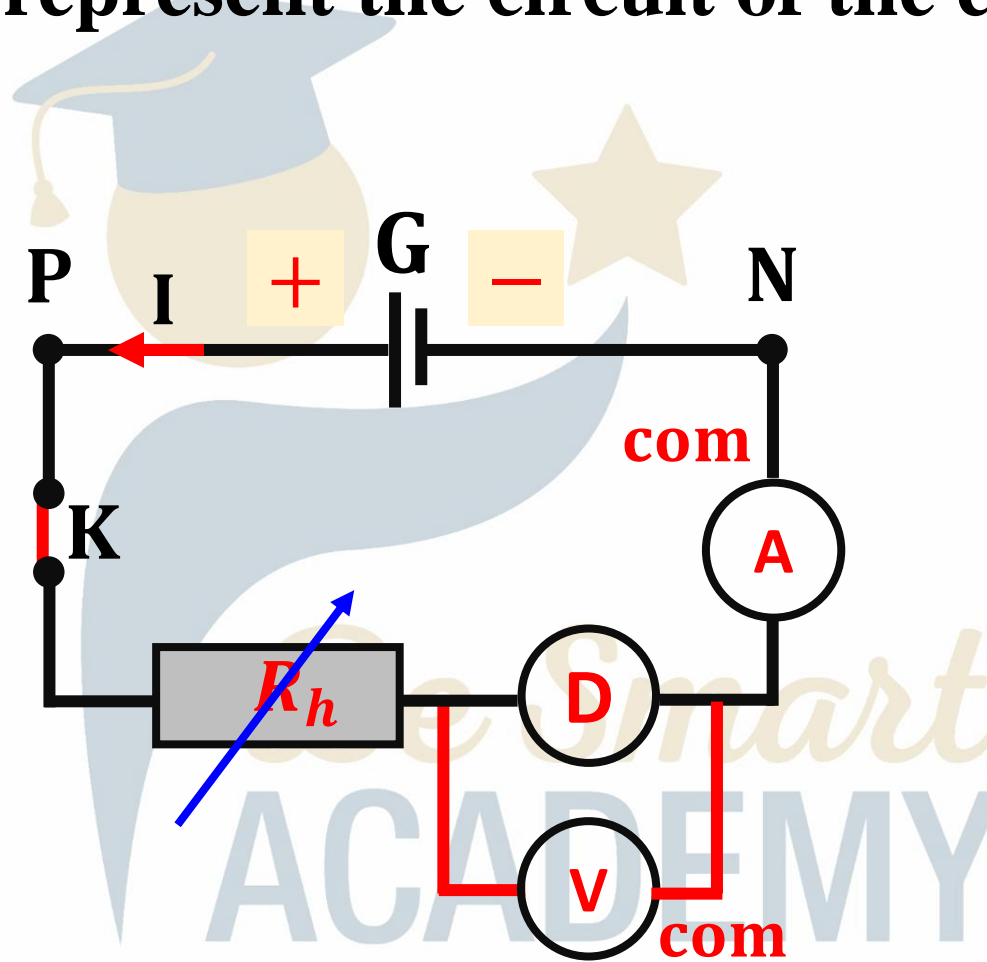1. Draw a diagram to represent the circuit of the experiment.




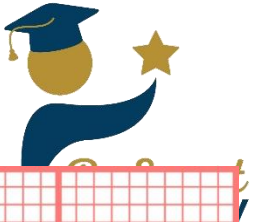Current – Voltage characteristic of a receiver



2. Draw the graph representing the voltage U as a function of the current I .

$I(\text{mA})$	0	50	100	150	200
$U(\text{V})$	2	3	4	5	6

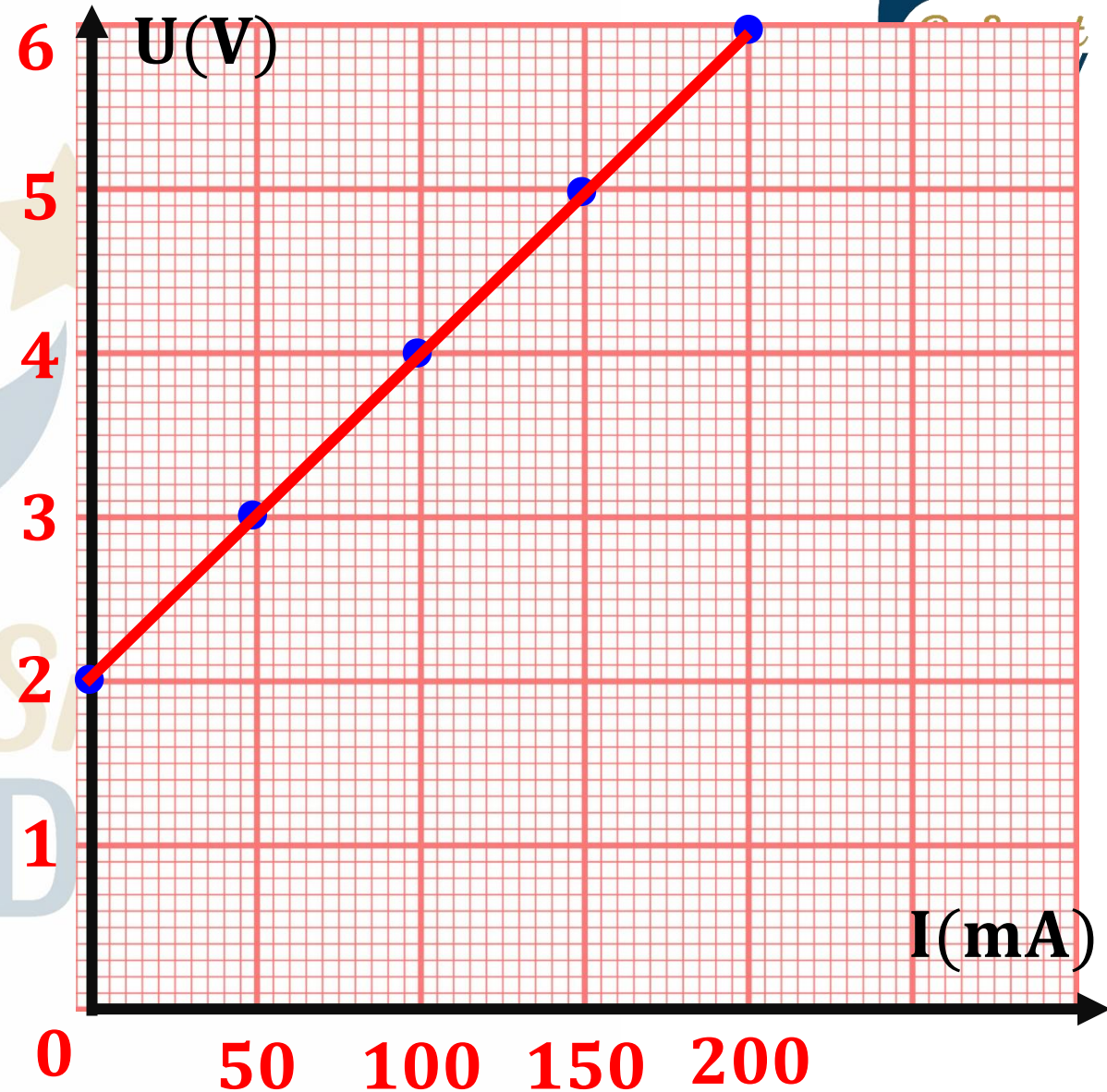


Current – Voltage characteristic of a receiver



3. What is the shape of the obtained graph. Deduce the nature of the load (D).

The obtained graph is a **St. line of positive slope and not passing through the origin.**

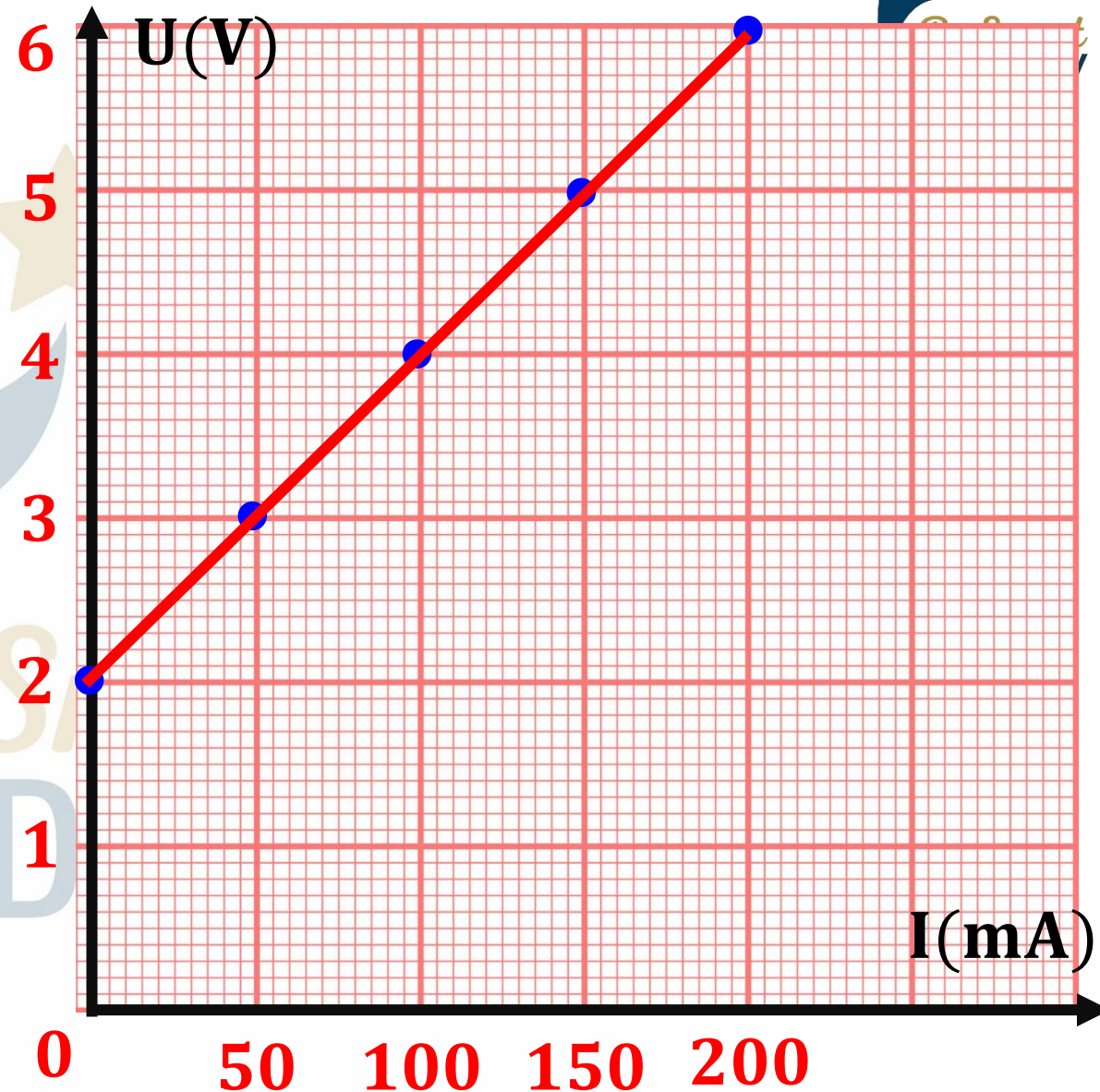(D) is a receiver, since its graph is a St. line of positive slope and not passing through the origin.



Current – Voltage characteristic of a receiver



4. Find the equation of the given straight line.


The equation of the St. line is:

$$U = aI + b$$

$$\text{slope} = a = \frac{U_2 - U_1}{I_2 - I_1}$$

$$a = \frac{5 - 3}{(150 - 50) \div 1000}$$

$$a = \frac{2}{0.1} = 20\text{V/A}$$

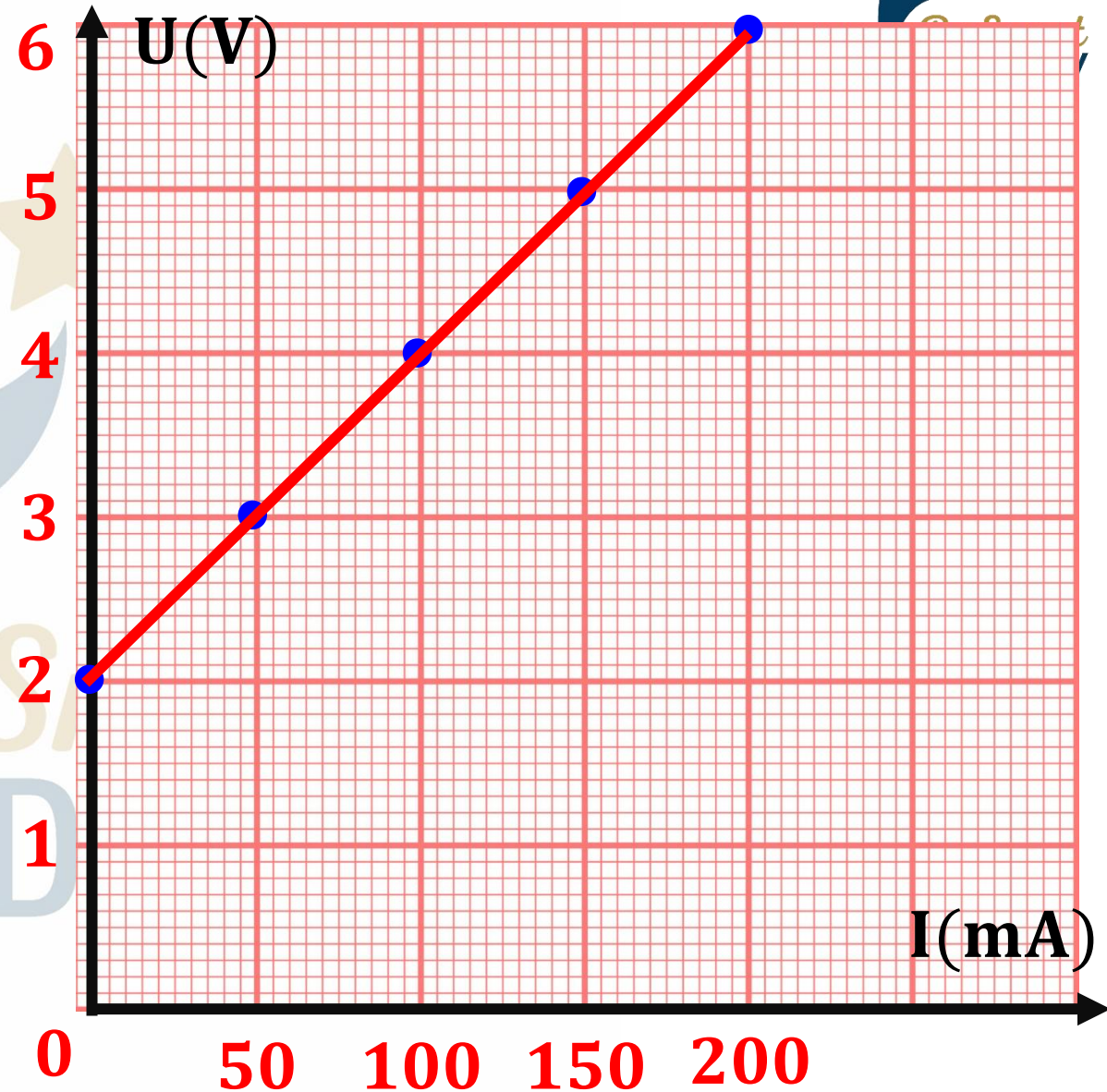

Current – Voltage characteristic of a receiver



$$a = 20\text{V/A}$$

$$U = 20I + b$$

b: is y-intercept then $b = 2$

Substitute $(50\text{mA}; 3\text{V})$ in the equation:


$$U = 20I + b$$

$$3 = 20 \times (50 \div 1000) + b$$

$$3 = 20 \times (0.05) + b$$

$$3 = 1 + b \quad \Rightarrow \quad b = 2$$

$$U = 20I + 2$$

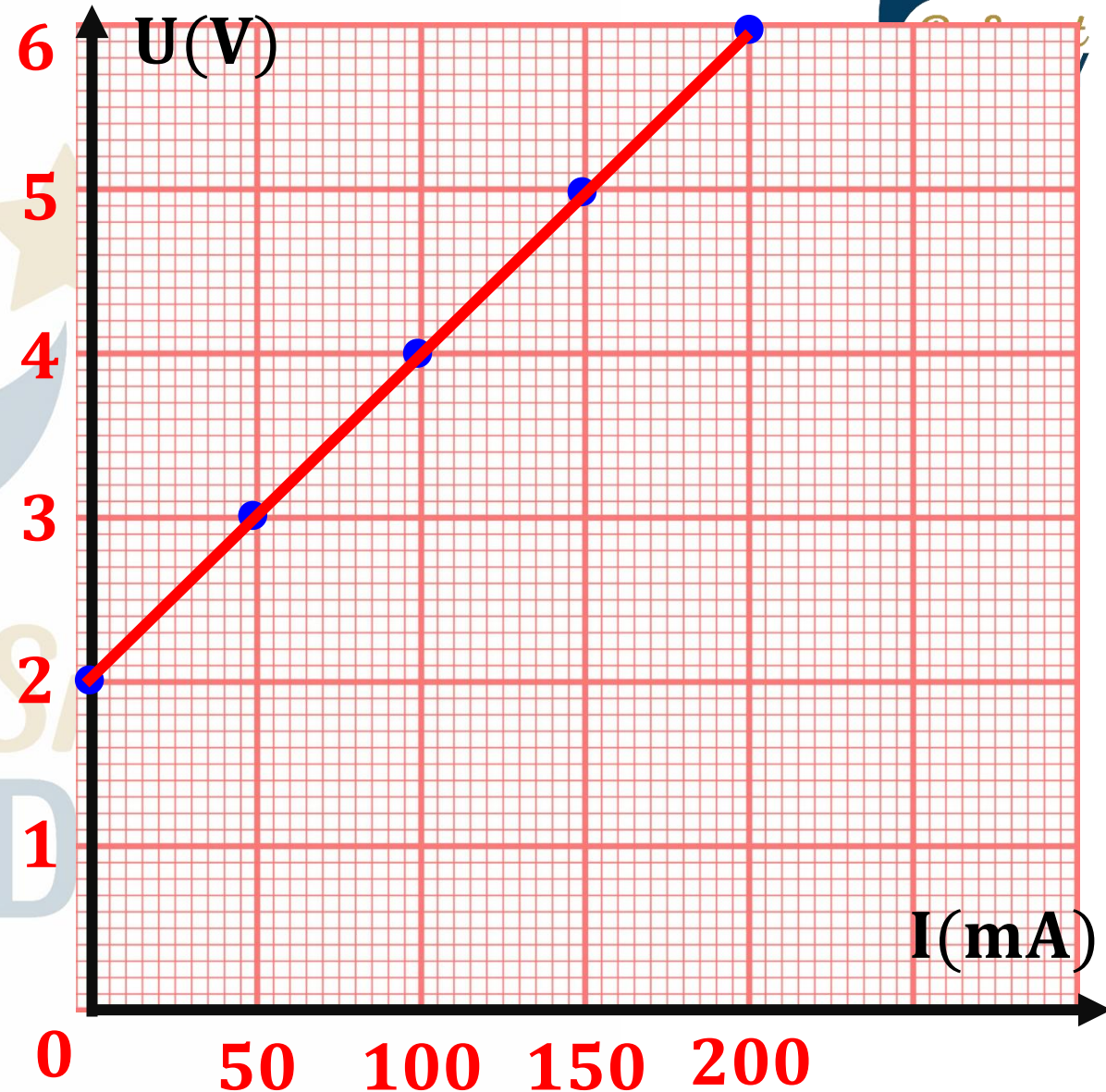

Current – Voltage characteristic of a receiver



5. Determine the values of the characteristics of the load (D).

St. line: $U = 20I + 2$ Ohm's law is $U = r'I + E'$

Compare the two equations:

$$r' = 20\Omega$$

$$E' = 2V$$

Physics – Grade 10

Unit One – Electricity



Chapter 5

Generator and Receiver

Be Smart
ACADEMY

Prepared & Presented by: **Mr. Mohamad Seif**



OBJECTIVES

1 Power consumed by a Receiver

2 The efficiency of a motor

ACADEMY

Power consumed by a Receiver



The expression of consumed power by receiver is:

$$P = V \times I$$

But the voltage of a receiver is:

$$V = r' \cdot I + E'$$

Then:

$$P = (r' I + E') \times I$$

$$P = r' \cdot I^2 + E' \cdot I$$

The **power dissipated (lost)** by the receiver due to Joule's effect:

$$P_{\text{dis}} = r' \cdot I^2$$

The **useful power** delivered by the receiver:

$$P_{\text{useful}} = E' I$$

$$P_{\text{consumed}} = P_{\text{dis}} + P_{\text{useful}}$$

Power consumed by a Receiver



Blocked motor:

The voltage across a receiver is:

$$V = r'I + E'$$

For a blocked motor:

$$E' = 0V$$

$$V = r'I + E'$$

$$V = r'I$$

In this case the motor acts as a pure resistor.

The efficiency of a motor



The efficiency of a motor:

$$\rho = \frac{P_{out}}{P_{in}} \times 100$$

$$\rho = \frac{P_{useful}}{P_{consumed}} \times 100$$

$$\rho = \frac{E' I}{V \times I}$$

$$\rho = \frac{E'}{V} \times 100$$

E' : back electromotive force of a receiver

V : voltage across the terminals of the receiver.

Power consumed by a Receiver



Application 4:

An electric motor M is characterized by $M(8V; 2\Omega)$.

The motor M receives a current $I = 3A$ during its normal function.

1. Calculate the power lost by the motor.
2. Calculate the power used by the motor.
3. Deduce the power consumed by the motor.
4. Determine the efficiency of this motor

Power consumed by a Receiver



M(8V; 2Ω); I = 3A

1. Calculate the power lost by the motor.

$$P_{\text{lost}} = r' I^2$$

$$P_{\text{lost}} = 2 \times (3)^2$$

$$P_{\text{lost}} = 18 \text{ Watt}$$

2. Calculate the power used by the motor.

$$P_{\text{used}} = E' \cdot I$$

$$P_{\text{used}} = 8 \times 3$$

$$P_{\text{used}} = 24 \text{ Watt}$$

Power consumed by a Receiver



M(8V; 2Ω); I = 3A

3. Deduce the power consumed by the motor

$$P_{consumed} = P_{lost} + P_{used}$$

$$P_{consumed} = 18 + 24$$

$$P_{consumed} = 42 \text{ Watt}$$

4. Determine the efficiency of this motor

$$\rho = \frac{P_{useful}}{P_{consumed}} \times 100$$

$$\rho = \frac{24}{42} \times 100$$

$$\rho = 57.14\%$$

Physics – Grade 10

Unit One – Electricity



Chapter 5

Generator and Receiver

Be Smart
ACADEMY

Prepared & Presented by: **Mr. Mohamad Seif**



OBJECTIVES

1 Generators in series

2 Generators in opposition

ACADEMY

Generators in series



The **positive pole** of $G_1(E_1; r_1)$ is connected to the **negative pole** of $G_2(E_2; r_2)$ then:

Both G_1 and G_2 act as a generator $G(E; r)$, where:

$$E = E_1 + E_2$$

and

$$r = r_1 + r_2$$




Generators in series



Application 5:

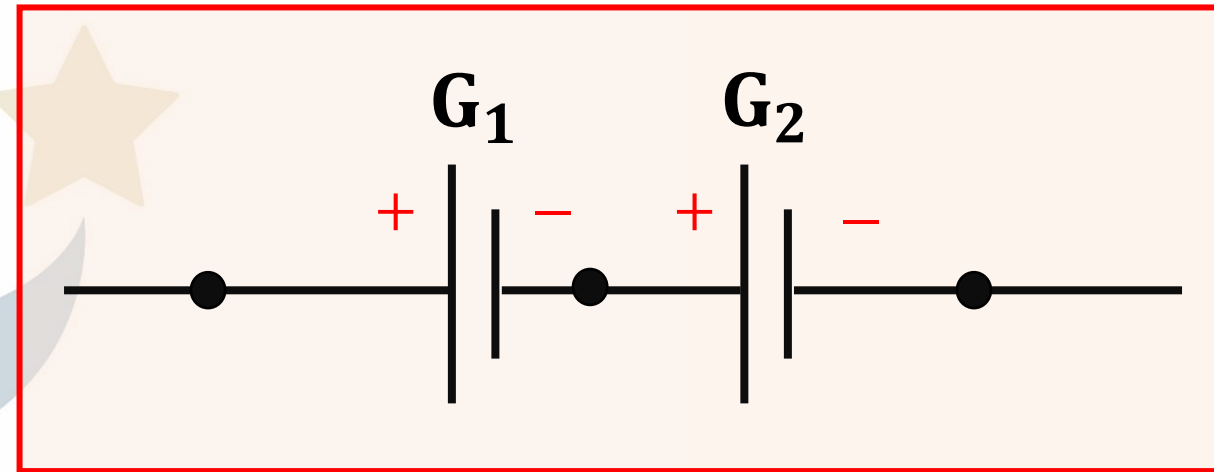
Consider two generators $G_1(5V; 1\Omega)$ and $G_2(8V; 2\Omega)$ connected as shown in the figure. Identify the role of each one



Both G_1 and G_2 acts as generators, since the negative pole of G_1 connected to positive pole of G_2

G_1 and G_2 can be replaced by G such that:

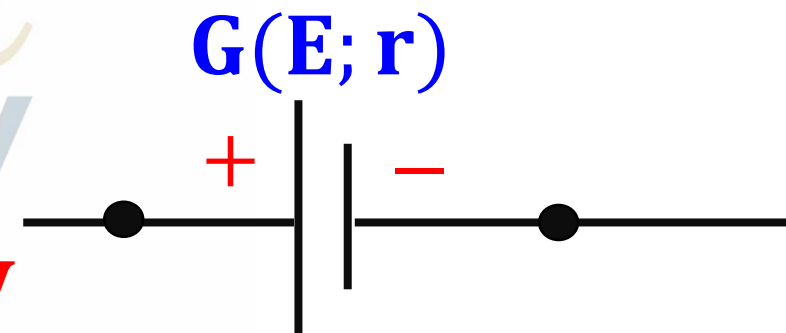
$$\begin{aligned} E &= E_1 + E_2 \Rightarrow E = 5V + 8V \Rightarrow E = 13V \\ r &= r_1 + r_2 \Rightarrow r = 1\Omega + 2\Omega \Rightarrow r = 3\Omega \end{aligned}$$



Generators in opposition



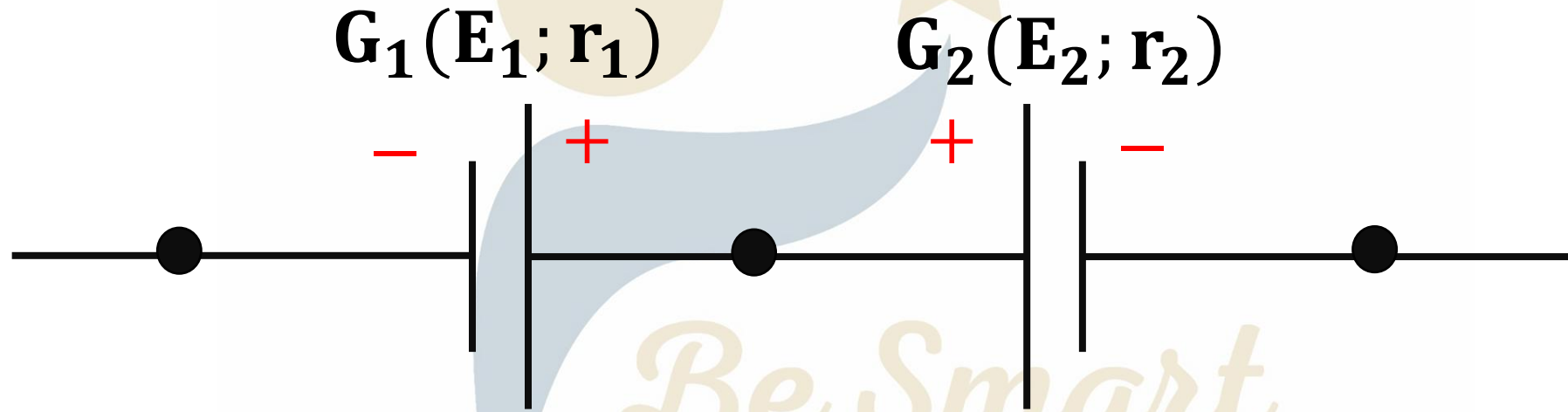The **positive pole** of $G_1(E_1; r_1)$ is connected to the **positive pole** of $G_2(E_2; r_2)$ then:




Then, the generator with **higher electromotive force acts as a generator** while **the other acts as a receiver**

Generators in opposition



Application 6:

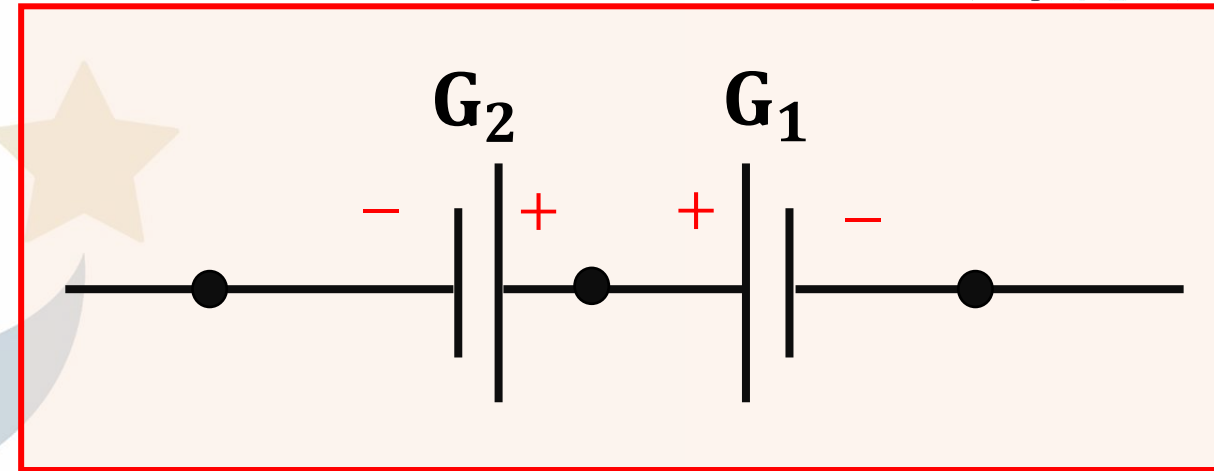Consider two generators $G_1(11V; 1\Omega)$ and $G_2(5V; 2\Omega)$ connected as shown in the figure. Identify the role of each one



The positive pole of G_1 is connected to positive pole of G_2 :

The one with higher electromotive force acts as generator, while the other acts as receiver

Since $E_1 = 11V > E_2 = 5V$:

Then G_1 acts as a **generator** and G_2 acts as a **receiver**

The End

