

Physics – Grade 10

Unit One – Electricity



Chapter 5 Generator and Receiver

Prepared & Presented by: **Mr. Mohamad Seif**




Think then Solve

Exercise 1:



Two generators $G_1(6V, 2\Omega)$, $G_2(18V, 1\Omega)$ are connected with a resistor of resistance $R = 20\Omega$ as shown in the adjacent figure.

1. Specify the role of G_1 and G_2 .
2. Draw the direction of the current in this circuit.
3. The current sent by the generator is $I = 0.5\text{ A}$.
 - a. Calculate the voltage across G_1 .
 - b. Calculate the voltage across G_2 .
 - c. Calculate the voltage across R

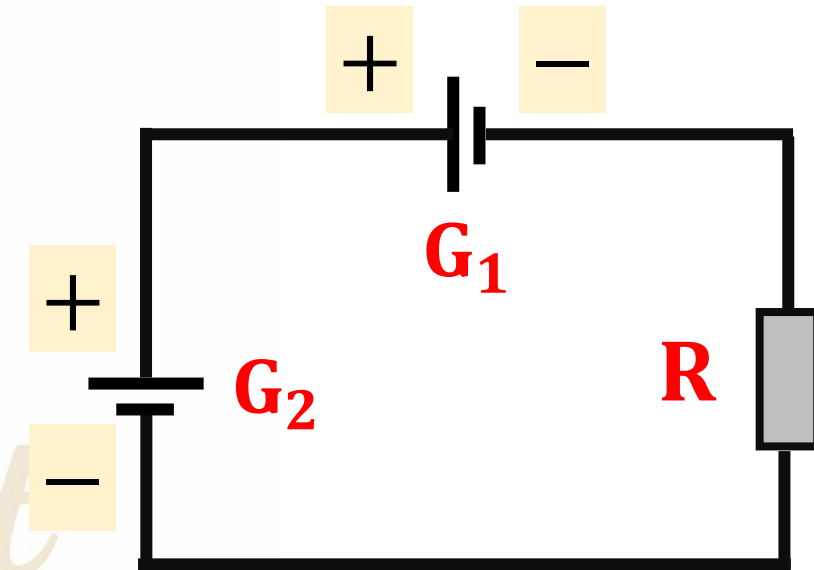

Exercise 1:



$G_1(6V, 2\Omega)$; $G_2(18V, 1\Omega)$ and $R = 20\Omega$.


1. Specify the role of G_1 and G_2 .

The positive pole of G_1 is connected to positive pole of G_2 then:

The two generators are connected in opposition then:

The one with higher electromotive force is the generator and the other is receiver:

G_2 is generator and G_1 is a receiver

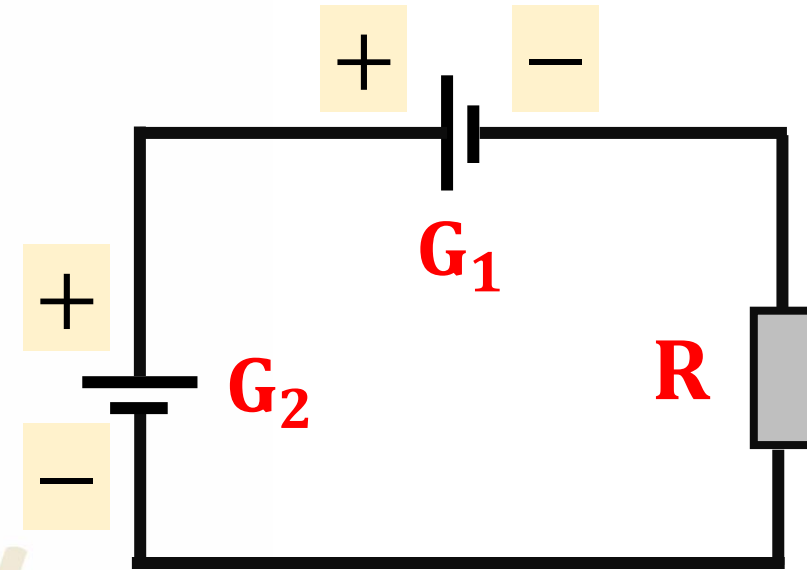

Exercise 1:



$G_1(6V, 2\Omega)$; $G_2(18V, 1\Omega)$ and $R = 20\Omega$.

2. Draw the direction of the current in this circuit.

The current leaves from positive pole of the generator.

3. The current send by the generator is $I = 0.5\text{ A}$


a. Calculate the voltage across G_1 .

$$U = r'I + E'$$

$$U = (2 \times 0.5) + 6$$

$$U = (1) + 6$$

$$U = 7V$$

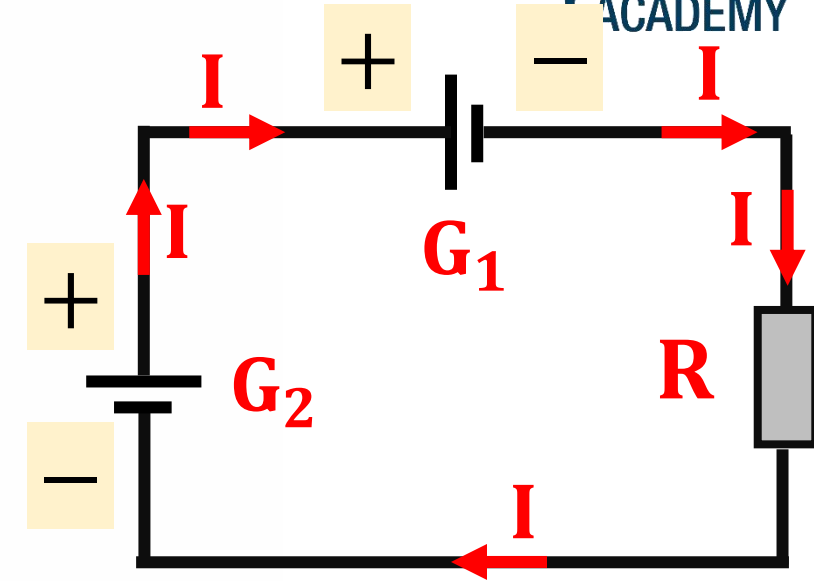

Exercise 1:



$G_1(6V, 2\Omega)$; $G_2(18V, 1\Omega)$ and $R = 20\Omega$.

b. Calculate the voltage across G_2 .

$$V = -rI + E$$

$$V = (-2 \times 0.5) + 18$$

$$V = (-1) + 18$$

$$V = 17V$$

c. Calculate the voltage across the resistor R .

$$V = RI$$

$$V = 20 \times 0.5$$

$$V = 10V$$




Think then Solve

Exercise 2:



A generator of characteristics $(E; r)$ is connected in series to an electric motor of $(E' = 6V; r' = 2\Omega)$ and to a resistor of resistance $R = 8\Omega$ as shown in the adjacent figure.

1. The motor functions normally and the power dissipated by the resistor is 2 W.
 - a. Calculate the current I_1 flowing in the circuit.
 - b. Determine the voltage across the generator.
 - c. Deduce a relation between E , and r .

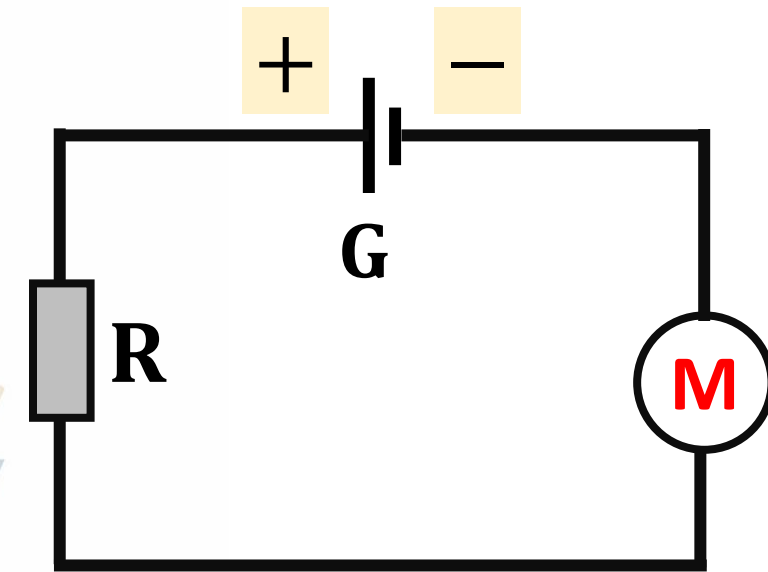

Exercise 2:



- 2. The motor is blocked; the power dissipated in R becomes 8W.**
- a. Calculate the current I_2 flowing in the circuit.**
 - b. Determine the voltage across the generator.**
 - c. Deduce a new relation between E and r .**
- 3. Using the relations in parts 2.c and 3.c, determine the values of E and r .**

Exercise 2:



$G(E; r); M(E' = 6V; r' = 2\Omega); R = 8\Omega$

1. The motor functions normally and the power dissipated in R is 2 W.

a. Calculate the current I_1 flowing in the circuit.

$$P = RI^2$$


$$I^2 = \frac{P}{R}$$

$$I^2 = \frac{P}{R} = \frac{2}{8}$$

$$I^2 = 0.25$$

$$I = \sqrt{0.25}$$

$$I = 0.5A$$

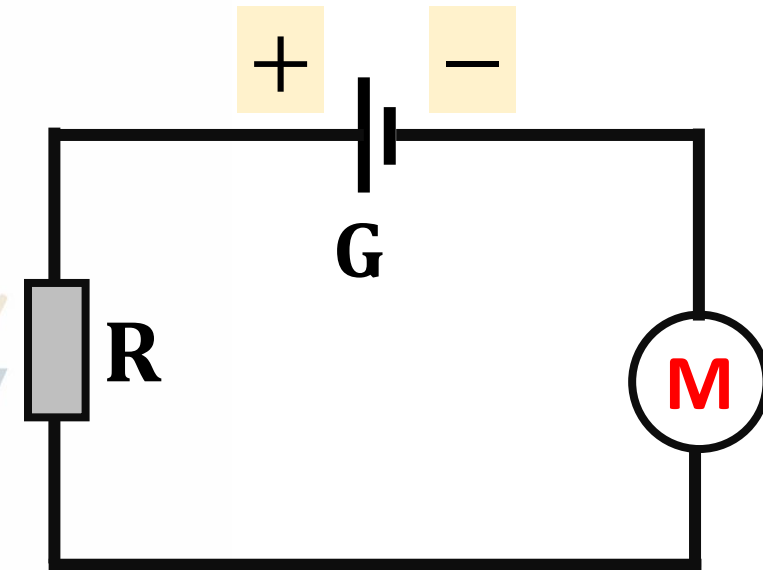

Exercise 2:



$G(E; r); M(E' = 6V; r' = 2\Omega); R = 8\Omega$

b. Determine the voltage across the generator.


Applying law of addition of voltage:

$$U_G = U_R + U_M$$

$$U_G = RI + r'I + E'$$

$$U_G = 8 \times 0.5 + 2 \times 0.5 + 6$$

$$U_G = 11V$$

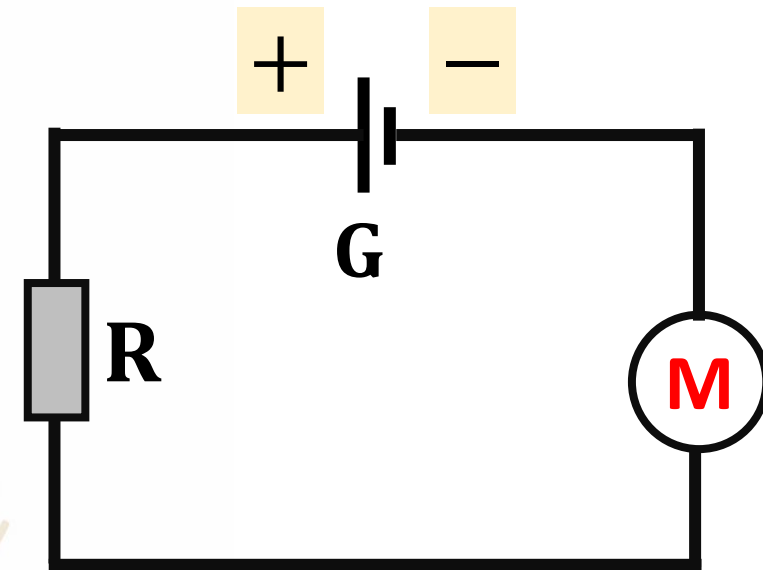

Exercise 2:




$G(E; r); M(E' = 6V; r' = 2\Omega); R = 8\Omega$

c. Deduce a relation between E , and r .

Using ohm's law of generator:

$$U_G = -rI + E$$

$$11 = -0.5r + E \dots \dots (1)$$

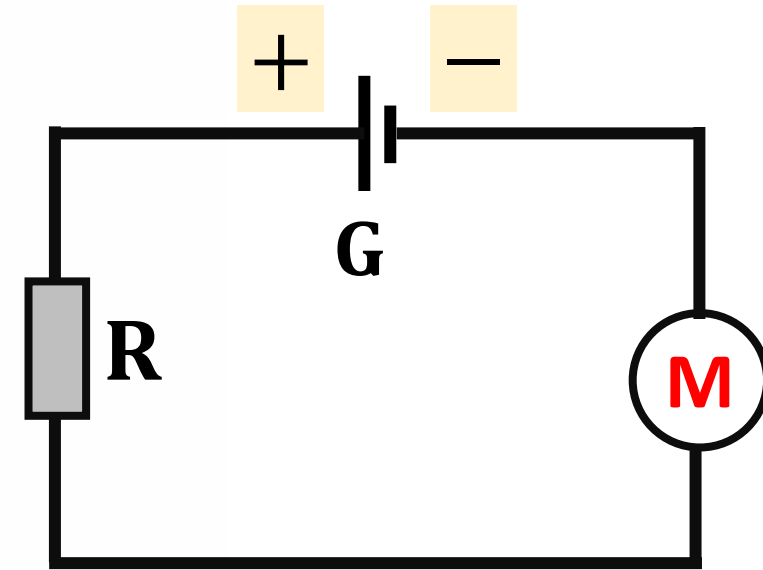

Exercise 2:



$G(E; r); M(E' = 0V; r' = 2\Omega); R = 8\Omega$


2. The motor is blocked; the power dissipated by R becomes 8W.
a. Calculate the current I_2 flowing in the circuit.

$$P = RI^2$$

$$I^2 = \frac{8}{8} = 1$$

$$I^2 = \frac{P}{R}$$

$$I = 1A$$

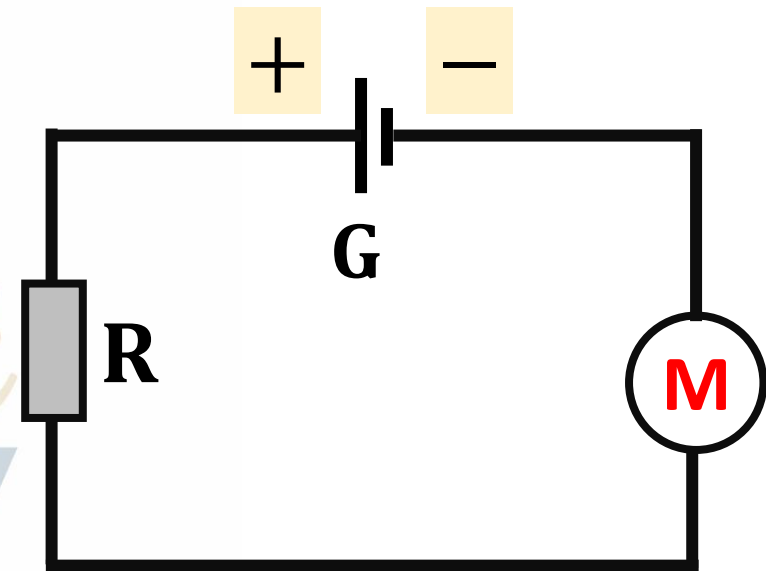

Exercise 2:



$G(E; r); M(E' = 0; r' = 2\Omega); R = 8\Omega$

b. Determine the voltage the generator.


Applying law of addition of voltage:

$$U_G = U_R + U_M$$

$$U_G = RI + r'I + E'$$

$$U_G = 8 \times 1 + 2 \times 1 + 0$$

$$U_G = 10V$$

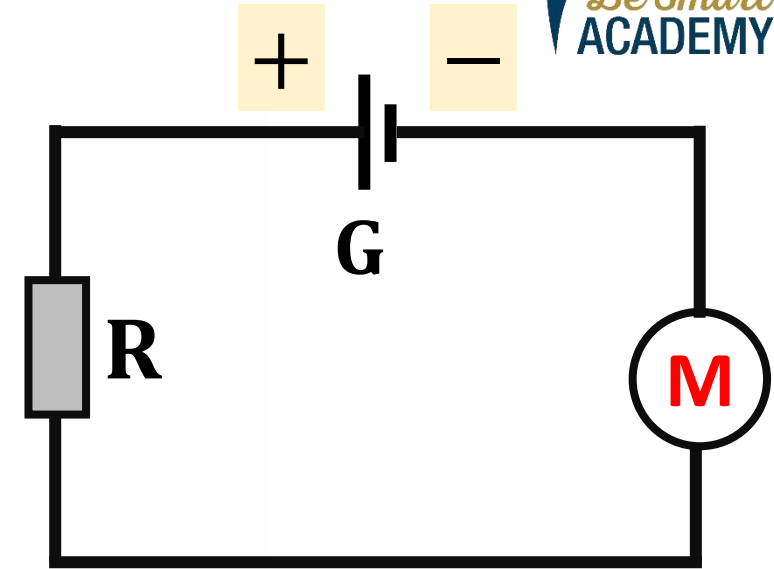

Exercise 2:



c. Deduce a new relation between E and r.

$$U_G = rI + E \quad \Rightarrow \quad 10 = -r + E \dots \dots (2)$$

4. Using the relations in parts 2.c and 3.c, determine the values of E and r.

$$\begin{cases} 11 = -0.5r + E \dots \dots (1) \\ 10 = -r + E \dots \dots (2) \end{cases}$$

Solving the system, we get:

$$\begin{cases} 11 = -0.5r + E \dots \dots \\ 10 = -r + E \dots \dots \times (-1) \end{cases}$$

Exercise 2:



$$\begin{cases} 11 = -0.5r + E \\ -10 = +r - E \end{cases}$$

Add the two equations:

$$11 - 10 = -0.5r + E + r - E$$

$$1 = +0.5r$$

$$r = \frac{1}{0.5}$$

$$r = 2\Omega$$

Substitute $r = 2\Omega$ in any equation:


$$11 = -0.5r + E$$

$$11 = -0.5(2) + E$$

$$11 = -1 + E$$

$$E = 12V$$

The End

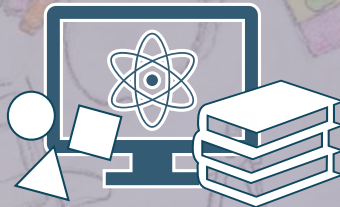




Think then Solve

Exercise 3:

The adjacent graph represents the curves of three electric dipoles: a motor M (E' ; r'), a generator G (E , r) and a resistor R .

1. Referring to the figure, associate to each dipole its corresponding graph.
2. Using the figure, determine the characteristic constants of each dipole.

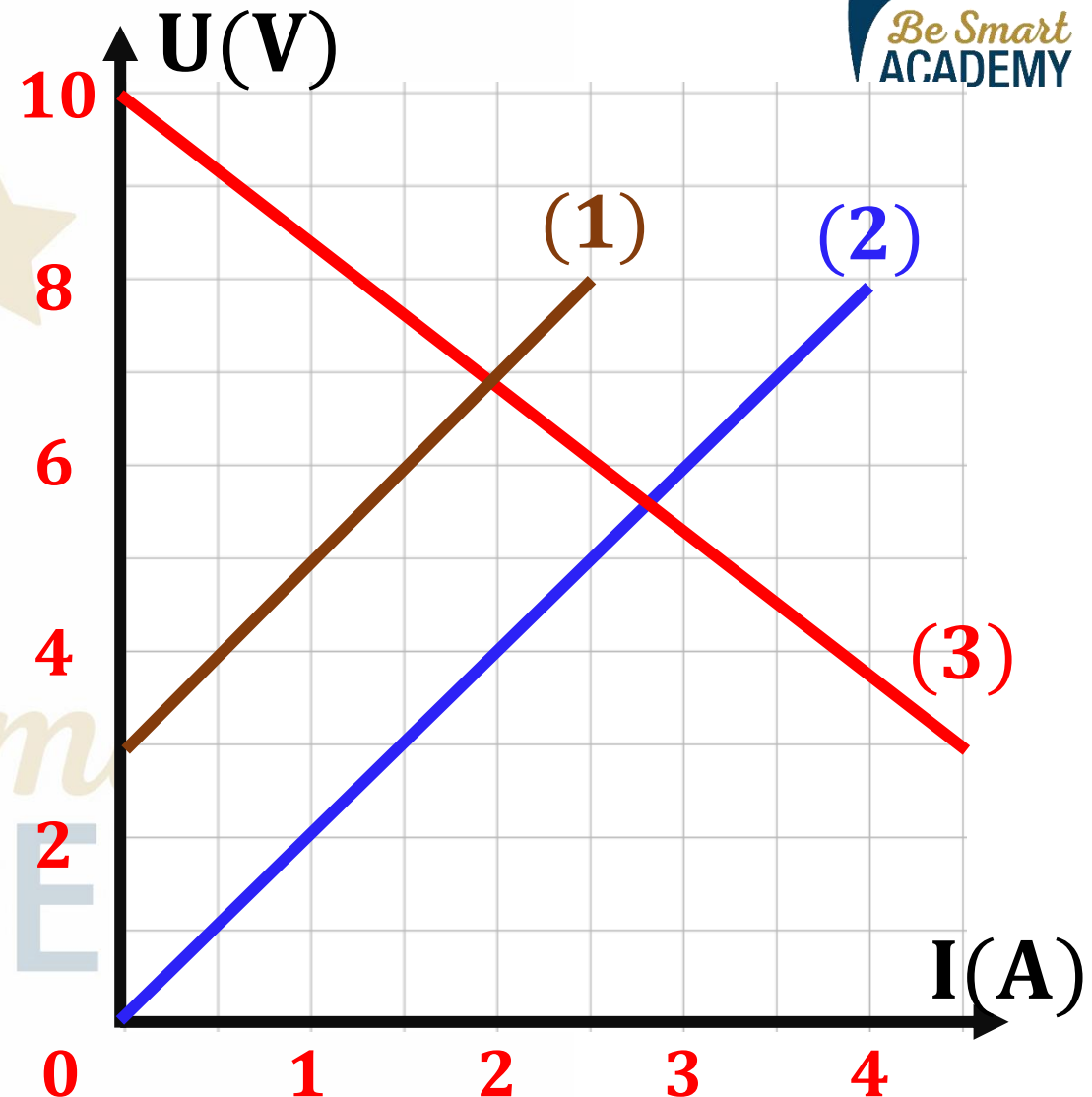


Exercise 3:



1. Referring to graph, associate to each dipole its corresponding graph.


Curve (1): refers to the motor M; because its curve is a straight line of **positive slope** and **NOT** passing through origin.

Curve (2): refers to the Resistor; because its curve is a **straight line** **passing through origin**.

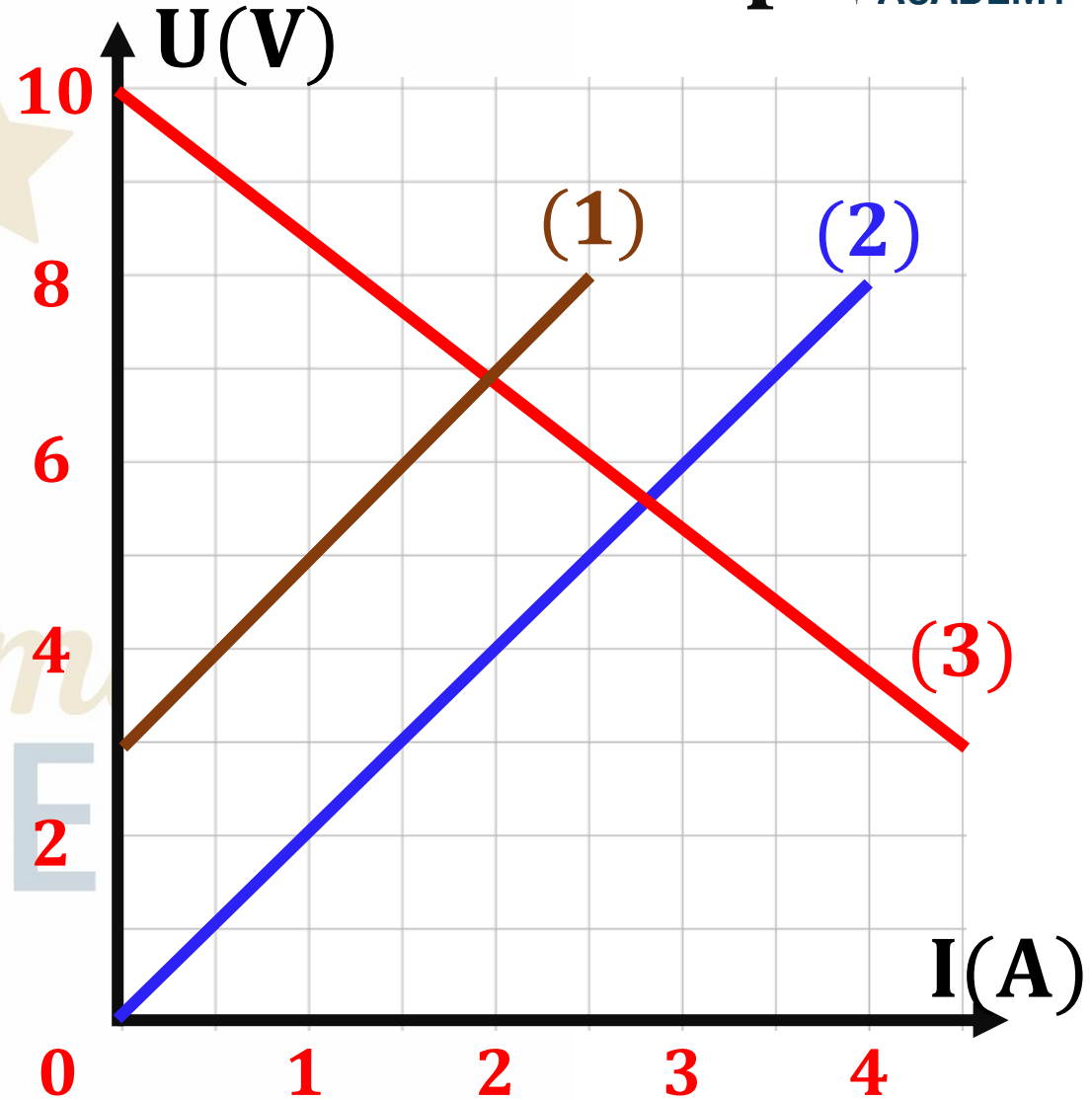

Exercise 3:

Curve (3): refers to the generator G; because its curve is a **straight line of negative slope** and **NOT** passing through origin.

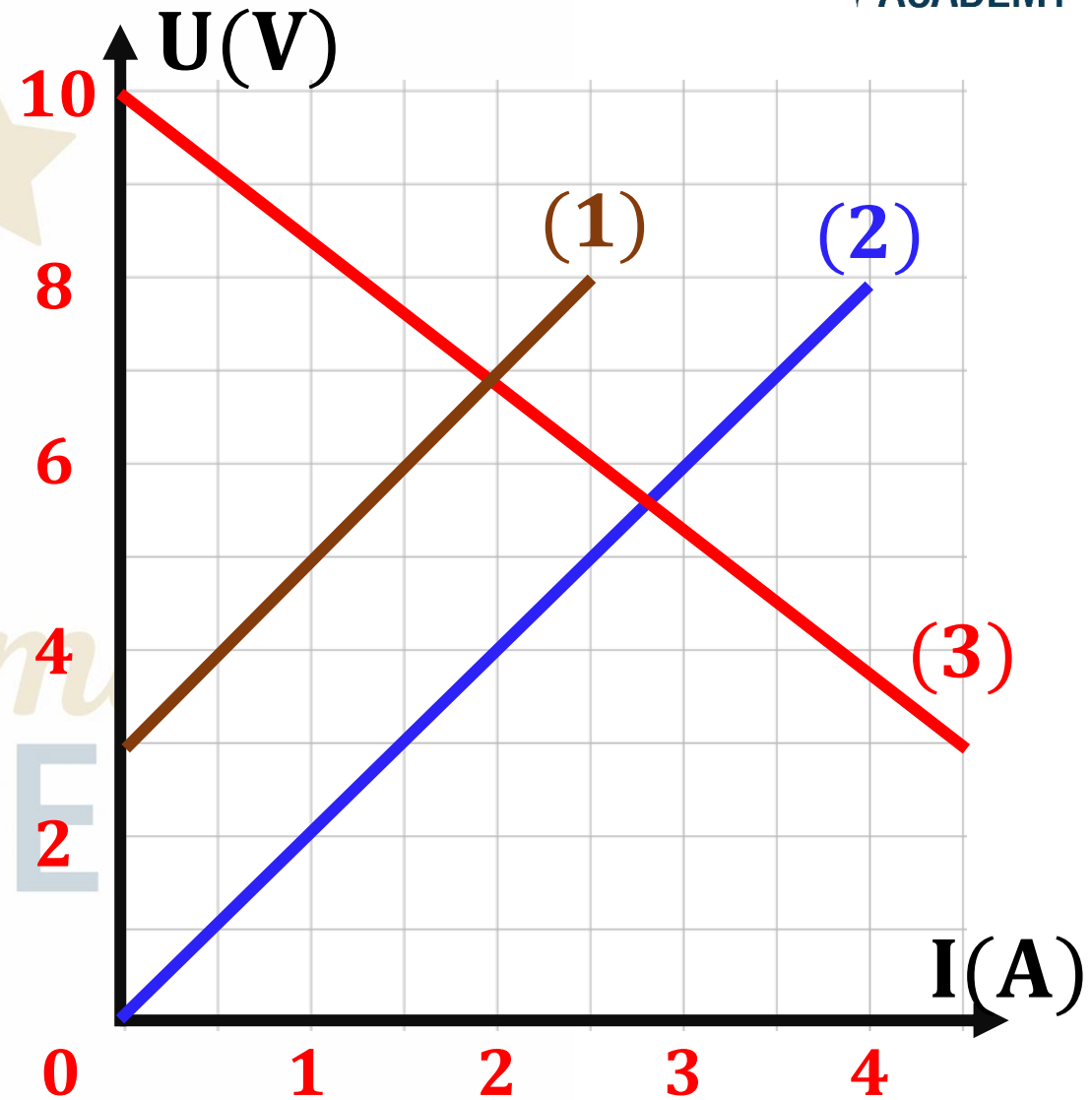

Exercise 3:



2. Using the graph, determine the characteristic constants of each dipole.


Curve (1) is for receiver:

Its equation is $U_M = a \cdot I + b$

Where a is slope ($a = r'$ and $b = E'$ is y-intercept

$$r' = a = \frac{U_2 - U_1}{I_2 - I_1} = \frac{8 - 4}{2.5 - 0.5}$$

$$r' = 2\Omega$$

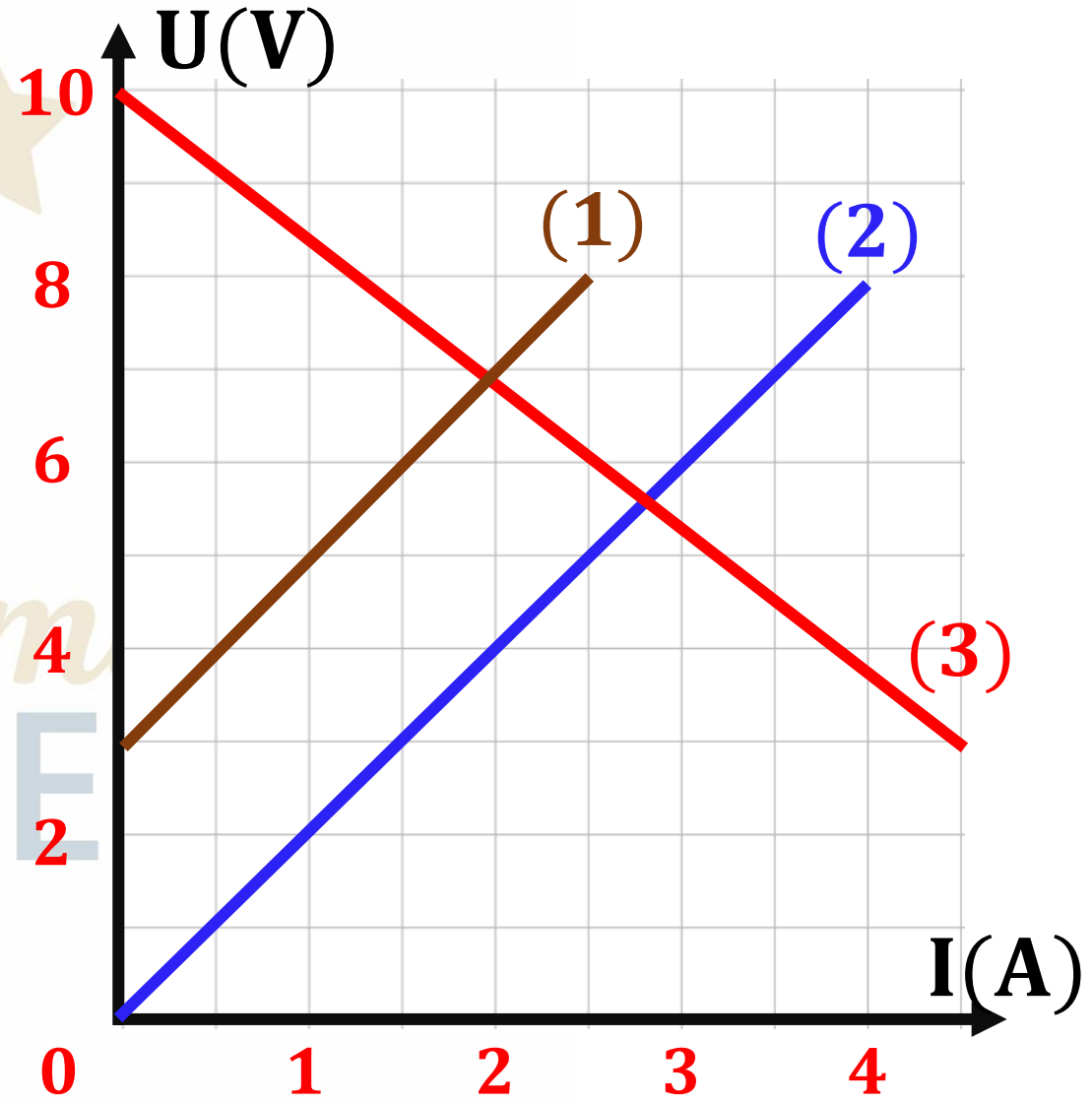

Exercise 3:



b: is y-intercept

$$b = E' = 3V$$


Curve (2) is for resistor:

Its equation is $U_R = R \cdot I$

Where a is slope ($a = R$):

$$R = a = \frac{U_2 - U_1}{I_2 - I_1} = \frac{8 - 0}{4 - 0}$$

$$R = 2\Omega$$

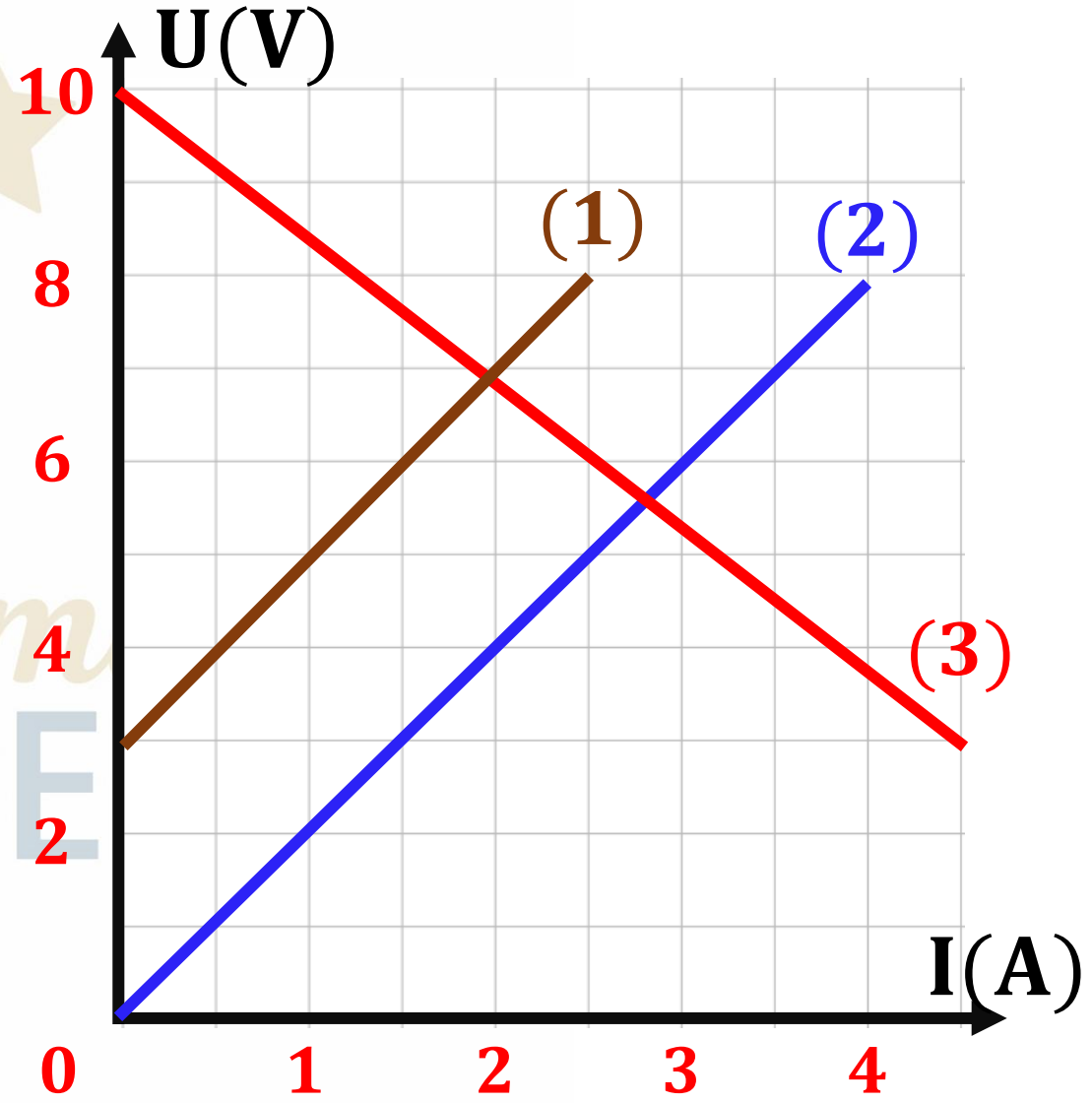

Exercise 3:



Curve (3) is for generator:

Its equation is $U_G = a \cdot I + b$


Where a is slope ($r = a$, and $b = E$ is y-intercept):

$$r = a = \frac{U_2 - U_1}{I_2 - I_1} = \frac{10 - 3}{0 - 4.5}$$

$$r = 1.55\Omega$$

$b = E$ is y-intercept

$$b = E = 10V$$

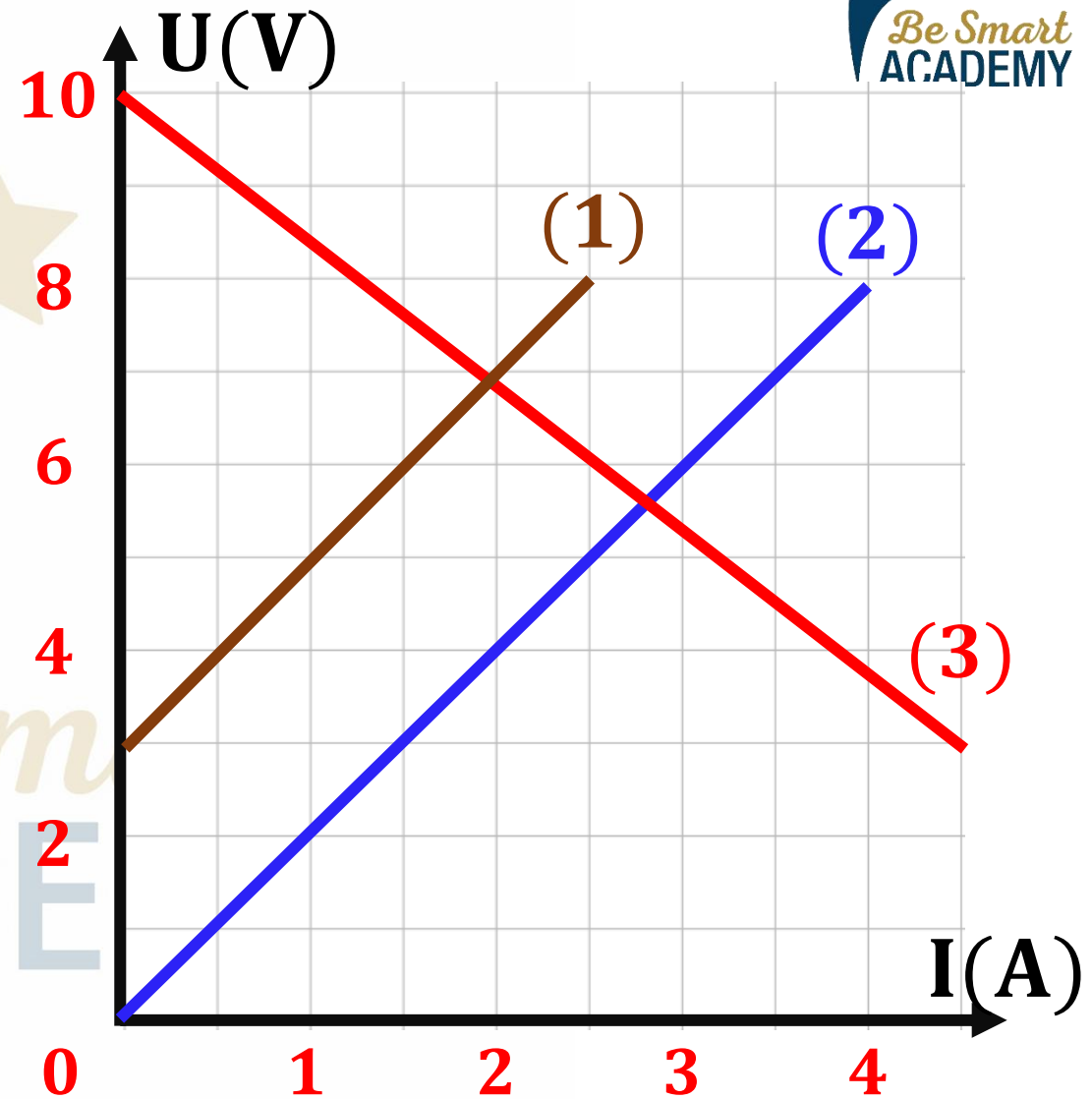

Exercise 3:


M ($E' = 3V$; $r' = 2\Omega$); G ($E = 10V$, $r = 1.55\Omega$); $R = 2\Omega$.



3. The motor M is connected across the generator G as shown. in the figure.

Determine, when possible, the current through the circuit, and the voltage across the motor.

$$\begin{aligned}U_G &= U_M \\-r \cdot I + E &= r' I + E' \\-1.55 \times I + 10 &= 2 \times I + 3 \\10 - 3 &= 2 \times I + 1.55 \times I\end{aligned}$$

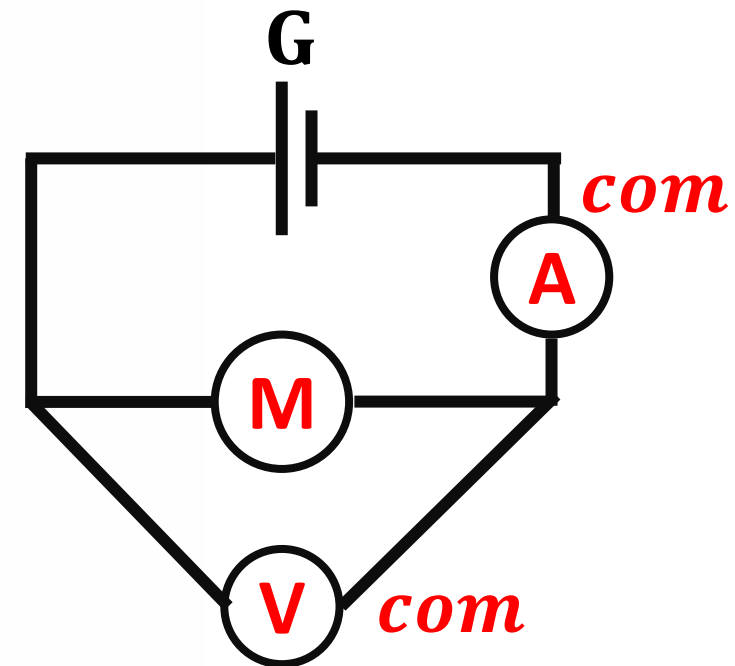


Exercise 3:

$$10 - 3 = 2 \times I + 1.55 \times I$$


$$7 = 3.55 \times I$$

$$I = \frac{7}{3.55}$$

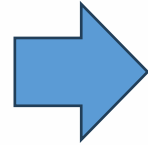

$$I = 1.97A$$

$$U_M = r'I + E'$$

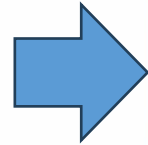

$$U_M = 2 \times 1.97 + 3$$

$$U_M = 6.94V$$

