


Physics – Grade 10

Unit One – Electricity



Chapter 5 Generator and Receiver

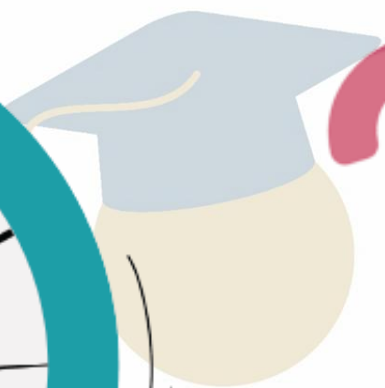Prepared & Presented by: **Mr. Mohamad Seif**



Be Smart
ACADEMY



Quiz 1


physics

Duration: 20 min



Given $G_1(48V; 2\Omega)$, $G_2(12V; 1\Omega)$, a motor $M(E'; r')$; and a rheostat R_h , an ammeter and a voltmeter and connected as shown.

1. Specify the role of G_1 and G_2 in the circuit.
2. For $R_h = 4\Omega$, the ammeter indicates 3 A. Determine the voltages across G_1 , G_2 and R_h .
3. Deduce the voltage U_M across the motor.
4. Find a relation between E' and r' .

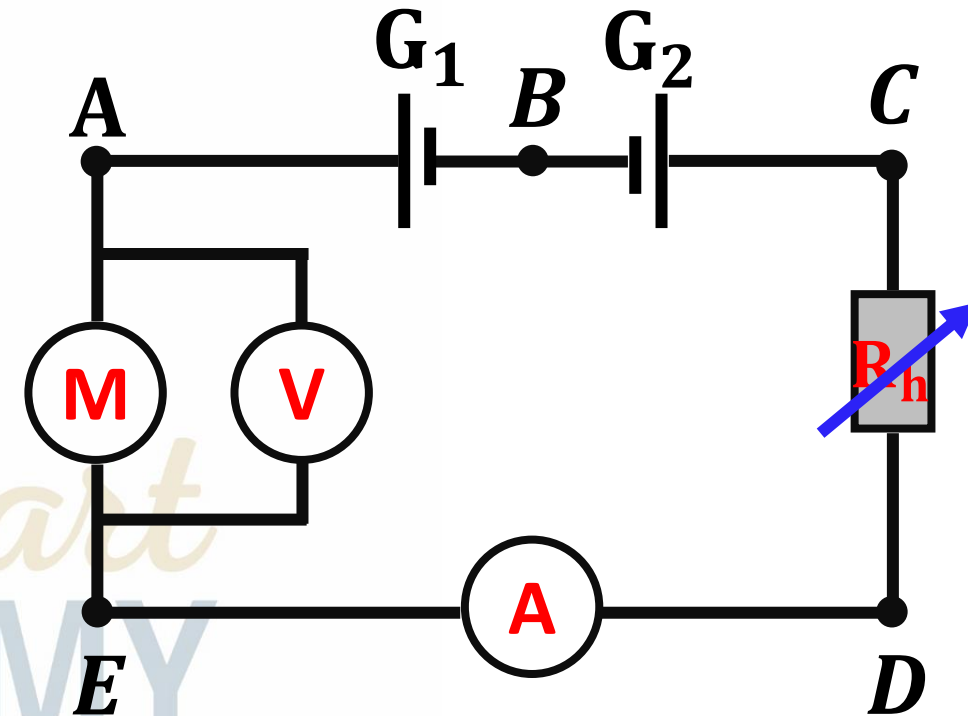

Quiz 1

physics

Duration: 20 min




$G_1(48V; 2\Omega)$; $G_2(12V; 1\Omega)$; $M(E'; r')$; and R_h .

1. Specify the role of G_1 and G_2 in the circuit.

The negative pole of G_1 is connected to negative pole of G_2 (connected in opposition):

G_1 acts as a generator and G_2 acts as receiver.

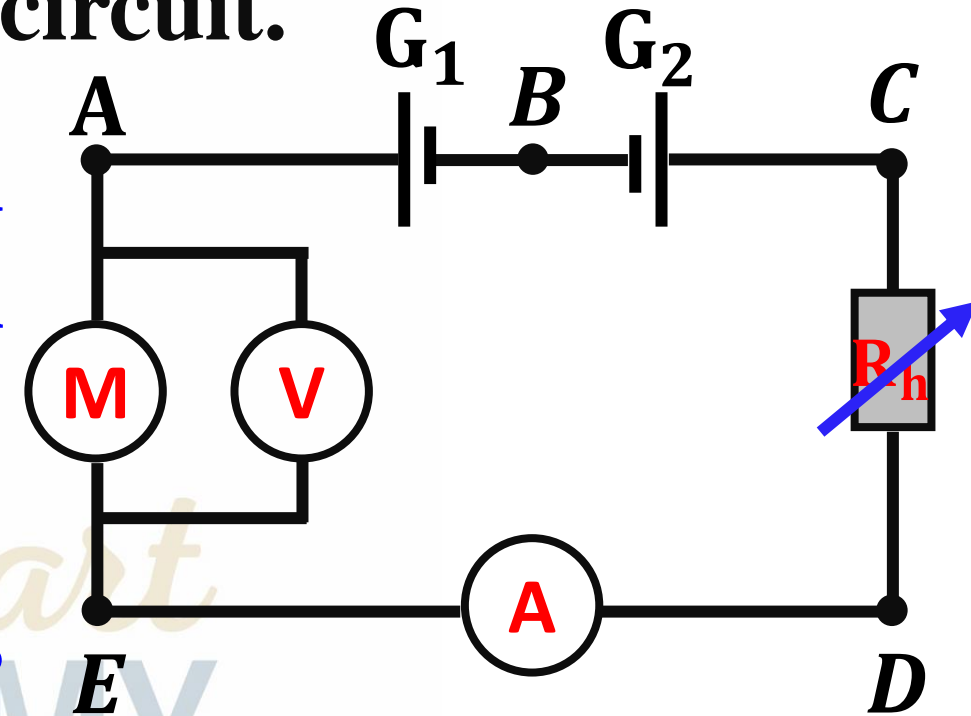

Quiz 1

physics

Duration: 20 min



$G_1(48V; 2\Omega); G_2(12V; 1\Omega); M(E'; r'); \text{ and } R_h.$

For $R_h = 4\Omega$, the ammeter indicates 3 A.

2. Determine the voltages across G_1 , G_2 and R_h .


$$U_{G1} = -rI + E$$

$$U_{G1} = -2 \times 3 + 48 \Rightarrow U_{G1} = 42V$$

$$U_{G2} = r'I + E'$$

$$U_{G2} = 1 \times 3 + 12 \Rightarrow U_{G2} = 15V$$

$$U_{Rh} = R_h \times I \Rightarrow U_{Rh} = 4 \times 3 \Rightarrow U_{Rh} = 12V$$

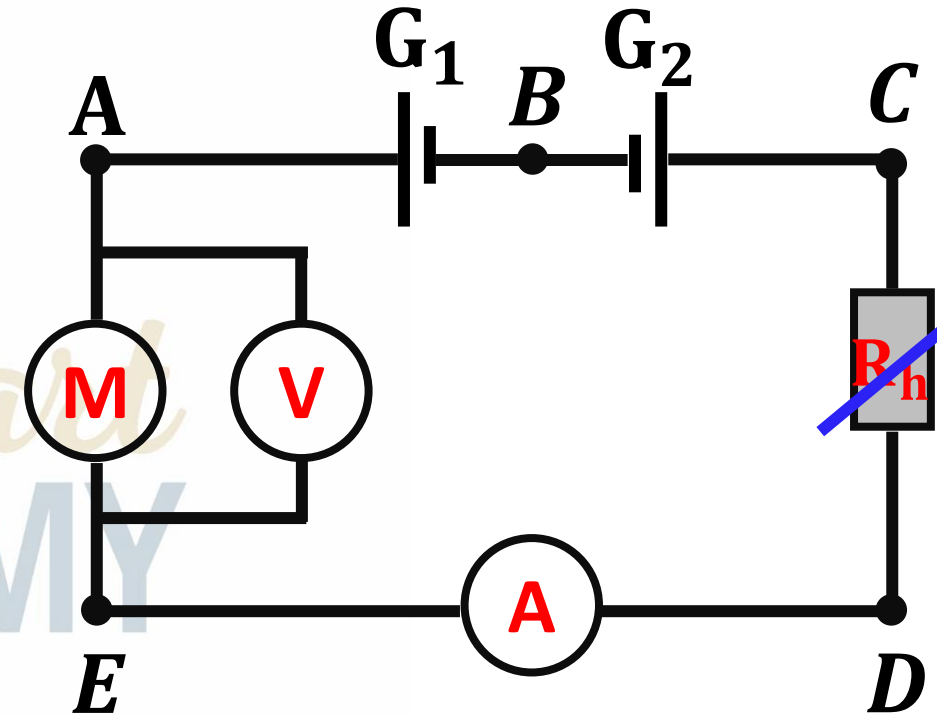

Quiz 1

physics

Duration: 20 min



$G_1(48V; 2\Omega)$; $G_2(12V; 1\Omega)$; $M(E'; r')$; and R_h .


3. Deduce the voltage U_M across the motor.

Using law of addition of voltage in series:

$$U_{G1} = U_M + U_{R_h} + U_{G2}$$

$$42V = U_M + 12V + 15V$$

$$U_M = 15V$$

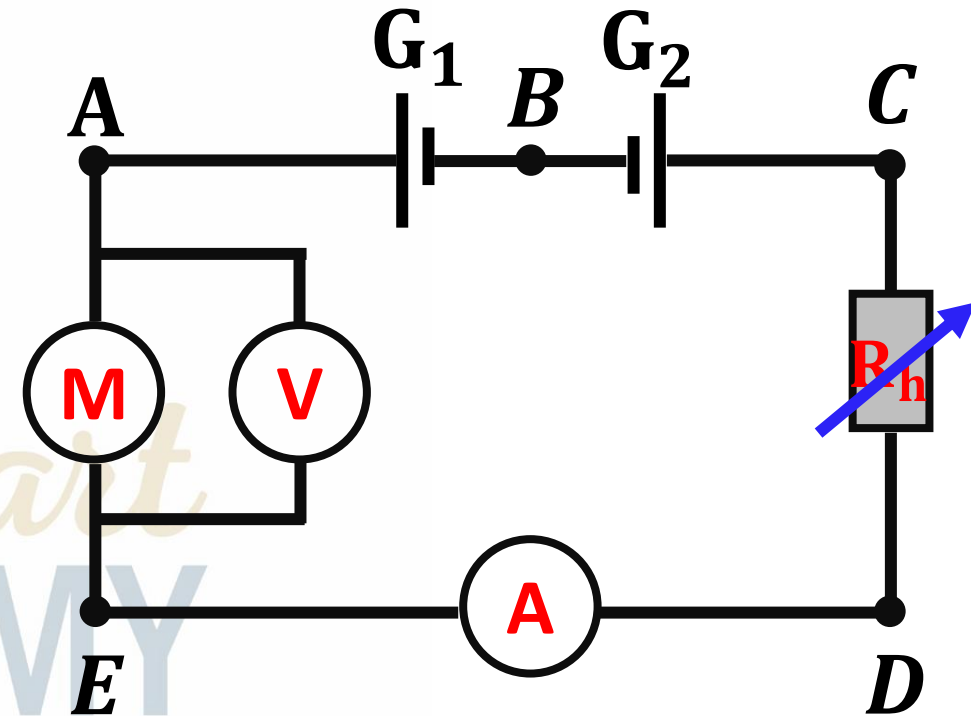

Quiz 1

physics

Duration: 20 min



$G_1(48V; 2\Omega); G_2(12V; 1\Omega); M(E'; r'); \text{ and } R_h.$


4. Find a relation between E' and r' .

The motor is a receiver then:

Use ohm's law of receiver:

$$U_M = r'I + E'$$

$$15V = 3 \times r' + E' \dots \dots (1)$$

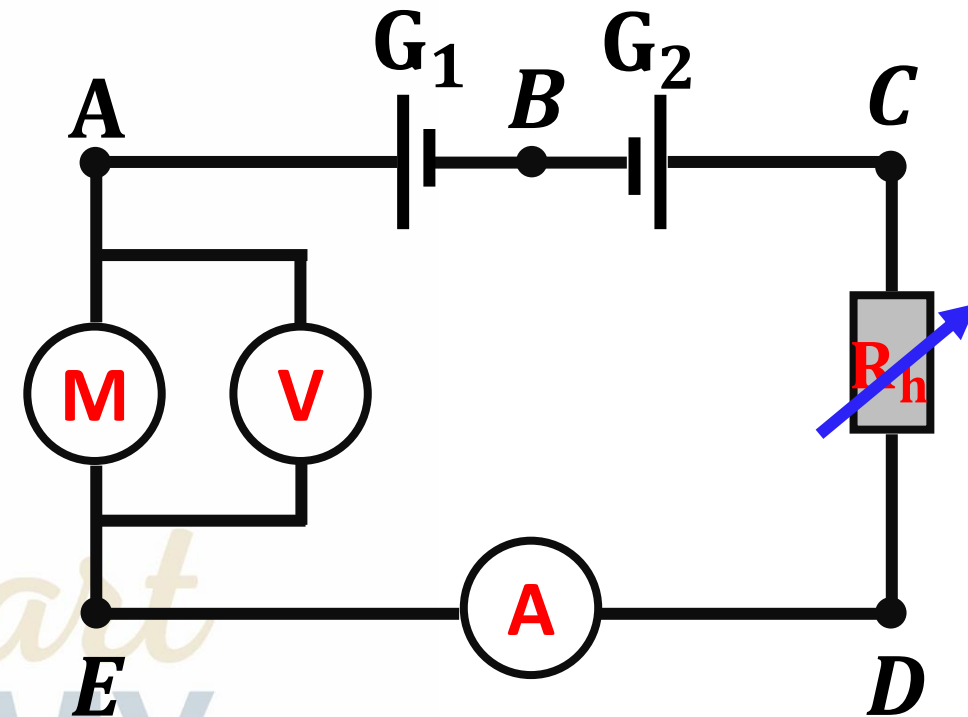

Quiz 1


physics

Duration: 20 min



5. For $R_h = 8\Omega$, the ammeter indicates 2 A, and the voltmeter indicates 14 V.

- a) Determine a relation between E' and r' .
- b) Determine the back e.m.f. (E') and the internal resistance (r') of the motor.
- c) Does the motor functions normally? Justify your answer.

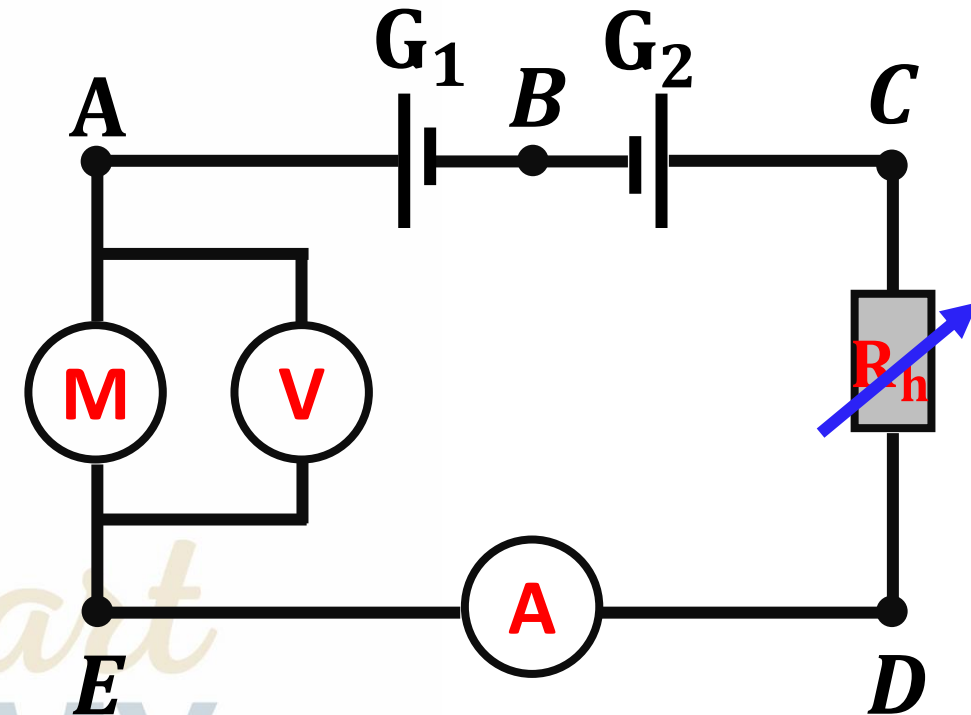

Quiz 1

physics

Duration: 20 min



$G_1(48V; 2\Omega); G_2(12V; 1\Omega); M(E'; r'); \text{ and } R_h.$


5. For $R_h = 8\Omega$, $I = 2\text{ A}$, $U_M = 14V$.

a) Determine a relation between E' and r' .

Using ohm's law of receiver:

$$U_M = r'I + E'$$

$$14V = 2 \times r' + E' \dots \dots (2)$$

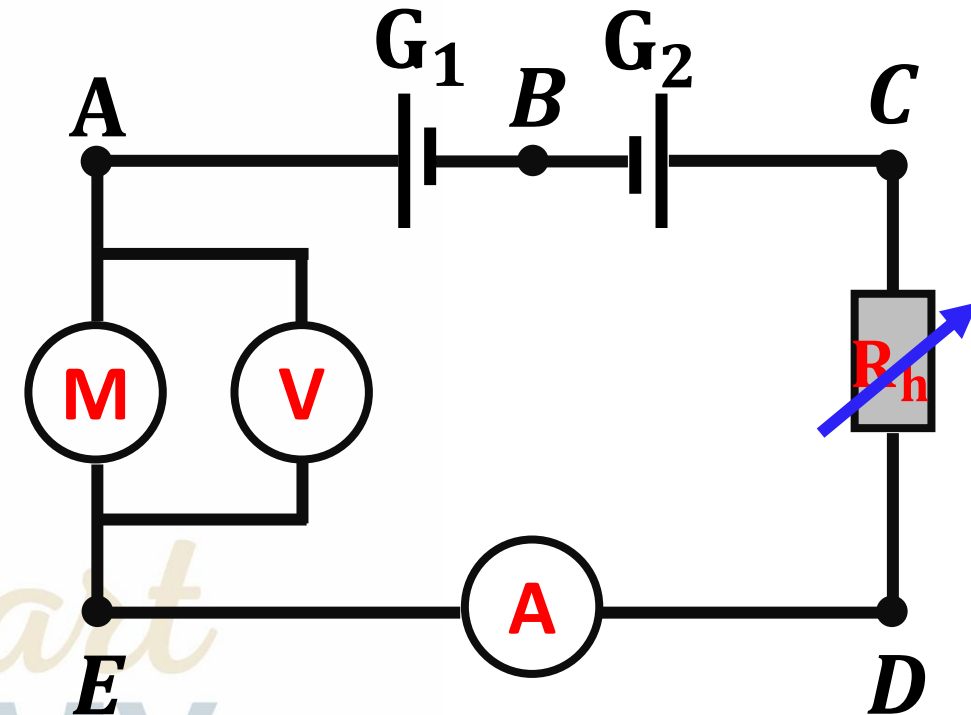

Quiz 1

physics

Duration: 20 min




$G_1(48V; 2\Omega); G_2(12V; 1\Omega); M(E'; r'); \text{ and } R_h.$

6. Determine the back e.m.f. (E') and the internal resistance (r') of the motor.

$$\begin{cases} 15V = 3r' + E' \dots\dots (1) \\ 14V = 2r' + E' \dots\dots (2) \quad (-1) \end{cases}$$

$$\begin{cases} 15V = 3 \times r' + E' \\ -14V = -2 \times r' - E' \end{cases}$$

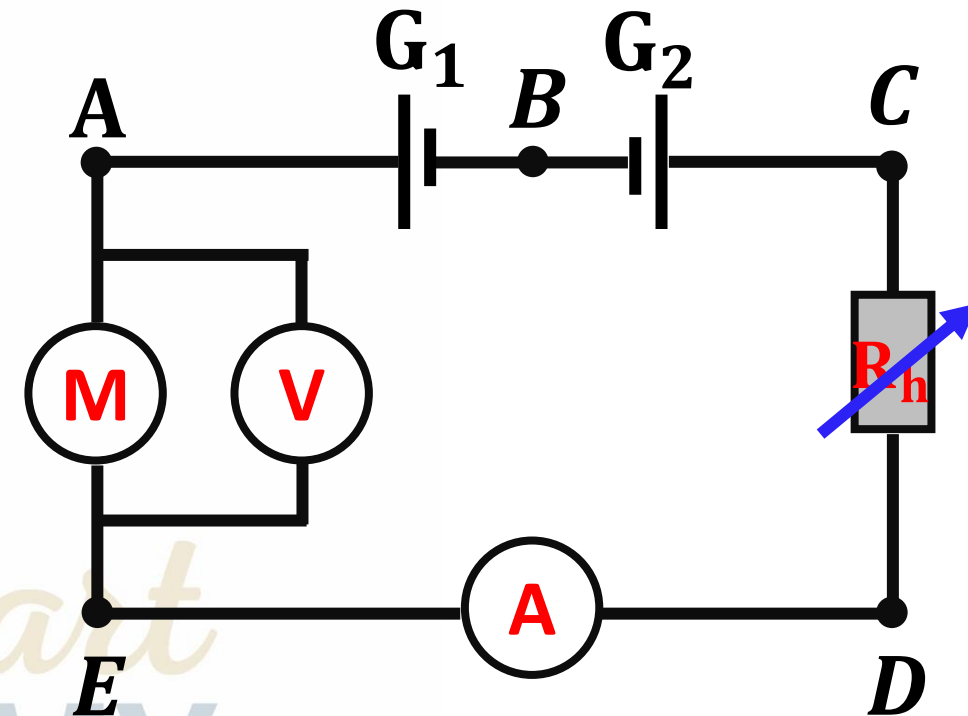

Quiz 1

physics

Duration: 20 min



$$\begin{cases} 15V = 3 \times r' + E' \\ -14V = -2 \times r' - E' \end{cases}$$

Add the above two equations:

$$15V - 14V = 3r' + \cancel{E'} - 2r' - \cancel{E'}$$

$$1 = r'$$

$$r' = 1\Omega$$

Substitute $r' = 1\Omega$ in any of the above equations:

$$15V = 3 \times (1) + E'$$


$$15V = 3 + E'$$


$$15 - 3 = E'$$

$$15V = 3 \times r' + E'$$

$$E' = 12V$$

The End

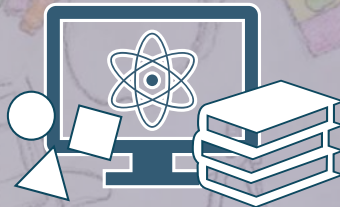

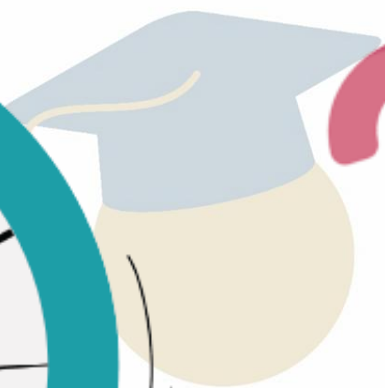

Be Smart
ACADEMY




Quiz 2

physics

Duration: 15 min



To know the nature of two electric loads D_1 and D_2 we connect them in series with DC generator of electromotive force E and internal resistance $r = 2\Omega$.

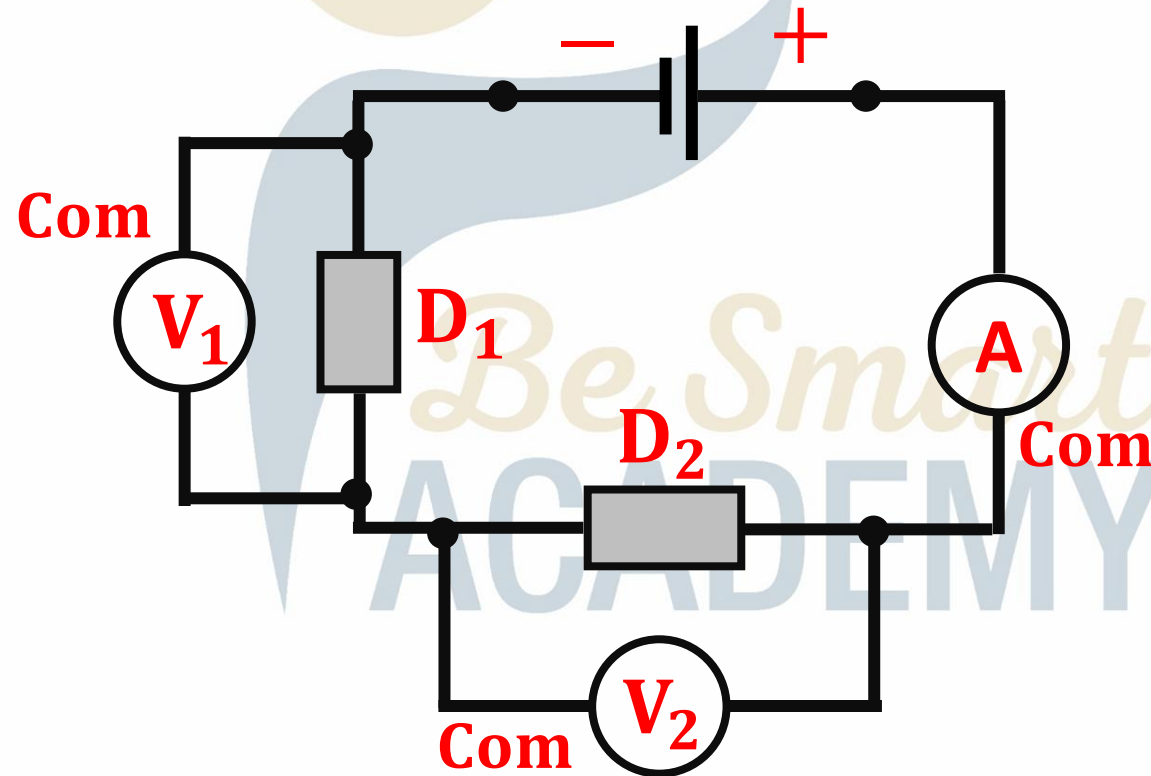

Quiz 2

physics

Duration: 15 min



Two voltmeters V_1 and V_2 are connected across the terminals of D1 and D2 and an ammeter A is connected as shown in the figure. The table below represents the readings of V_1 , V_2 and A.

I (mA)	0	100	200	300	400
V_1 (V)	0	1	2	3	4
V_2 (V)	2.5	3	3.5	4	4.5

Quiz 2

physics

Duration: 15 min



1. Trace the I-V characteristic curves of the two electric loads D_1 , and D_2 .

Scale: x – axis: $1\text{cm} \rightarrow 0.1\text{A}$ & y – axis: $1\text{cm} \rightarrow 1\text{V}$

2. Indicate with justification the nature of the electric loads D_1 , and D_2 .

3. Find the equations of the two graphs that correspond to D_1 , and D_2 .

4. Deduce the characteristics of D_1 , and D_2 .

5. For $I = 0.3\text{A}$. Determine, by applying the law of addition of voltages, the value of E of the generator.

Quiz 2


physics

Duration: 15 min



1. Trace the I-V characteristic curves of the two electric loads D_1 and D_2

I (mA)	0	100	200	300	400
V_1 (V)	0	1	2	3	4
V_2 (V)	2.5	3	3.5	4	4.5

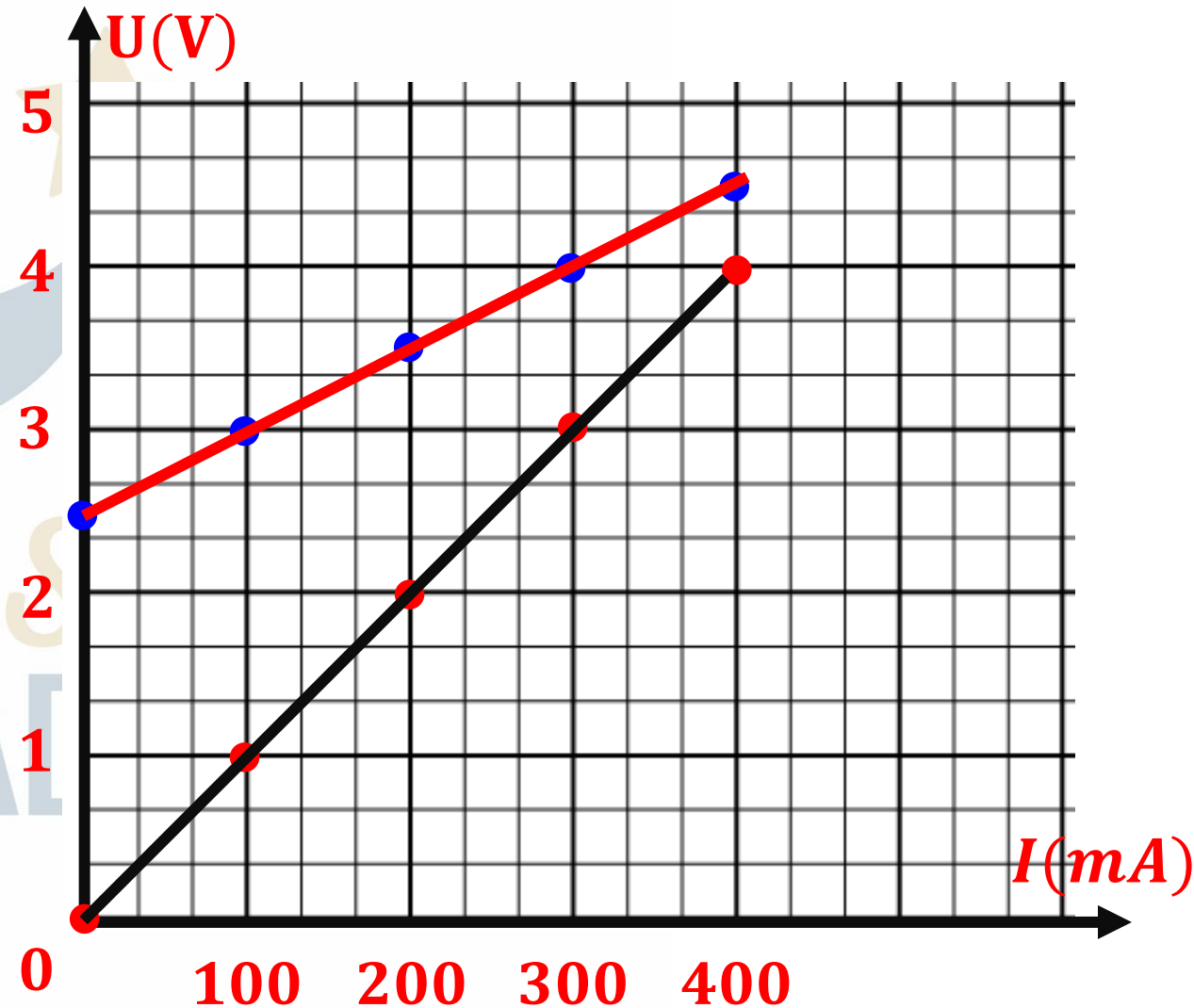

2. Indicate with justification the nature of the electric loads D_1 , and D_2 .

D_1 is a resistor, since the shape of its graph is a straight line passing through the origin.

D_2 is a receiver, since the shape of its graph is an increasing straight line and NOT passing by origin.

Quiz 2

physics

Duration: 15 min



3. Find the equations of the two graphs that correspond to D_1 , and D_2


For D_1 : The equation is:
 $U = aI$; where a is slope.

$$a = \frac{U_2 - U_1}{I_2 - I_1} = \frac{2 - 1}{0.2 - 0.1}$$

$$a = 10V / A$$

The equation is:

$$U = 10I$$

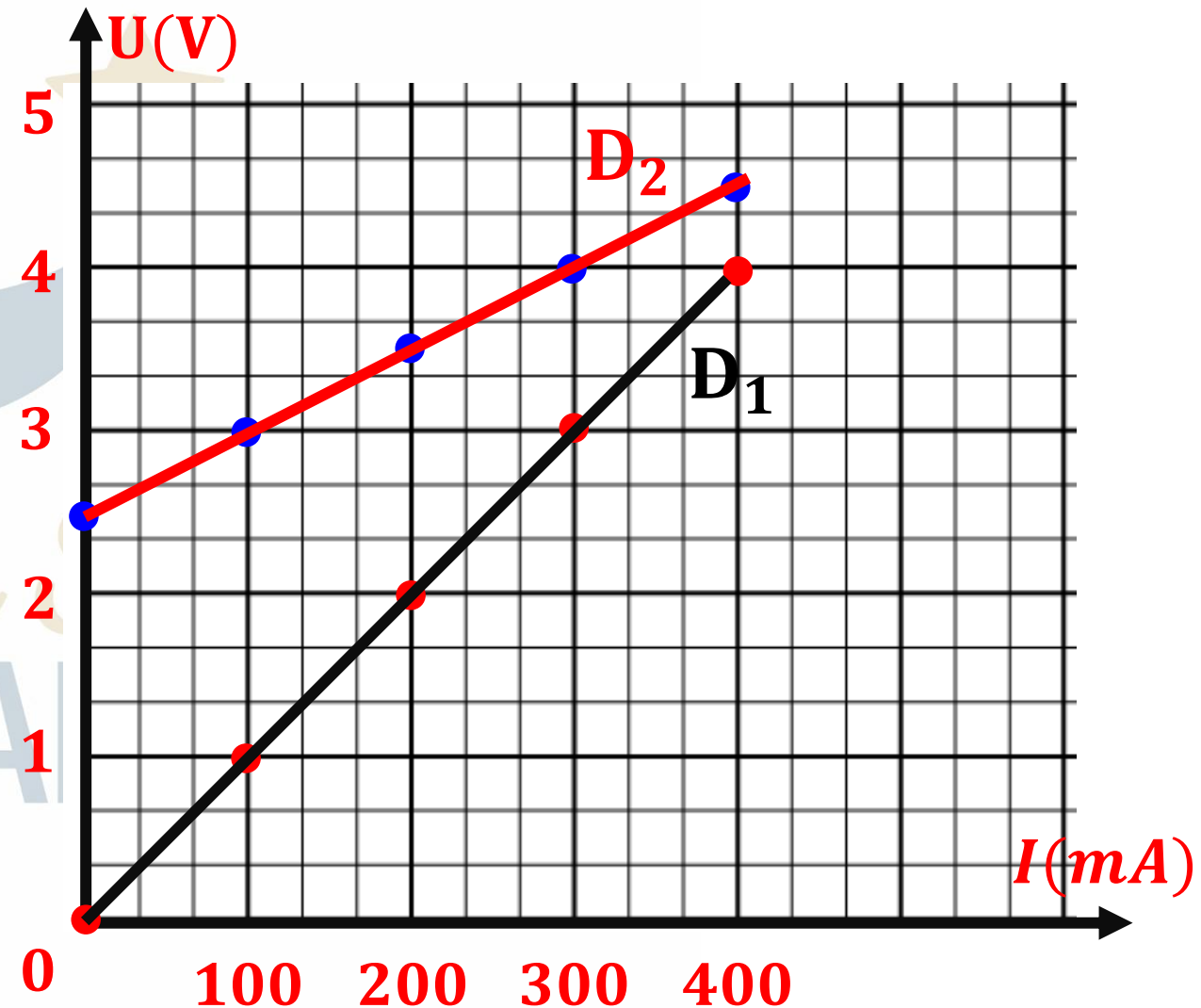

Quiz 2

physics

Duration: 15 min



For D_2 : The general equation is $U = a \cdot I + b$; with k is slope

$$a = \frac{U_2 - U_1}{I_2 - I_1} = \frac{4.5 - 4}{0.2 - 0.1}$$


$$a = 5V / A$$

b is y- intercept

$$b = 2.5V$$

The equation is:

$$U = 5 \cdot I + 2.5$$

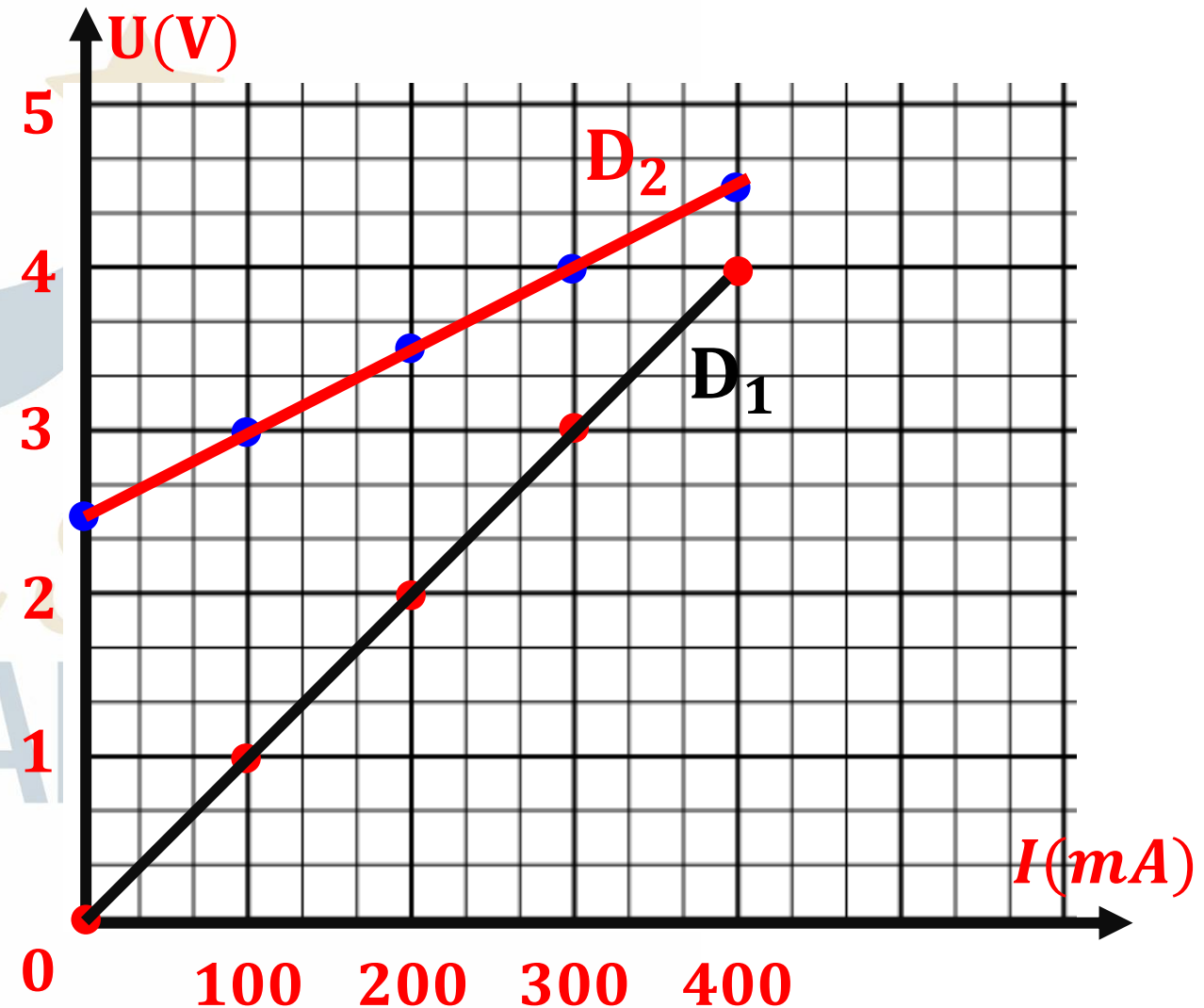

4. Deduce the characteristics values of D_1 , and D_2 .

D_1 is resistor with equation:

$$U = 10I$$

The ohm's law of resistor is

$$U = R.I$$

Compare the two equations:

$$R = 10\Omega$$

D_2 is a receiver with equation:

$$U = 5.I + 2.5$$

The ohm's law of receiver is

$$U = r'.I + E'$$

Compare the two equations:

$$r' = 5\Omega$$

$$E' = 2.5\Omega$$

Quiz 2

physics

Duration: 15 min



5. For $I=0.3\text{A}$. Determine, by applying the law of addition of voltages, the value of E of the generator.


$$U_G = U_R + U_M$$

$$-rI + E = RI + r'I + E'$$

$$-2 \times 0.3 + E = 10 \times 0.3 + 5 \times 0.3 + 2.5$$

$$-0.6 + E = 3 + 1.5 + 2.5$$

$$E = 3 + 1.5 + 2.5 + 0.6$$

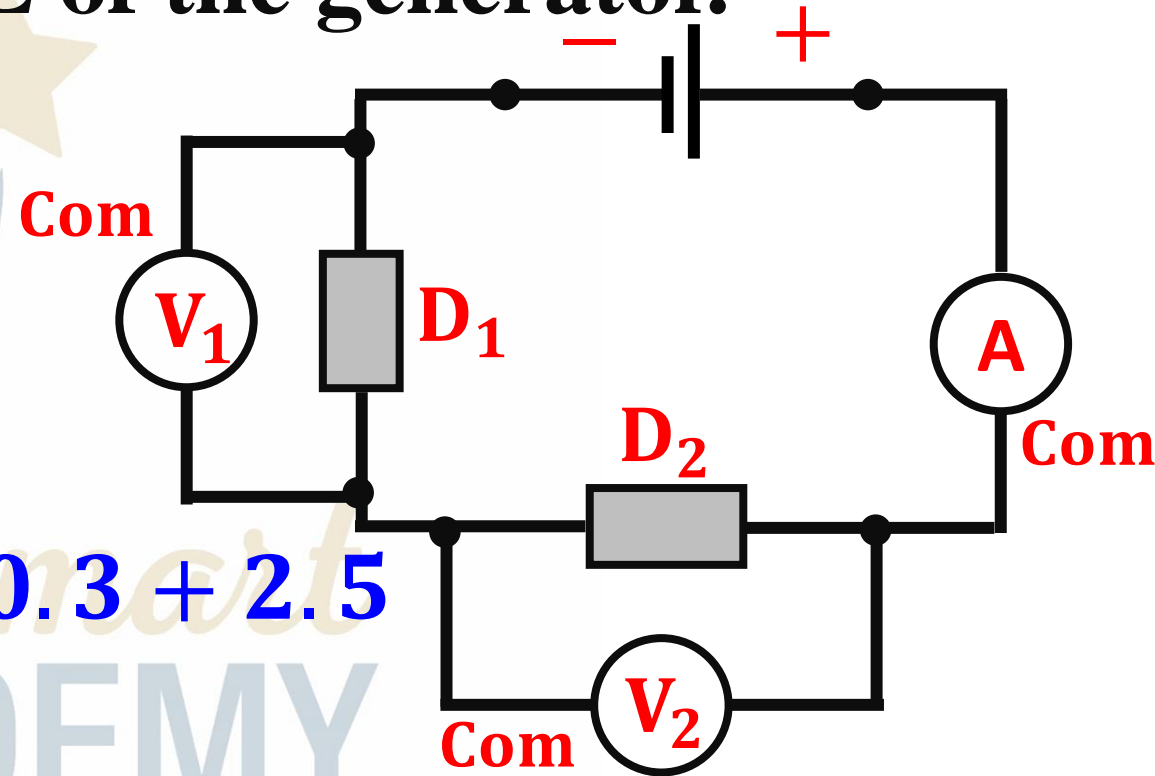

$$E = 7.6\text{V}$$

The End

