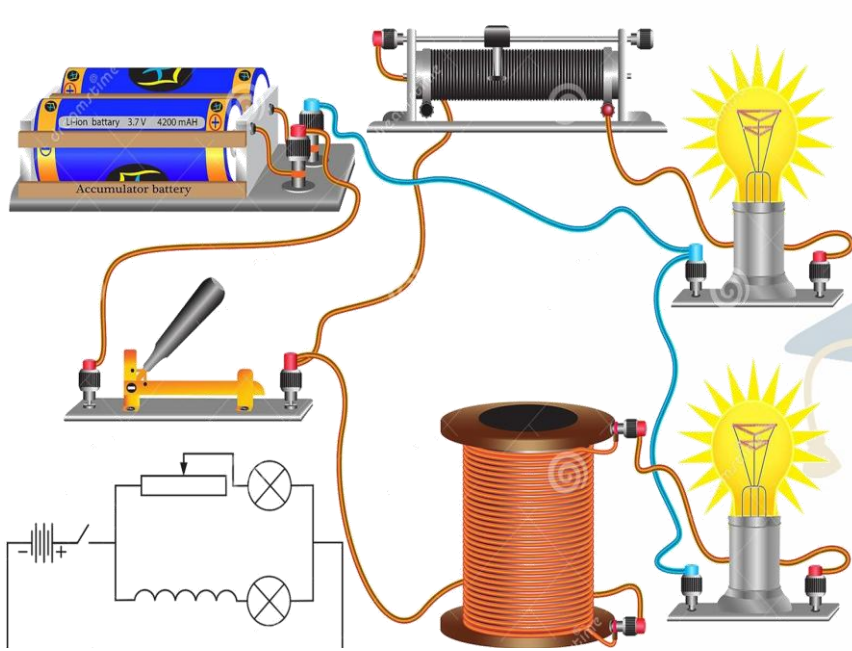



What is Self Induction?



Physics – Grade 12

Unit Two – Electricity

Chapter 9 – Self Induction

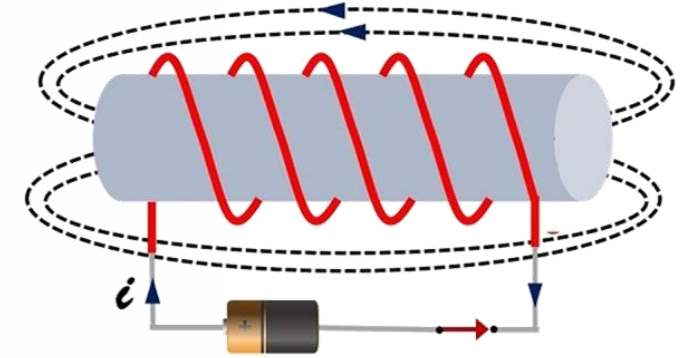


Prepared & Presented by: **Mr. Mohamad Seif**


PROBLEM SOLVING



problem

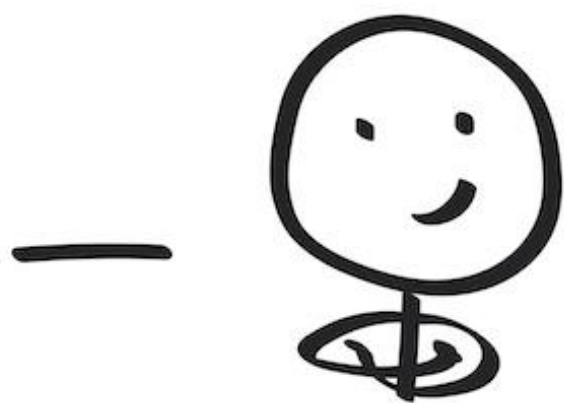

thinking

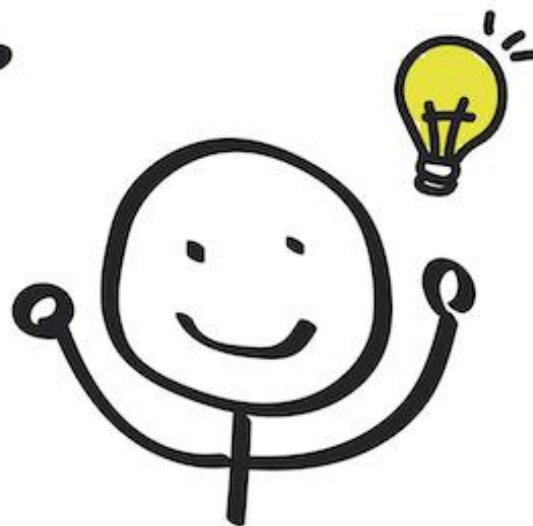


solution

Exercise 1

To determine the characteristics of a coil, we set up the circuit of the adjacent figure which is formed of the coil (L , r), a resistor of resistance $R = 2.5\Omega$, a generator of constant emf $E = 6\text{ V}$ and of negligible resistance and a switch K .

At the instant $t_0 = 0$, we close the switch K .

At an instant t , the circuit carries a current i .

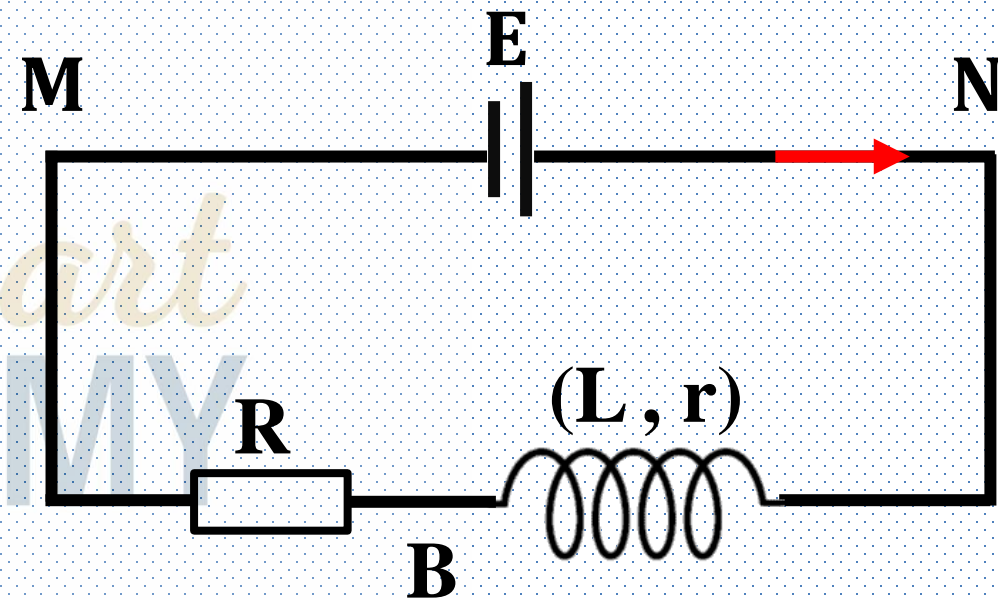

Exercise 1

- 1) Derive the differential equation describing the variations of i as a function, of time.
- 2) The solution of this equation is of the form $i = I_0(1 - e^{-\frac{t}{\tau}})$, where I_0 and τ are constants.
Determine, in terms of E , R_{eq} and L , the expressions of I_0 and τ .
- 3) Give, as a function of time, the expression of the voltage u_{MB} .

Exercise 1

1) Derive the differential equation describing the variations of i as a function, of time.


Apply law of addition of voltages:

$$u_{NM} = u_{NB} + u_{BM}$$

$$E = ri + L \frac{di}{dt} + Ri$$

$$E = (R + r)i + L \frac{di}{dt}$$

Where $R_{eq} = (R + r)$

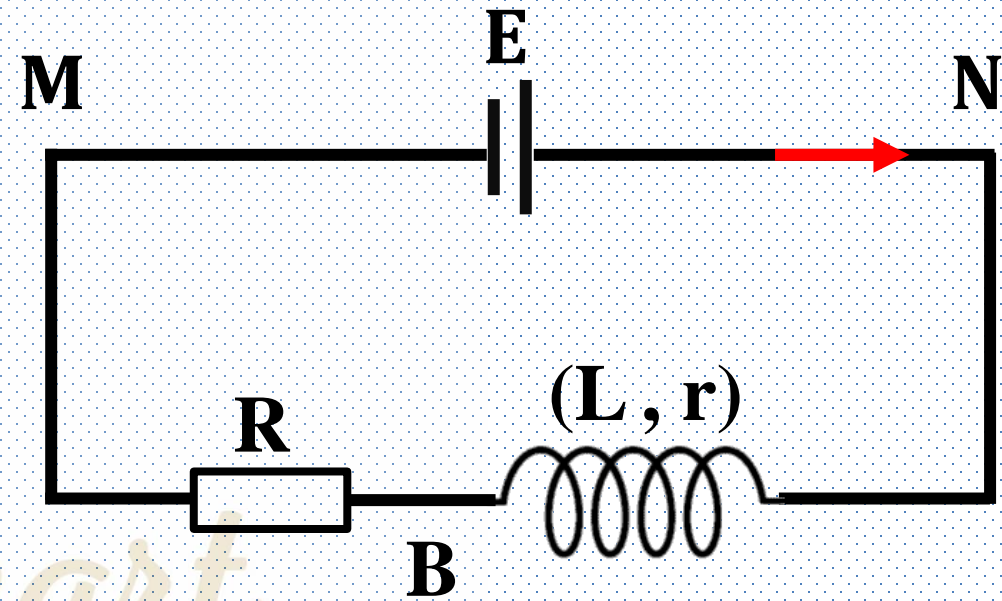

Differential equation in terms of current i

Exercise 1

2) The solution of this equation is of the form $i = I_0(1 - e^{-\frac{t}{\tau}})$, where I_0 and τ are constants. Determine, in terms of the given, the expressions of I_0 and τ .

$$E = R_{eq}i + L \frac{di}{dt}$$

$$i = I_0(1 - e^{-\frac{t}{\tau}})$$

$$\frac{di}{dt} = \frac{I_0}{\tau} \cdot e^{-\frac{t}{\tau}}$$

Substitute i and $\frac{di}{dt}$ in differential equation.

$$E = R_{eq}I_0(1 - e^{-\frac{t}{\tau}}) + L \cdot \frac{I_0}{\tau} \cdot e^{-\frac{t}{\tau}}$$

Exercise 1

$$E = R_{eq}I_0 - R_{eq}I_0e^{-\frac{t}{\tau}} + \frac{LI_0}{\tau} \cdot e^{-\frac{t}{\tau}}$$
$$E + R_{eq}I_0e^{-\frac{t}{\tau}} = R_{eq}I_0 + \frac{LI_0}{\tau} \cdot e^{-\frac{t}{\tau}}$$

By identification we get:

$$E = R_{eq}I_0$$

$$R_{eq}I_0 = \frac{LI_0}{\tau}$$



$$I_0 = \frac{E}{R_{eq}}$$



$$\tau = \frac{L}{R_{eq}}$$


Exercise 1

3) Give, as a function of time, the expression of the voltage u_{MB} .

$$u_{MB} = -Ri$$

$$u_{MB} = -R \left[I_0 \left(1 - e^{-\frac{t}{\tau}} \right) \right]$$

$$u_{MB} = -RI_0 \left(1 - e^{-\frac{t}{\tau}} \right)$$

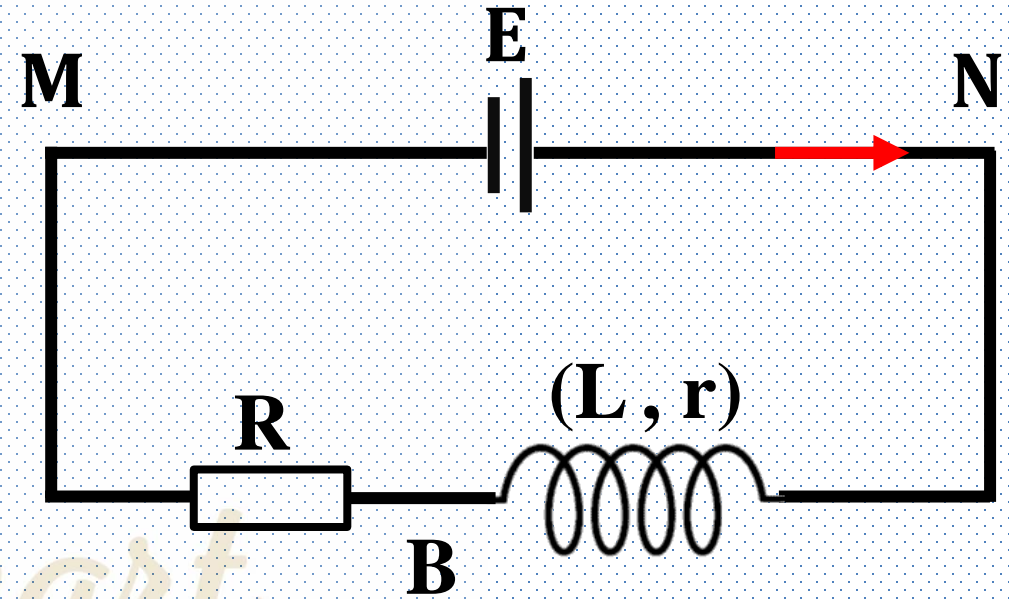


Exercise 1

4) The variations of the voltages u_{NB} and u_{MB} , as a function of time, are given in the adjacent waveform.

a) Specify, with justification, the curve which gives the variations of u_{BM} as a function of time.

b) Determine the value of r and that of I_0 .

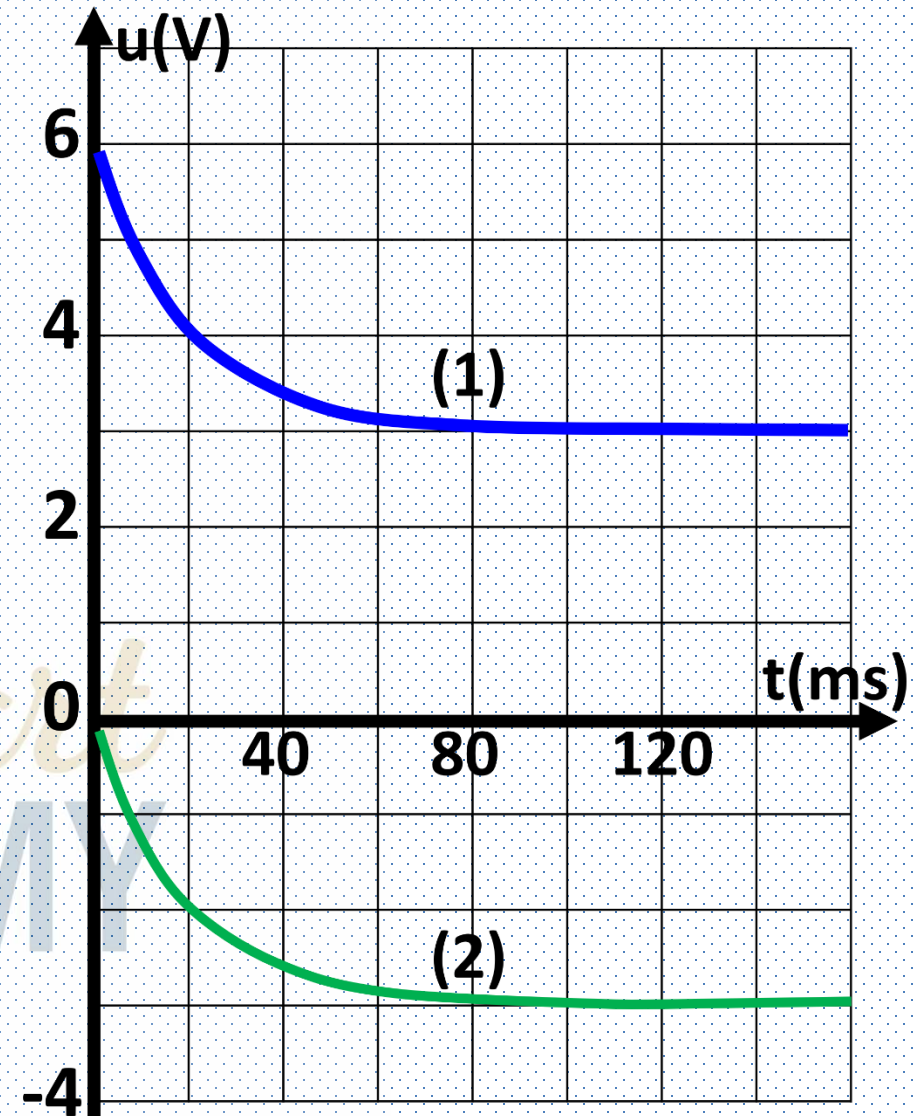


Exercise 1

a) Specify, with justification, the curve which gives the variations of u_{BM} as a function of time.

Curve (2) is for u_{MB} because according to the given circuit

$$u_{MB} = -Ri$$

So, the voltage is negative.

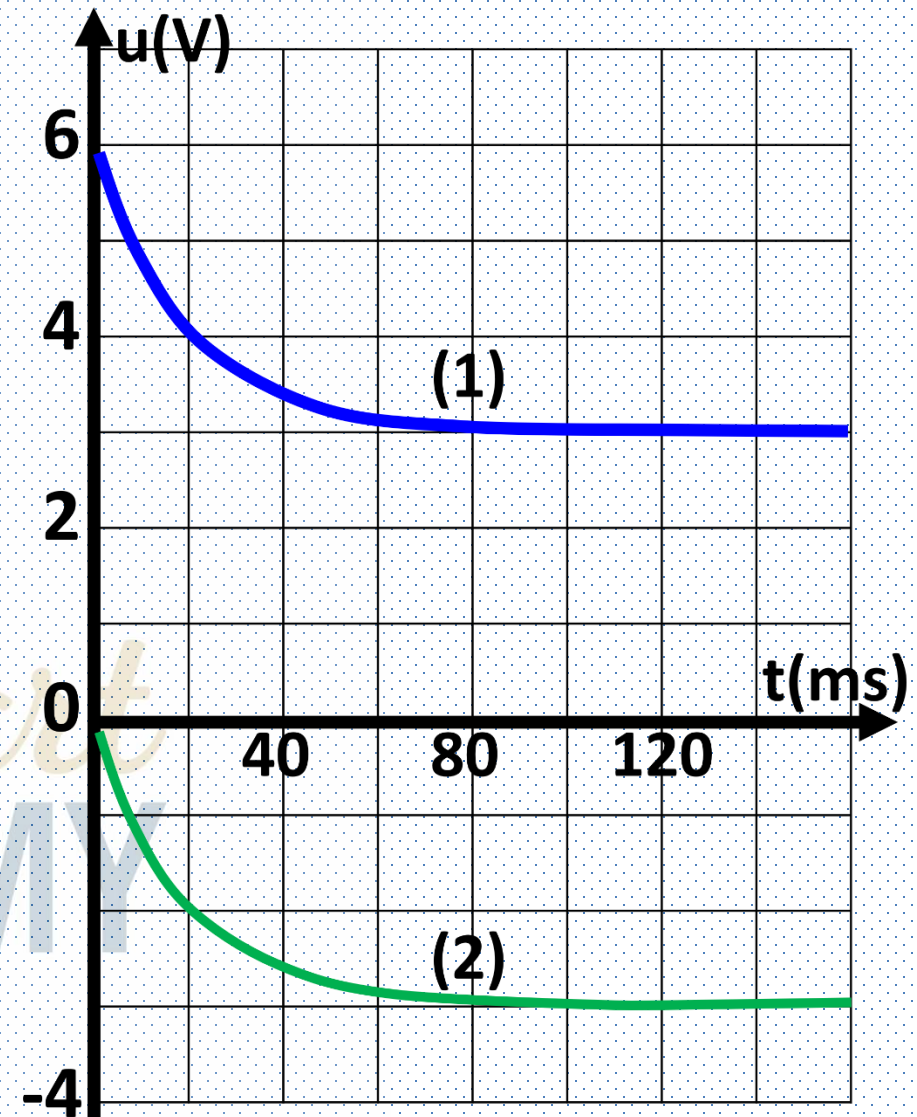

Exercise 1

b) Determine the value of r and that of I_0 .


$$u_{MB} = -Ri$$

$$u_{MB(max)} = -RI_0$$

$$-3 = -2.5I_0$$

$$I_0 = \frac{-3}{-2.5}$$

$$I_0 = 1.2A$$

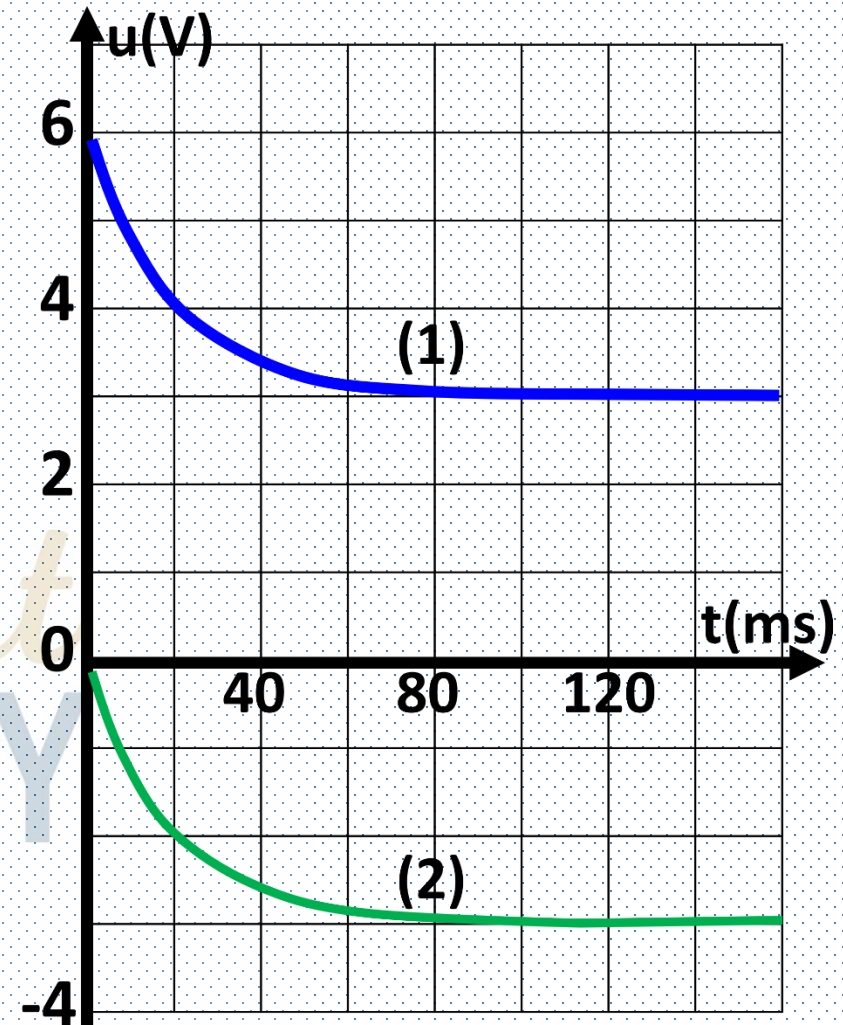

Exercise 1

$$I_0 = \frac{E}{R_{eq}} \Rightarrow I_0 = \frac{E}{R + r}$$


$$1.2 = \frac{6}{2.5 + r}$$

$$2.5 + r = \frac{6}{1.2}$$

$$2.5 + r = 5$$

$$r = 5 - 2.5$$

$$r = 2.5\Omega$$

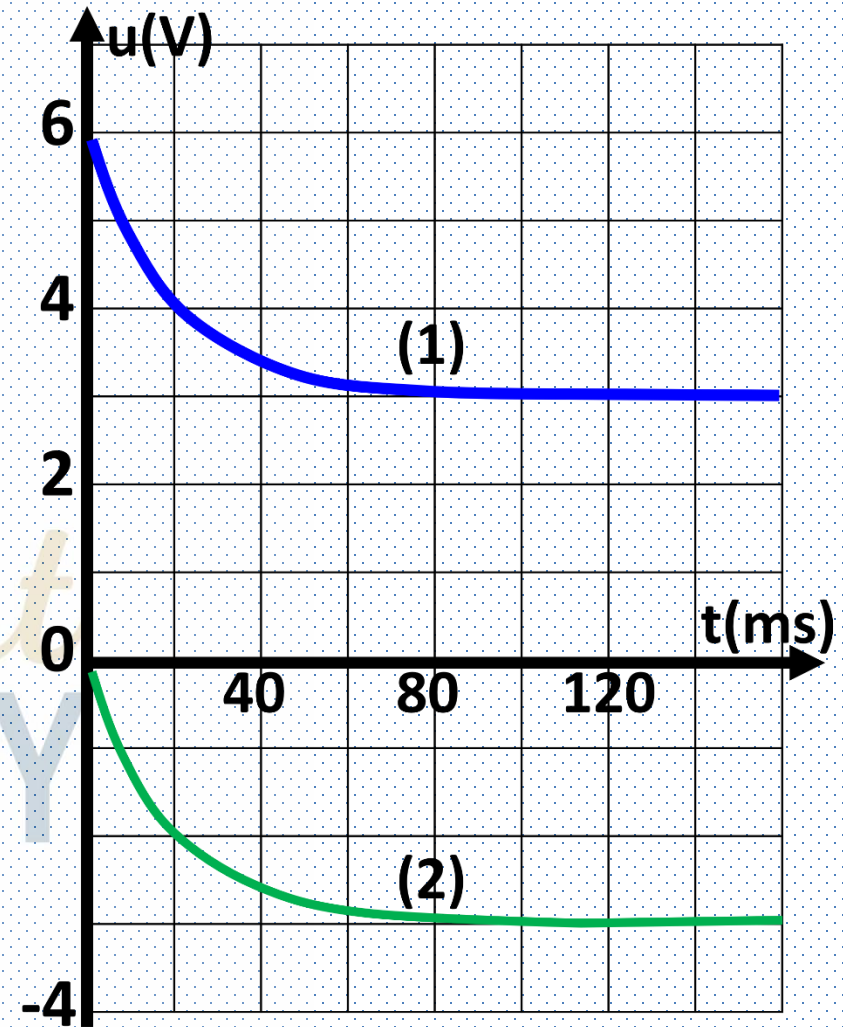

Exercise 1

5) Show that the equation of the tangent to the curve (2) at a point of abscissa t' is given by:


$$u = -\frac{RI_0}{\tau} \cdot e^{-\frac{t}{\tau}}(t - t') - RI_0(1 - e^{-\frac{t}{\tau}})$$

The slope of the tangent is given by:

$$\frac{du_{MB}}{dt} = -\frac{RI_0}{\tau} \cdot e^{-\frac{t}{\tau}}$$

At $t = t'$

$$\frac{du_{MB}}{dt} = -\frac{RI_0}{\tau} \cdot e^{-\frac{t'}{\tau}}$$

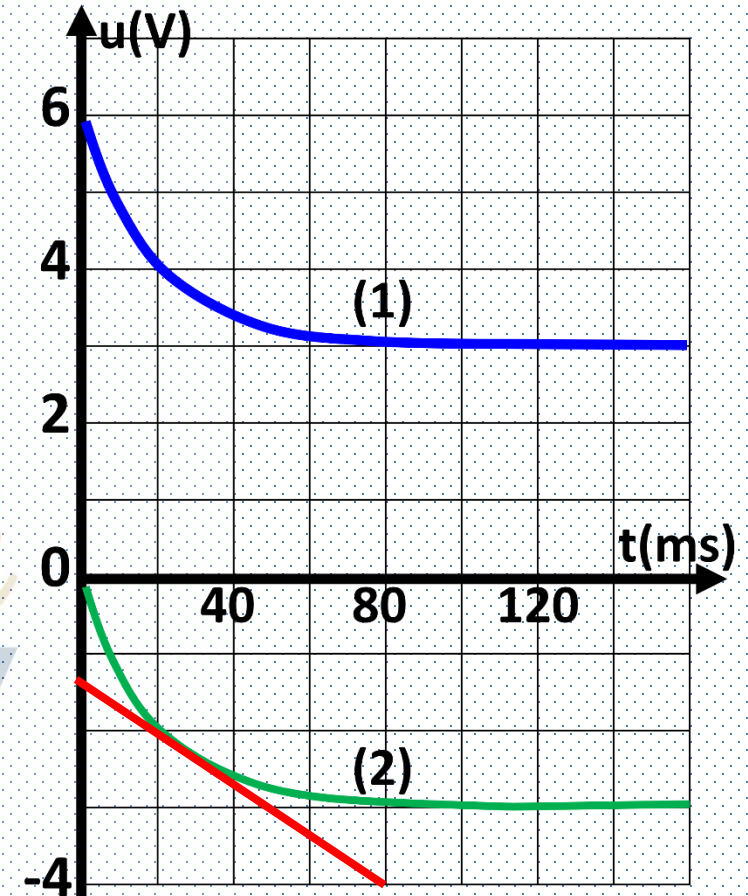

Exercise 1

The equation of the tangent is given by:


$$u = at + b$$

$$u = -\frac{RI_0}{\tau} \cdot e^{-\frac{t'}{\tau}} \cdot t + b$$

For $t = t'$

$$u = -RI_0(1 - e^{-\frac{t'}{\tau}})$$

$$-RI_0(1 - e^{-\frac{t'}{\tau}}) = -\frac{RI_0}{\tau} \cdot e^{-\frac{t'}{\tau}} \cdot t' + b$$

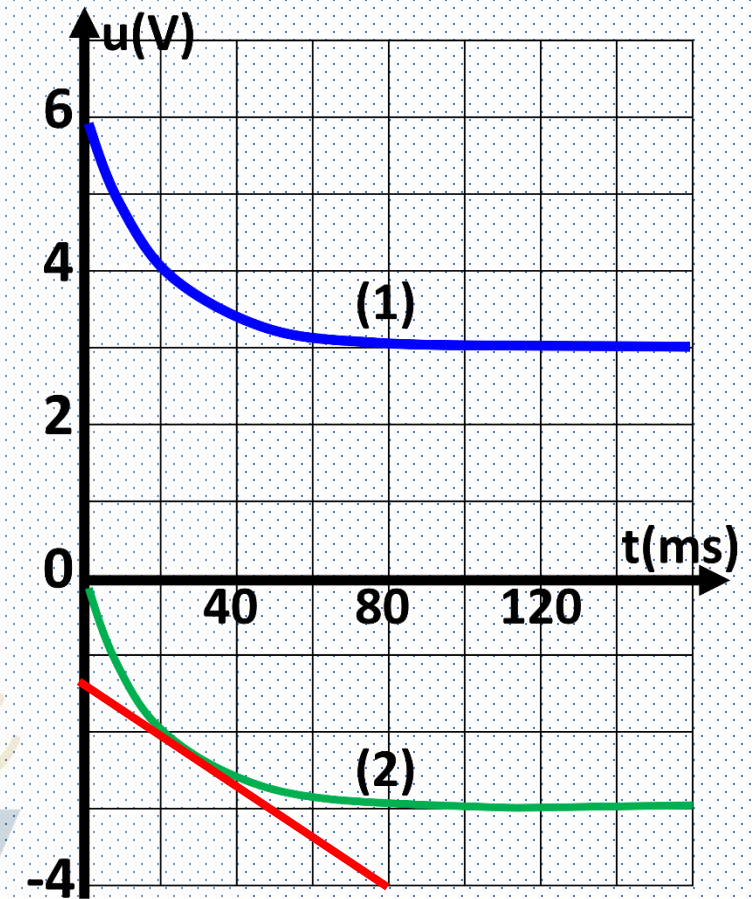

Exercise 1

$$-RI_0(1 - e^{-\frac{t'}{\tau}}) = -\frac{RI_0}{\tau} \cdot e^{-\frac{t'}{\tau}} \cdot t' + b$$

$$b = \frac{RI_0}{\tau} \cdot e^{-\frac{t'}{\tau}} \cdot t' - RI_0(1 - e^{-\frac{t'}{\tau}})$$

$$u = -\frac{RI_0}{\tau} \cdot e^{-\frac{t'}{\tau}} \cdot t + b$$

$$u = -\frac{RI_0}{\tau} \cdot e^{-\frac{t'}{\tau}} \cdot t + \frac{RI_0}{\tau} \cdot e^{-\frac{t'}{\tau}} \cdot t' - RI_0(1 - e^{-\frac{t'}{\tau}})$$

Exercise 1

$$u = -\frac{RI_0}{\tau} \cdot e^{-\frac{t'}{\tau}} \cdot t + \frac{RI_0}{\tau} \cdot e^{-\frac{t'}{\tau}} \cdot t' - RI_0 \left(1 - e^{-\frac{t'}{\tau}}\right)$$

$$u = -\frac{RI_0}{\tau} \cdot e^{-\frac{t'}{\tau}} \cdot [-t + t'] - RI_0 \left(1 - e^{-\frac{t'}{\tau}}\right)$$

Exercise 1

6) Show that this tangent meets the asymptote to this curve at a point of abscissa $t = t' + \tau$

The asymptote is $u = -RI_0$

$$u = -\frac{RI_0}{\tau} \cdot e^{-\frac{t'}{\tau}} \cdot [-t + t'] - RI_0 \left(1 - e^{-\frac{t'}{\tau}}\right)$$

$$-RI_0 = -\frac{RI_0}{\tau} \cdot e^{-\frac{t'}{\tau}} \cdot [-t + t'] - RI_0 \left(1 - e^{-\frac{t'}{\tau}}\right)$$

$$1 = \frac{1}{\tau} \cdot e^{-\frac{t'}{\tau}} \cdot [-t + t'] + 1 - e^{-\frac{t'}{\tau}}$$

Exercise 1

$$1 = \frac{1}{\tau} \cdot e^{-\frac{t'}{\tau}} \cdot [-t + t'] + 1 - e^{-\frac{t'}{\tau}}$$

$$0 = +\frac{1}{\tau} \cdot e^{-\frac{t'}{\tau}} \cdot [-t + t'] - e^{-\frac{t'}{\tau}}$$

$$e^{-\frac{t'}{\tau}} = \frac{1}{\tau} \cdot e^{-\frac{t'}{\tau}} \cdot [-t + t']$$

$$1 = \frac{1}{\tau} \cdot [-t + t']$$

$$\tau = [-t + t']$$

$$t' = \tau + t$$

Exercise 1

7) Deduce the values of τ and L .


From the graph $\tau = 20ms$

$$\tau = \frac{L}{r + R}$$


$$L = \tau(R + r)$$

$$L = 20 \times 10^{-3} (2.5 + 2.5)$$

$$L = 0.1H$$

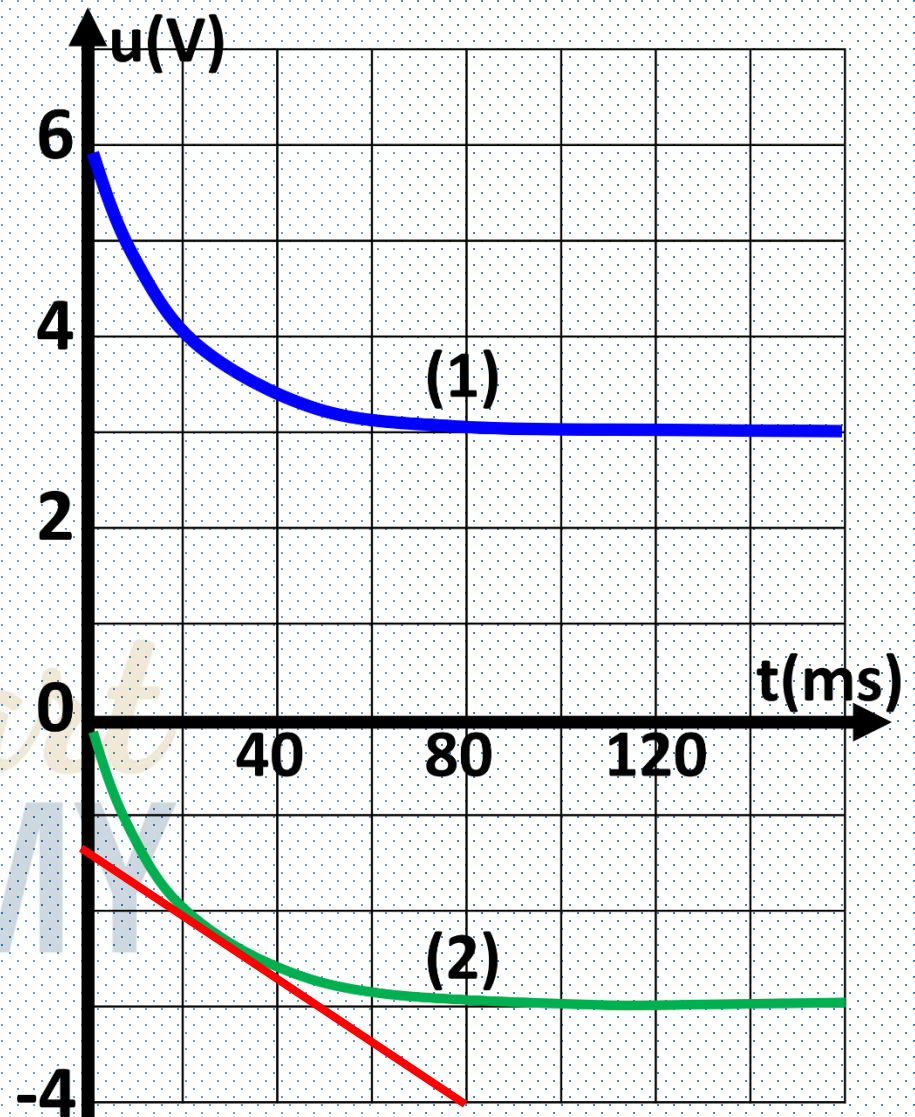

The End

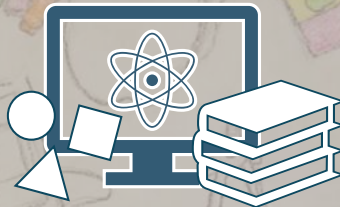


PROBLEM SOLVING



problem




thinking

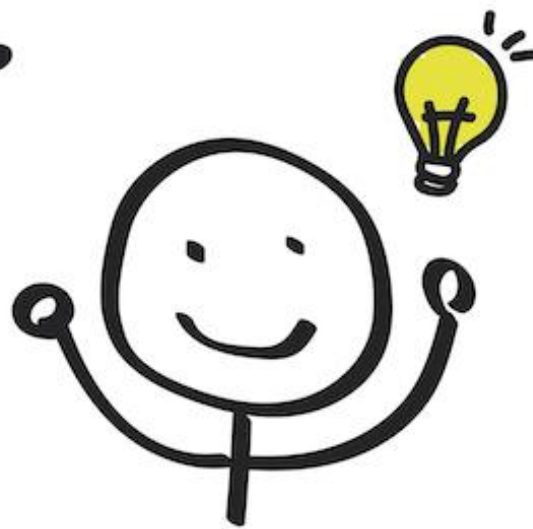

solution

Exercise 2

The figure below consists of an ideal generator of e.m.f E , a coil of internal resistance r & Inductance $L = 4mH$ and a resistor of resistance R .

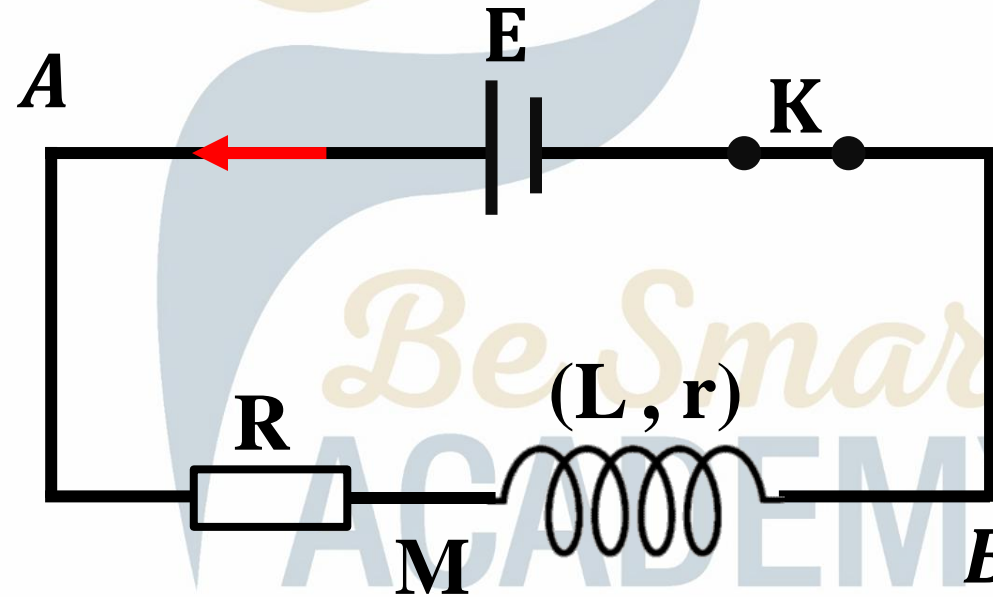

Exercise 2


Part A: Graphical study:

The adjacent curve represents the current in the circuit as a function of time. (T) is the tangent to this curve at the point of abscissa $t_0 = 0$.

1. Justify that the coil is the seat of self-induction in $[0; 10\text{ms}]$.

2. Calculate the self-induced e.m.f e_1 at $t_0 = 0$.

3. Justify that there is no induced e.m.f. after $t = 10\text{ms}$.

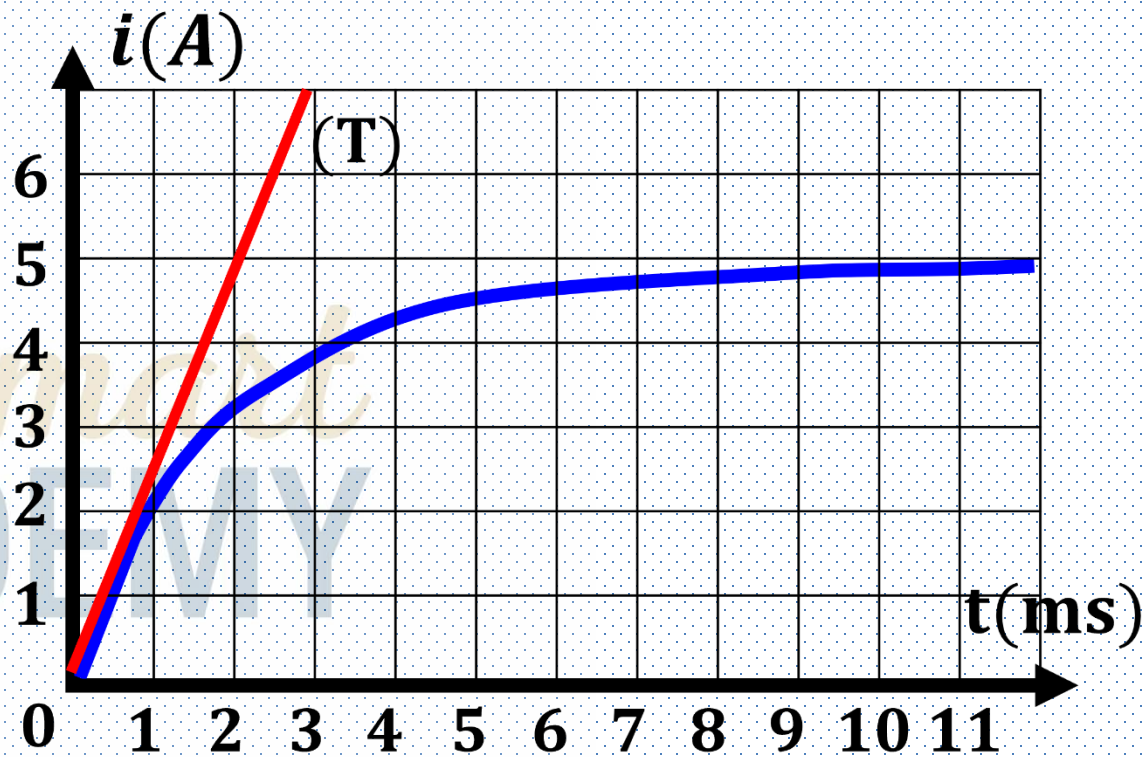


Exercise 2

1. Justify that the coil is the seat of self-induction in $[0; 10\text{ms}]$.

During the time interval $[0; 10\text{ms}]$, the current is variable, so the circuit is the seat of a self-induced e.m.f “e”

2. Calculate the self-induced e.m.f e_1 at $t_0 = 0$.

$$e = -L \frac{di}{dt} = -4 \times 10^{-3}$$

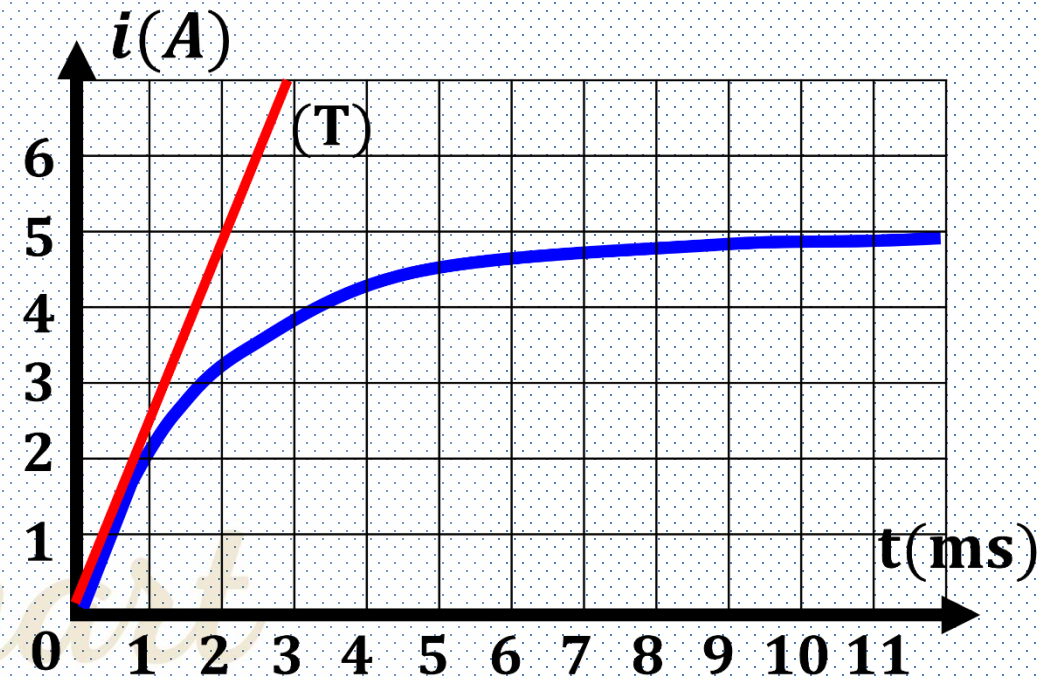


Exercise 2

2. Calculate the self-induced e.m.f e_1 at $t_0 = 0$.

$$e = -L \frac{di}{dt}$$

Where $\frac{di}{dt}$ is slope of tangent at $t = 0$
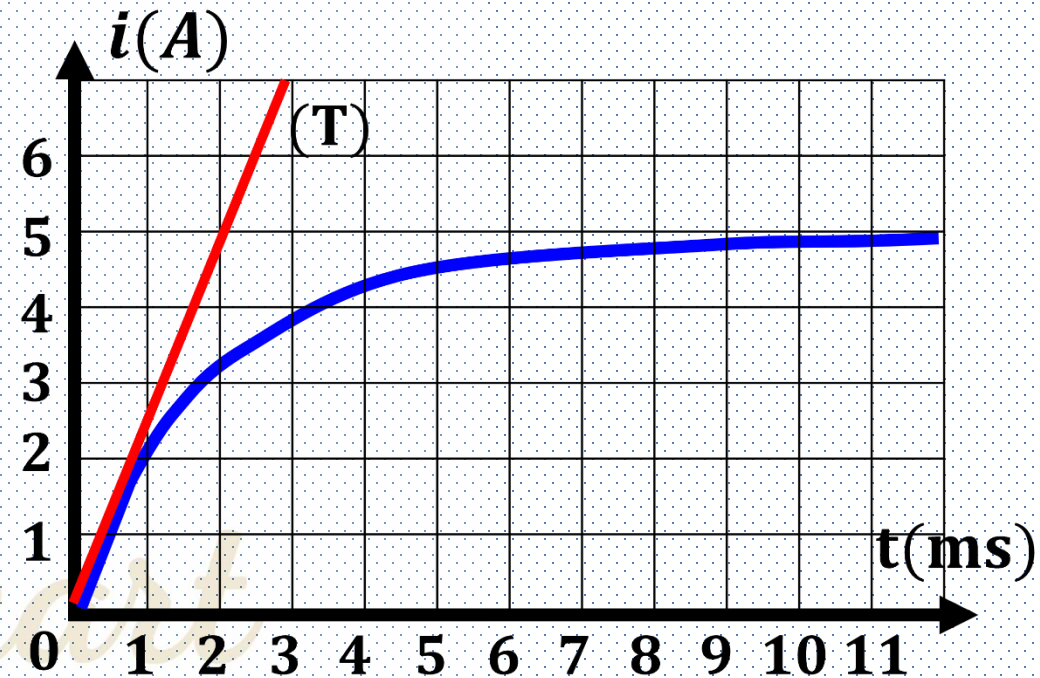
$$\frac{di}{dt} = \frac{\Delta i}{\Delta t} = \frac{5 - 0}{(2 - 0) \times 10^{-3}} = 2500 \text{ A/s}$$




$$e = -L \frac{di}{dt} \Rightarrow e = -4 \times 10^{-3} \times (2500) \Rightarrow e = -10 \text{ V}$$

Exercise 2

3. Justify that there is no induced e.m.f. after $t = 10\text{ms}$.

For $t > 10\text{ms}$, the steady state is reached, and the current becomes constant at maximum value.

$$e = -L \frac{di}{dt} = -L(0) = 0$$

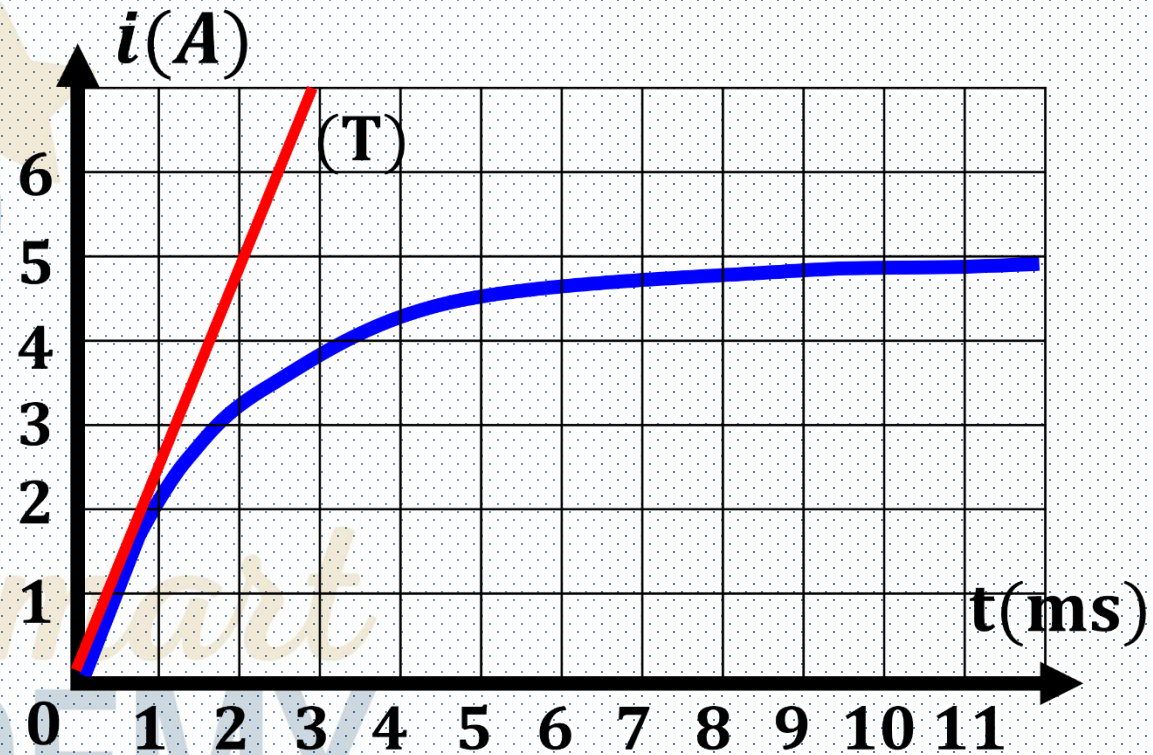


So, there is no induced e.m.f “e”

Exercise 2

4. Using the tangent (T), determine the value of the time constant τ .

The time constant τ is the abscissa of the point of intersection between the tangent (T) and the horizontal line $i = I_{max}$.

$$\tau = 2ms$$

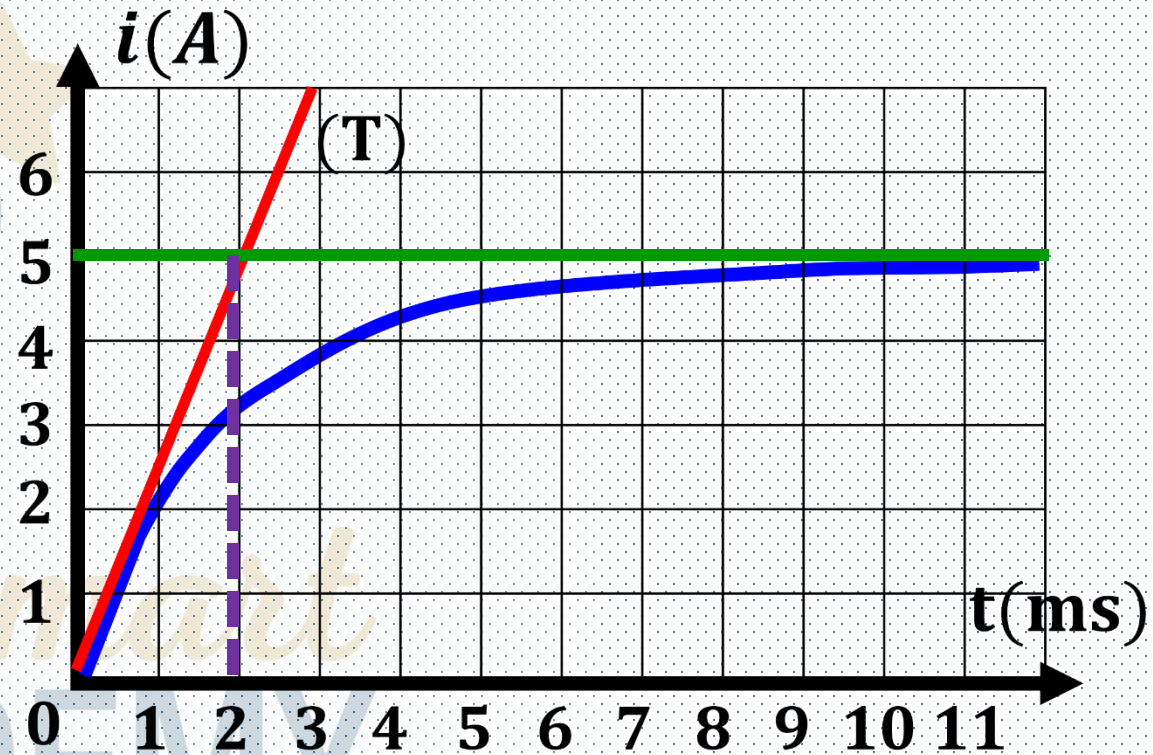


Exercise 2

5. Calculate the magnetic energy stored in the coil when the steady state is reached

$$E = \frac{1}{2} L I_0^2$$

$$E = 0.5 \times 4 \times 10^{-3} (5^2)$$

$$E = 0.05J$$

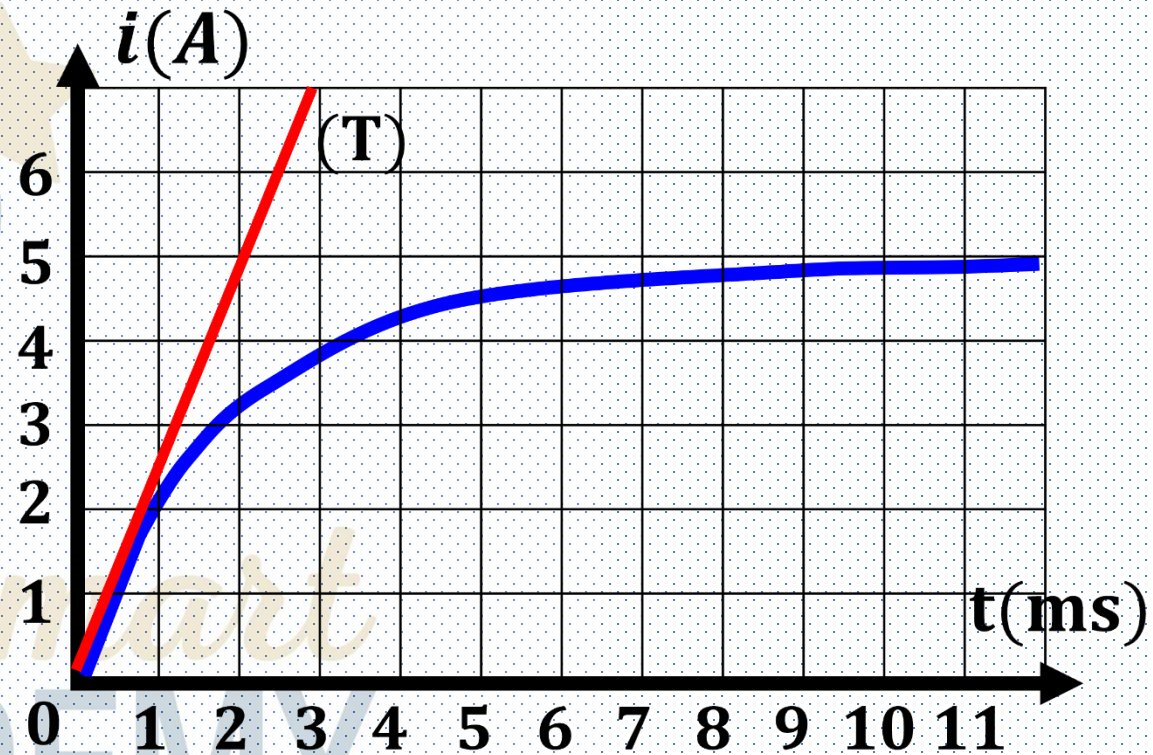

Exercise 2

Part B: Theoretical study:

1. Give the relation between the self-induced electromotive force e_1 , with L and $\frac{di}{dt}$.
2. Show that the differential equation that governs the evolution of the self-induced e.m.f. is given by:
$$\frac{de_1}{dt} + \left(\frac{R + r}{L} \right) \cdot e_1 = 0$$
3. Applying the law of addition of voltages, show that at $t_0 = 0$ the induced e.m.f. $e_1 = -E$

Exercise 2

Part B: Theoretical study:

1. Give the relation between the self-induced electromotive force e_1 , with L and $\frac{di}{dt}$.

$$e_1 = -\frac{d\phi}{dt}$$

Where the magnetic flux ϕ is given by $\phi = Li$

$$e_1 = -\frac{d\phi}{dt} = -\frac{d(Li)}{dt}$$

$$e_1 = -L \frac{di}{dt}$$

Exercise 2

2. Show that the differential equation that governs the evolution of the self-induced e.m.f. is given by:

$$\frac{de_1}{dt} + \left(\frac{R + r}{L} \right) \cdot e_1 = 0$$

$$u_{AB} = u_{AM} + u_{MB}$$

$$E = Ri + (ri - e_1)$$

$$E = (R + r)i - e_1$$

Exercise 2

$$E = (R + r)i - e_1$$

Derive this equation w.r.t time: $0 = (R + r) \frac{di}{dt} - \frac{de_1}{dt}$

But $e_1 = -L \frac{di}{dt}$

$$\frac{di}{dt} = -\frac{e_1}{L}$$

$$0 = (R + r) \left[-\frac{e_1}{L} \right] - \frac{de_1}{dt}$$

$$\frac{de_1}{dt} + \frac{(R + r)}{L} \cdot e_1 = 0$$

Exercise 2

3. Applying the law of addition of voltages, show that at $t_0 = 0$ the induced e.m.f. $e_1 = -E$

$$u_{AB} = u_{AM} + u_{MB}$$

$$E = Ri + (ri - e_1)$$

$$E = (R + r)i - e_1$$

At $t_0 = 0, i = 0$ then: $E = (R + r)(0) - e_1$

$$-E = e_1$$

Exercise 2

4. Determine the expressions of A & k so that $e_1 = Ae^{-kt}$ is a solution of the differential equation.

$$e_1 = Ae^{-kt}$$

$$\frac{de_1}{dt} = -Ake^{-kt}$$

Substitute e_1 and $\frac{de_1}{dt}$ in differential equation.

$$\frac{de_1}{dt} + \frac{(R+r)}{L} \cdot e_1 = 0$$

$$-Ake^{-kt} + \frac{(R+r)}{L} \cdot Ae^{-kt} = 0$$

Exercise 2

$$-Ake^{-kt} + \frac{(R+r)}{L} \cdot Ae^{-kt} = 0$$

$$+A \cdot e^{-kt} \left[-k + \frac{(R+r)}{L} \right] = 0$$

$$-k + \frac{(R+r)}{L} = 0$$

$$k = \frac{(R+r)}{L}$$

Exercise 2



$$e_1 = Ae^{-kt}$$

At $t=0$, $e_1 = -E$

$$-E = Ae^0$$

$$-E = A$$

$$e_1 = -Ee^{-\frac{(R+r)}{L}t}$$

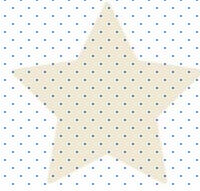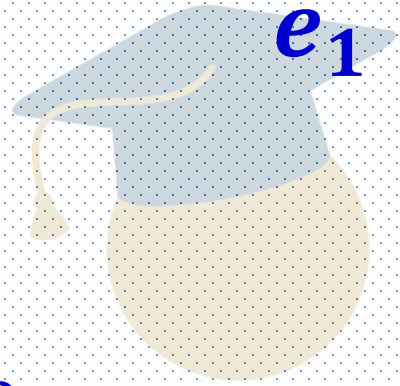

Be Smart

ACADEMY

Exercise 2

5. Deduce the role of the coil in the circuit.

Because the value of e_1 is negative ($e_1 < 0$) then:

The coil acts as a generator in opposition

6. Show that the expression of the current $i(t)$ can be written $i = a\left(1 - e^{-\frac{t}{\tau}}\right)$ where a & τ are constants whose expressions are to be determined.

$$e_1 = -L \frac{di}{dt} \Rightarrow -\frac{e_1}{L} = \frac{di}{dt} \Rightarrow di = -\frac{e_1}{L} dt$$

Exercise 2

$$di = -\frac{e_1}{L} dt \quad \Rightarrow \quad i = -\int \frac{e_1}{L} dt$$

$$i = -\frac{1}{L} \int e_1 dt$$

$$i = -\frac{1}{L} \int -E e^{-\frac{(R+r)}{L}t} dt$$

$$i = \frac{E}{L} \int e^{-\frac{(R+r)}{L}t} dt$$

Exercise 2

$$di = -\frac{e_1}{L} dt \quad \Rightarrow \quad i = -\int \frac{e_1}{L} dt$$

$$i = -\frac{1}{L} \int e_1 dt$$

$$i = -\frac{1}{L} \int -E e^{-\frac{(R+r)}{L}t} dt \quad \Rightarrow \quad i = \frac{E}{L} \int e^{-\frac{(R+r)}{L}t} dt$$

$$i = \frac{E}{L} \left[-\frac{1}{\frac{(R+r)}{L}} \right] e^{-\frac{(R+r)}{L}t} + C$$

Exercise 2

$$i = \frac{E}{L} \left[-\frac{1}{\frac{(R+r)}{L}} \right] e^{-\frac{(R+r)}{L}t} + C$$

$$i = -\frac{E}{L} \left[\frac{L}{R+r} \right] e^{-\frac{(R+r)}{L}t} + C \quad \Rightarrow \quad i = -\frac{E}{R+r} e^{-\frac{(R+r)}{L}t} + C$$

At $t = 0$; $i = 0$

$$0 = -\frac{E}{R+r} e^0 + C \quad \Rightarrow \quad C = \frac{E}{R+r}$$

Exercise 2

$$i = -\frac{E}{R+r} e^{-\frac{(R+r)}{L}t} + C$$

And

$$C = \frac{E}{R+r}$$

$$i = -\frac{E}{R+r} e^{-\frac{(R+r)}{L}t} + \frac{E}{R+r}$$

$$i = \frac{E}{R+r} \left(1 - e^{-\frac{(R+r)}{L}t} \right)$$

$$i = a \left(1 - e^{-\frac{t}{\tau}} \right)$$


The End




PROBLEM SOLVING



problem

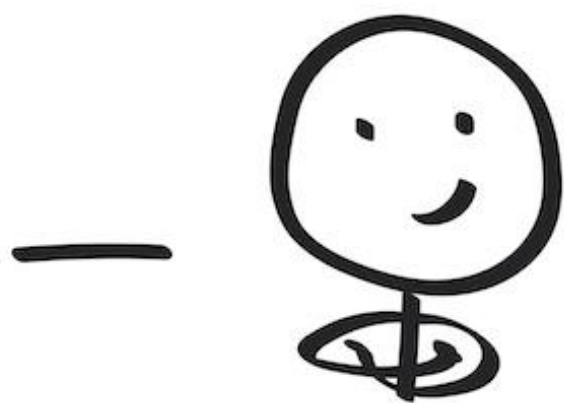

thinking

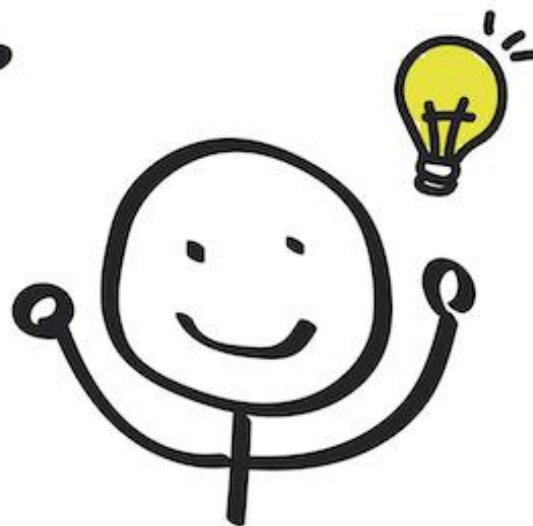


solution

Exercise 3:

The circuit of document 1 consists of:

- An ideal generator of constant electromotive force E .
- A coil of inductance L and resistance r .
- A resistor of resistance $R = 110\Omega$.
- A double switch K .; an ammeter and connecting wires.

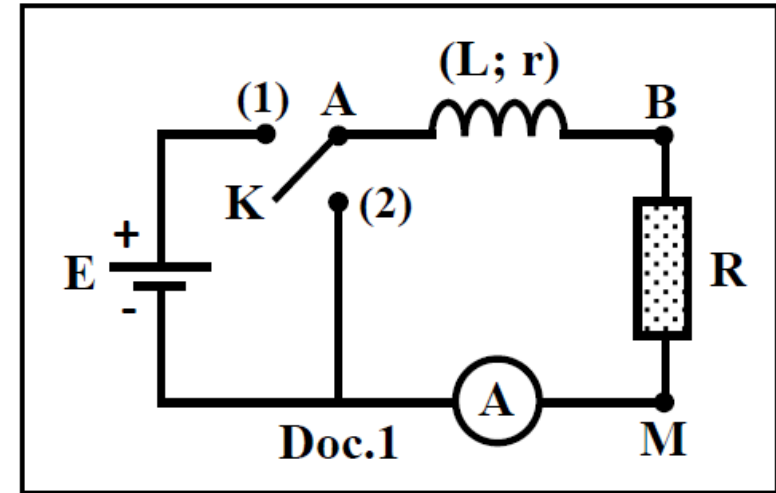The aim of this exercise is to determine the characteristics L and r of the coil.




A. Analytical study of the growth of the current.

At the instant $t_0 = 0$, the switch K is turned to position (1). At the instant t , the circuit carries an electric current i .

A convenient apparatus records the variations of the voltage $u_L = u_{AB}$ across the coil and the voltage $u_R = u_{BM}$ across the resistor. We obtain the waveforms of document 2.

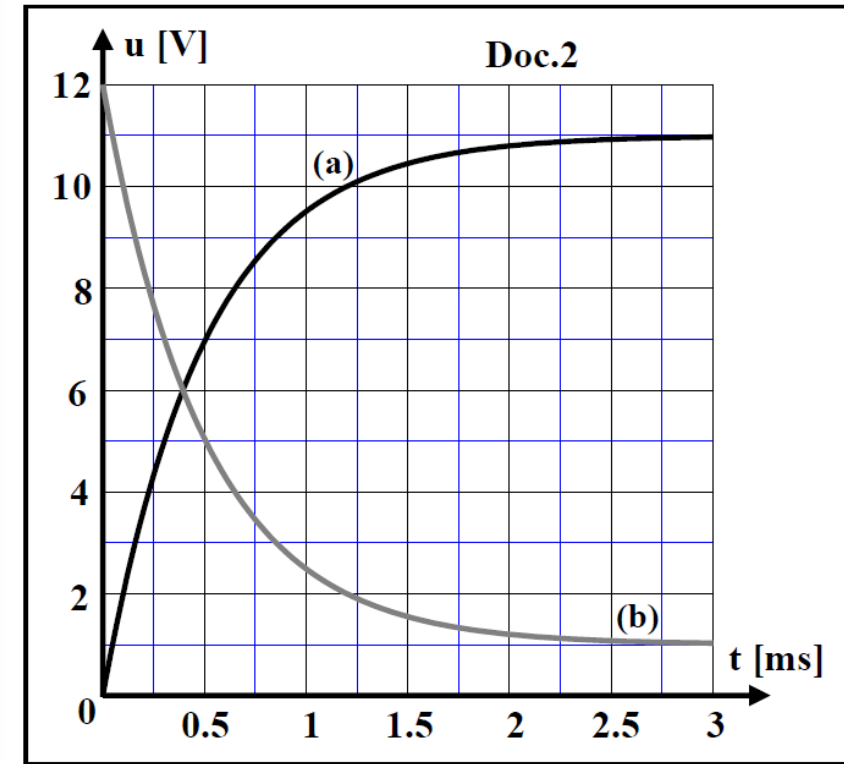1. Curve (a) represents the variation of u_R as a function of time. Why?
2. Applying the law of addition of voltages, derive the first order differential equation that governs the variation of the current i as a function of time.
3. Deduce the expression of the steady state current I_0 in terms of E , R and r .
4. The solution of the differential equation has the form $i = A + Be^{-\frac{t}{\tau}}$, where A , B and τ are constants. Determine the expressions of A , B and τ in terms of E , L , R and r .
5. Determine:
 - 5.1. the values of I_0 , r and E .
 - 5.2. the time constant τ ; then, deduce the value of L .



B. Analytical study of the decay of current

At a new origin of time t_0 , the switch K is turned to position (2). At the instant t , the circuit carries an electric current i .


1. Draw the circuit and indicate the direction of the electric current.
2. Show that the differential equation that governs the variation of the voltage u_R across the resistor is given by $\frac{du_R}{dt} + \frac{R+r}{L} u_R = 0$
3. The solution of the differential equation has the form $u_R = D e^{-\alpha t}$, where D and α are constants. Show that $D = R I_0$ and $\alpha = \frac{1}{\tau}$
4. Deduce that $i = I_0 e^{-\frac{t}{\tau}}$
5. Determine the magnetic energy W_m lost by the coil between $t_0 = 0\text{s}$ and $t_1 = \tau$.

6. The energy dissipated due to joule's effect in the resistor between t_0 and t_1 , is given by W_h

$$= \int_0^{t_1} Ri^2 dt.$$

6.1. Determine the value of W_h

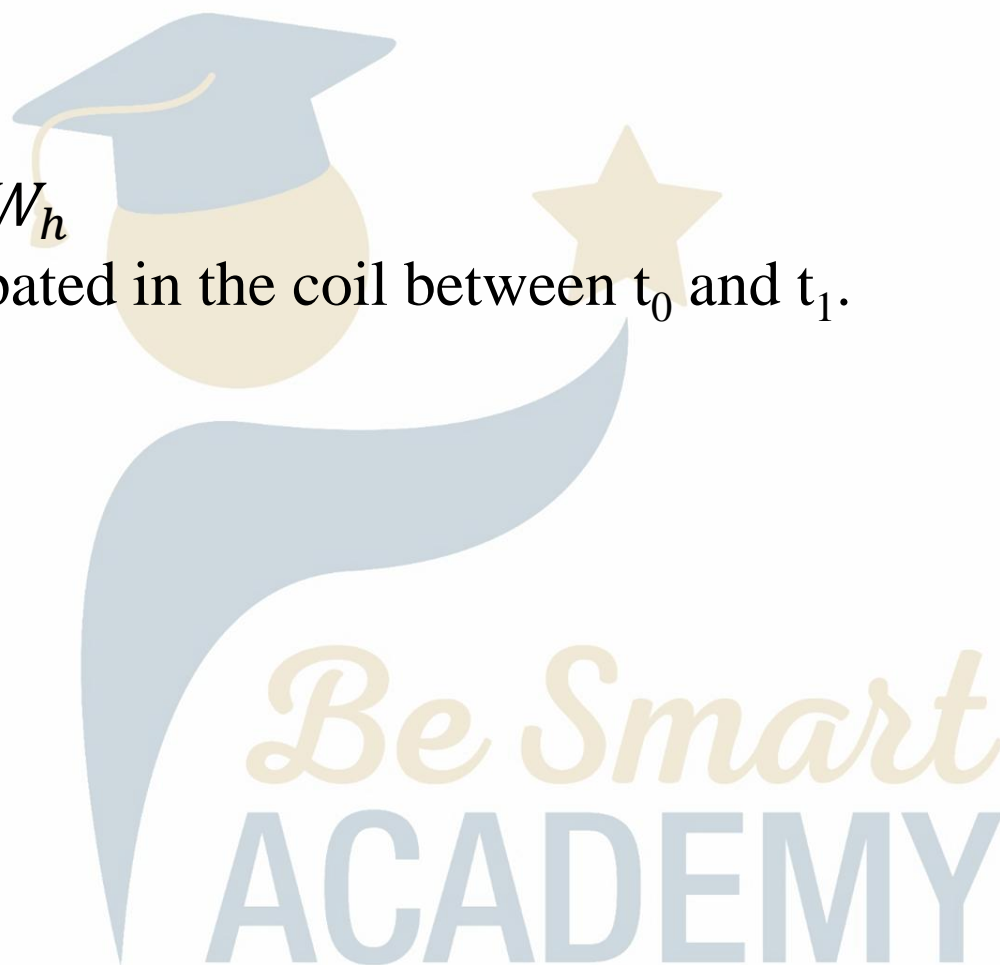6.2 Deduce the energy dissipated in the coil between t_0 and t_1 .



1. Curve (a) represents the variation of u_R as a function of time. Why?

Curve (a) corresponds to u_R since it increases exponentially with time.

2. Applying the law of addition of voltages, derive the first order differential equation that governs the variation of the current i as a function of time.

Law of addition of voltages:

$$u_{AM} = u_{AB} + u_{BM}$$

$$u_G = u_R + u_L \quad \Rightarrow$$


$$E = Ri + ri + L \frac{di}{dt}$$

$$E = (R + r)i + L \frac{di}{dt}$$

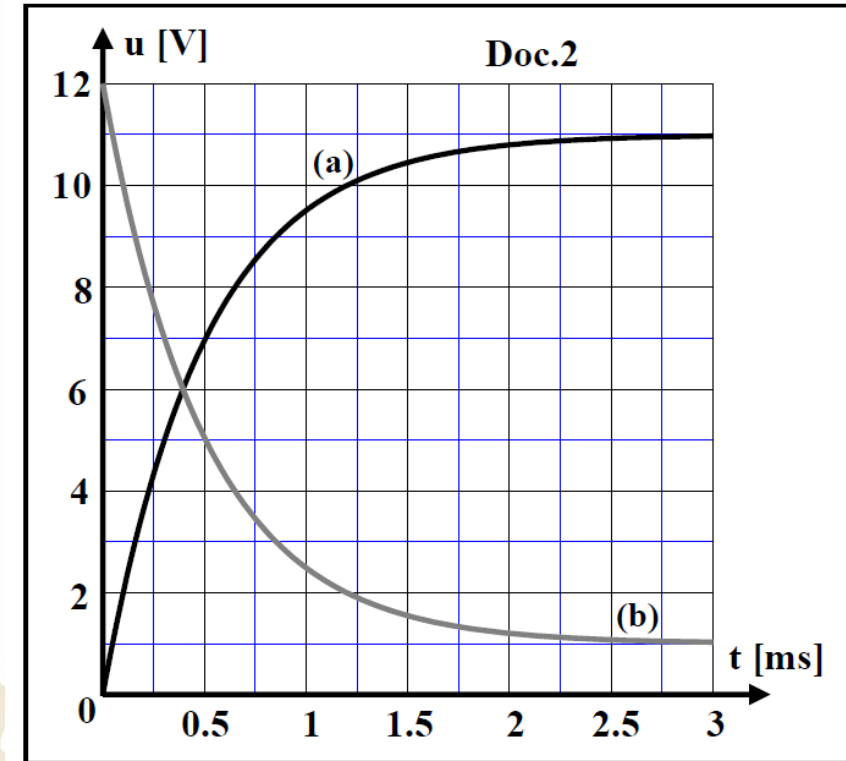3. Deduce the expression of the steady state current I_0 in terms of E , R and r .

In the steady state: $i = I_0 = \text{const}$ and $\frac{di}{dt} = 0$

$$\Rightarrow E = (R + r)I_0 + 0 \Rightarrow I_0 = \frac{E}{R + r}$$



4. The solution of the differential equation has the form $i = A + Be^{-\frac{t}{\tau}}$ where A, B and τ are constants. Determine the expressions of A, B and τ in terms of E, L, R and r.

$$i = A + Be^{-\frac{t}{\tau}} \Rightarrow \frac{di}{dt} = B\left(-\frac{1}{\tau}\right)e^{-\frac{t}{\tau}} \Rightarrow \frac{di}{dt} = -\frac{B}{\tau}e^{-\frac{t}{\tau}}$$

Replace i and di/dt in the differential equation: $\Rightarrow E = (R + r)(A + Be^{-\frac{t}{\tau}}) + L\left(-\frac{B}{\tau}e^{-\frac{t}{\tau}}\right)$

$$\Rightarrow E = (R + r)A + (R + r)Be^{-\frac{t}{\tau}} - L\left(\frac{B}{\tau}e^{-\frac{t}{\tau}}\right) \Rightarrow E + L\left(\frac{B}{\tau}e^{-\frac{t}{\tau}}\right) = (R + r)A + (R + r)Be^{-\frac{t}{\tau}}$$

By identification:

$$E = (R + r)A \Rightarrow A = \frac{E}{R + r}$$

$$\text{and } L\frac{B}{\tau} = (R + r)B \Rightarrow \tau = \frac{L}{R + r}$$

5. Determine:

5.1. the values of I_0 , r and E .

5.2. the time constant τ ; then, deduce the value of L .

5.1. In the steady state:

From graph: $u_R = 11V$ and $u_L = 1V$

$$u_R = RI_0 \Rightarrow I_0 = \frac{u_R}{R} \Rightarrow I_0 = \frac{11}{110} = 0.1A$$

$$u_L = rI_0 \Rightarrow r = \frac{u_L}{I_0} \Rightarrow r = \frac{1}{0.1} = 10\Omega$$


$$I_0 = \frac{E}{R+r} \Rightarrow E = (R+r)I_0$$

$$\Rightarrow E = (110+10) \times 0.1 = 12V$$

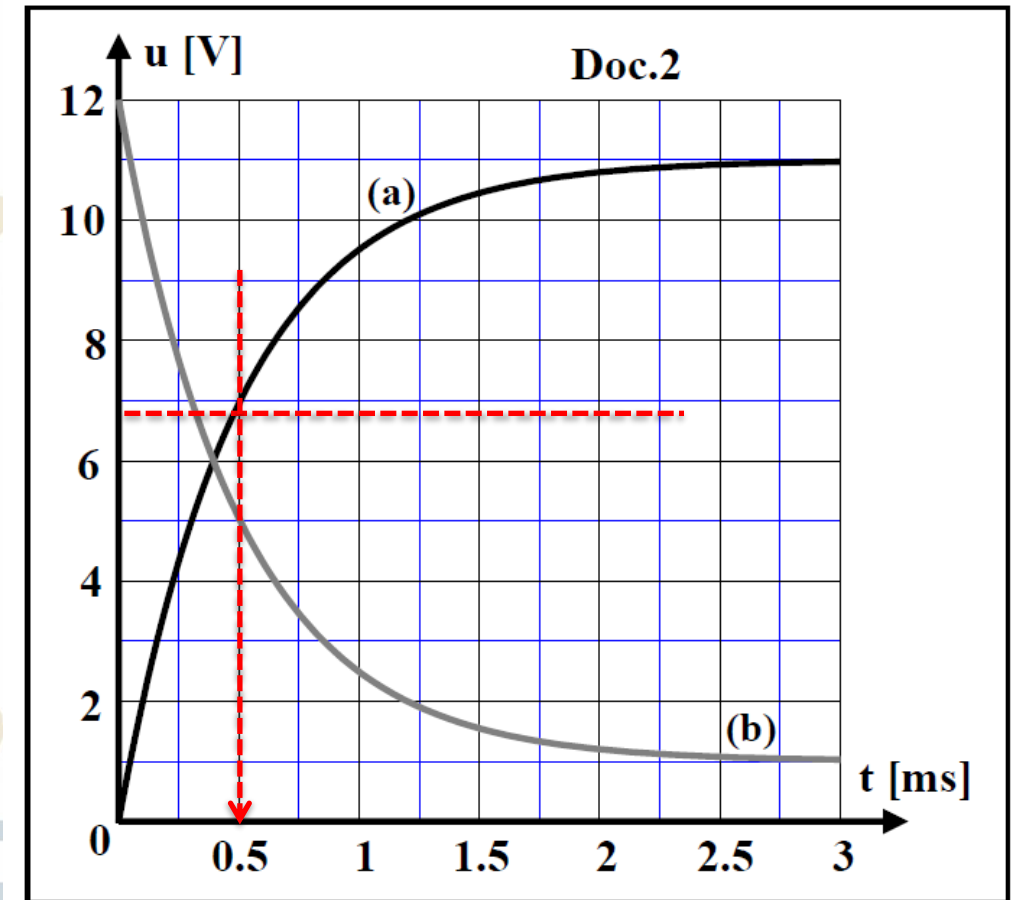5.2. At $t = \tau$; $u_R = 0.63u_{R_{\max}} = 0.63 \times 11 = 6.93V$.

Graphically, $\tau = 0.5ms$.

$$\text{But } \tau = \frac{L}{R+r} \Rightarrow L = (R+r)\tau = (110+10) \times 0.5 \times 10^{-3} \Rightarrow L = 0.06H$$



1. Draw the circuit and indicate the direction of the electric current.

2. Show that the differential equation that governs the variation of the voltage u_R across the resistor is given by $\frac{du_R}{dt} + \frac{R+r}{L}u_R = 0$

Apply law of addition of voltages:

$$u_L + u_R = 0 \Rightarrow ri + L \frac{di}{dt} + Ri = 0$$


$$\Rightarrow (R+r)i + L \frac{di}{dt} = 0$$

$$\text{But } u_R = Ri \Rightarrow i = \frac{u_R}{R}$$

$$\Rightarrow (R+r) \frac{u_R}{R} + L \frac{d(\frac{u_R}{R})}{dt} = 0$$

$$\text{Multiply by: } \frac{R}{L}$$
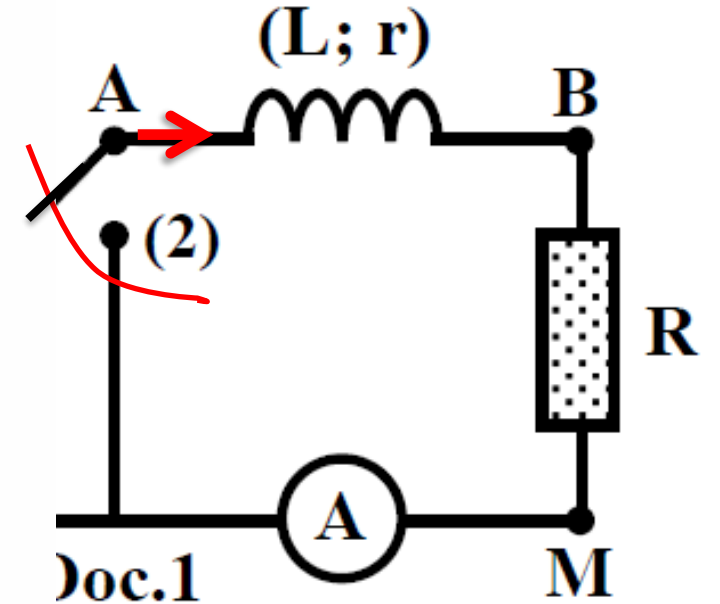
$$\Rightarrow \frac{du_R}{dt} + \frac{(R+r)}{L}u_R = 0$$



3. The solution of the differential equation has the form $u_R = De^{-\alpha t}$ where D and α are constants. Show that $D=RI_0$ and $\alpha = \frac{1}{\tau}$

$$u_R = De^{-\alpha t} \Rightarrow \frac{du_R}{dt} = D(-\alpha)e^{-\alpha t} = -D\alpha e^{-\alpha t}$$

Replace u_R and du_R/dt in the differential equation:

$$\Rightarrow -D\alpha e^{-\alpha t} + \frac{(R+r)}{L}(De^{-\alpha t}) = 0$$

$$\Rightarrow De^{-\alpha t}(-\alpha + \frac{(R+r)}{L}) = 0$$

$$\text{But } De^{-\alpha t} \neq 0 \Rightarrow (-\alpha + \frac{(R+r)}{L}) = 0 \Rightarrow \alpha = \frac{(R+r)}{L} = \frac{1}{\tau}$$

$$\text{At } t_0 = 0, i = I_0 \text{ and } u_R = RI_0 \Rightarrow RI_0 = De^0 \Rightarrow D = RI_0$$

4. Deduce that $i = I_0 e^{-\frac{t}{\tau}}$

$$u_R = D e^{-\alpha t} \Rightarrow Ri = D e^{-\alpha t} \Rightarrow i = \frac{D e^{-\alpha t}}{R} \Rightarrow i = \frac{R I_0 e^{-\frac{1}{\tau} t}}{R} \Rightarrow i = I_0 e^{-\frac{t}{\tau}}$$

5. Determine the magnetic energy W_m lost by the coil between $t_0 = 0$ s and $t_1 = \tau$.

$$\text{At } t = 0: i_0 = I_0 e^0 = 0.1 \text{ A}$$

$$\text{At } t_1 = \tau: i_1 = I_0 e^{-1} = 0.1 \times 0.37 = 0.037 \text{ A}$$

$$\text{Magnetic energy lost: } W_m = W_{t=0} - W_{t=\tau} \Rightarrow W_m = \frac{1}{2} L i_0^2 - \frac{1}{2} L i_1^2$$

$$\Rightarrow W_m = \frac{1}{2} L (i_0^2 - i_1^2) \Rightarrow W_m = \frac{1}{2} \times 0.06 (0.1^2 - 0.037^2) \Rightarrow W_m = 2.59 \times 10^{-4} \text{ J}$$

6. The energy dissipated due to joule's effect in the resistor between t_0 and t_1 , is given

by $W_h = \int_{t_0}^{t_1} Ri^2 dt$

6.1. Determine the value of W_h .

6.2 Deduce the energy dissipated in the coil between t_0 and t_1 .

$$6.1. W_h = \int_0^{t_1} Ri^2 dt \quad \Rightarrow W_h = \int_0^{t_1} R(I_0 e^{-\frac{t}{\tau}})^2 dt$$

$$\Rightarrow W_h = \int_0^{t_1} RI_0^2 e^{-\frac{2t}{\tau}} dt \quad \Rightarrow W_h = RI_0^2 \int_0^{t_1} e^{-\frac{2t}{\tau}} dt$$

$$\Rightarrow W_h = RI_0^2 \left\{ \left[\frac{1}{-\frac{2}{\tau}} \right] e^{-\frac{2t}{\tau}} \right|_0^{t_1 = \tau} \Rightarrow W_h = -\frac{RI_0^2 \tau}{2} e^{-\frac{2t}{\tau}} \bigg|_0^{t_1 = \tau} \Rightarrow W_h = -\frac{RI_0^2 \tau}{2} (e^{-2} - e^0)$$

$$\Rightarrow W_h = -\frac{110 \times 0.1^2 \times 0.5 \times 10^{-3}}{2} (e^{-2} - 1) \quad \Rightarrow W_h = 2.38 \times 10^{-4} J$$

$$6.2. W = W_m - W_h$$

$$\Rightarrow W = 2.59 \times 10^{-4} - 2.38 \times 10^{-4}$$

$$\Rightarrow W = 0.21 \times 10^{-4} \text{ J}$$

